

Chapter 5: Selectors and Shifters

Computer Structure - Spring 2004

Dr. Guy Even

Tel-Aviv Univ.

- p.1

Goals

- Selectors:
 - review definition of multiplexer.
 - build $(n : 1)$ -multiplexers.
- Shifters:
 - Cyclic shifter (Barrel shifter)
 - Logical Shifter
 - Arithmetic Shifter


- p.2

Multiplexer

DEF: A **mux-gate** (also known as a **$(2 : 1)$ -multiplexer**) is a combinational gate that has three inputs $D[0]$, $D[1]$, S and one output Y . The functionality is defined by

$$Y = \begin{cases} D[0] & \text{if } S = 0 \\ D[1] & \text{if } S = 1. \end{cases}$$

Equivalently: $Y = D[S]$

 

- p.3

Selectors

DEF: An $(n:1)$ -mux is a combinational circuit defined as follows:

Input: $D[n-1 : 0]$ and $S[k-1 : 0]$ where $k = \lceil \log_2 n \rceil$.

Output: $Y \in \{0, 1\}$.

Functionality:

$$Y = D[\langle \vec{S} \rangle].$$

Example: Let $n = 4$, $D[3 : 0] = 0101$, and $S[1 : 0] = 11$. The output Y should be 1.

- \vec{D} - data input
- \vec{S} - select input
- simplify: assume that n is a power of 2, namely, $n = 2^k$.

- p.4

Implementation of $(n:1)$ -MUX

We will present two implementations:


- a decoder based implementation
- a tree-like implementation

- p.5

$(n:1)$ -MUX : a decoder based implementation

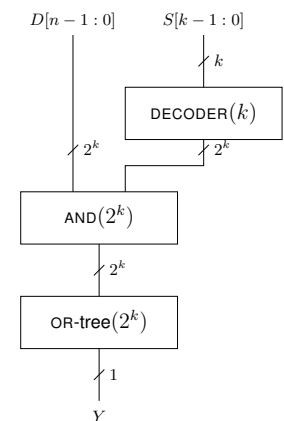
Question:

- correctness
- cost
- delay
- asymptotic optimality



- p.6

(n:1)-MUX : a tree-like implementation

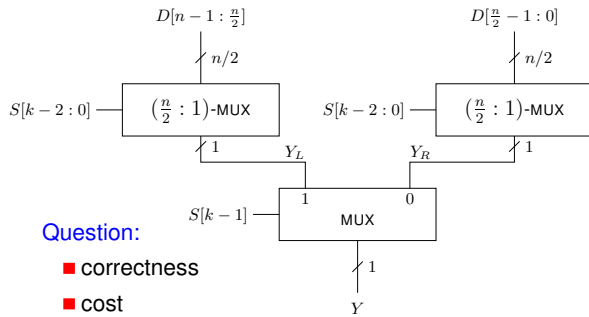

Question:

- correctness
- cost
- delay
- asymptotic optimality


- p.7

Which design is better?

- both designs are asymptotically optimal.
- based on the tables of Müller & Paul, the tree-like design is better.
- decision is based on specific gate costs in the technology one uses.
- fast MUX-gates in CMOS (transmission gates) do not restore the signals well.
⇒ long paths consisting only of MUX-gates are not allowed.

- p.8

Cyclic shift - example

 

- p.9

Cyclic shift - definition

The string $b[n-1:0]$ is a **cyclic left shift by i positions** of the string $a[n-1:0]$ if

$$\forall j : b[j] = a[\text{mod}(j-i, n)].$$

Example: Let $a[3:0] = 0010$. A cyclic left shift by one position of \bar{a} is the string 0100. A cyclic left shift by 3 positions of \bar{a} is the string 0001.

- p.10

Barrel Shifter

DEF: A **BARREL-SHIFTER**(n) is a combinational circuit defined as follows:

Input: $x[n-1:0]$ and $sa[k-1:0]$ where $k = \lceil \log_2 n \rceil$.

Output: $y[n-1:0]$.

Functionality: \vec{y} is a cyclic left shift of \vec{x} by $\langle s\bar{a} \rangle$ positions. Formally,

$$\forall j \in [n-1:0] : y[j] = x[\text{mod}(j - \langle s\bar{a} \rangle, n)].$$

- \vec{x} - data input
- $s\bar{a}$ - shift amount input
- simplify - assume that n is a power of 2, namely, $n = 2^k$.

- p.11

CLS(n, i) - Cyclic Left Shift by 2^i positions

DEF: A **CLS**(n, i) is a combinational circuit defined as follows:

Input: $x[n-1:0]$ and $s \in \{0, 1\}$.

Output: $y[n-1:0]$.

Functionality:

$$\forall j \in [n-1:0] : y[j] = x[\text{mod}(j - s \cdot 2^i, n)].$$


Equivalently,

$$y[j] = \begin{cases} x[j] & \text{if } s = 0 \\ x[\text{mod}(j - 2^i, n)] & \text{if } s = 1. \end{cases}$$

⇒ can implement CLS(n, i) with a row of n MUX-gates.

- p.12


CLS(4, 1)

 

Evident that a $\text{CLS}(n, i)$ requires a lot of area for the wires.
Our model does not capture routing cost.

- p.13

 BARREL-SHIFTER(n) - a chain of $\text{CLS}(n, i)$



- p.14

BARREL-SHIFTER(n) - correctness

Define the strings $y_i[n-1:0]$, for $0 \leq i \leq k-1$, recursively as follows:

$$y_0[n-1:0] \leftarrow \text{CLS}_{n,0}(x[n-1:0], sa[0])$$

$$y_{i+1}[n-1:0] \leftarrow \text{CLS}_{n,i+1}(y_i[n-1:0], sa[i+1])$$

Claim: $y_{k-1}[n-1:0]$ is a cyclic left shift of $x[n-1:0]$ by $\langle sa[k-1:0] \rangle$ positions.

Proof: Induction. $k=0$ - trivial because $\text{CLS}(n, 0)$ shifts by zero/one position.

- p.15

induction step

-
- $y_i[j] = \text{CLS}_{n,i}(y_{i-1}[n-1:0], sa[i])[j]$ (by definition of y_i)
 $= y_{i-1}[\text{mod}(j - 2^i \cdot sa[i], n)]$ (by definition of $\text{CLS}_{n,i}$).
- Let $\ell = \text{mod}(j - 2^i \cdot sa[i], n)$.
- Ind. Hyp. $\Rightarrow y_{i-1}[\ell] = x[\text{mod}(\ell - \langle sa[i-1:0] \rangle, n)]$.
- Note that

$$\text{mod}(\ell - \langle sa[i-1:0] \rangle, n) = \text{mod}(j - 2^i \cdot sa[i] - \langle sa[i-1:0] \rangle, n)$$

$$= \text{mod}(j - \langle sa[i:0] \rangle, n).$$
- Therefore $y_i[j] = x[\text{mod}(j - \langle sa[i:0] \rangle, n)]$, and the claim follows.

- p.16

Logical Shifting - motivation

- Used for shifting binary strings that represent unsigned integers in binary representation.
- Shifting to the left by s positions corresponds to

$$\langle \vec{y} \rangle \leftarrow \text{mod}(\langle \vec{x} \rangle \cdot 2^s, 2^n).$$
- Shifting to the right by s positions corresponds to

$$\langle \vec{y} \rangle \leftarrow \left\lfloor \frac{\langle \vec{x} \rangle}{2^s} \right\rfloor.$$

- p.17

Bi-Directional Logical Shifter - definition

A **LOG-SHIFT**(n) is a combinational circuit defined as follows:

Input:

- $x[n-1:0] \in \{0, 1\}^n$,
- $sa[k-1:0] \in \{0, 1\}^k$, where $k = \lceil \log_2 n \rceil$, and
- $\ell \in \{0, 1\}$.

Output: $y[n-1:0] \in \{0, 1\}^n$.

Functionality: If $\ell = 1$, then logical left shift as follows:

$$y[n-1:0] \triangleq x[n-1 - \langle \vec{sa} \rangle : 0] \cdot 0^{\langle \vec{sa} \rangle}.$$

If $\ell = 0$, then logical right shift as follows:

$$y[n-1:0] \triangleq 0^{\langle \vec{sa} \rangle} \cdot x[n-1 : \langle \vec{sa} \rangle].$$

- p.18

Bi-Directional Logical Shifter - example

Example: Let $x[3 : 0] = 0010$. If $sa[1 : 0] = 10$ and $\ell = 1$, then LOG-SHIFT(4) outputs $y[3 : 0] = 1000$. If $\ell = 0$, then the output equals $y[3 : 0] = 0000$.

- p.19

Bi-Directional Logical Shifter - implementation

- As in the case of cyclic shifters, we break the task of designing a logical shifter into sub-tasks of logical shifts by powers of two.
 - Loosely speaking, an $LBS(n, i)$ is a logical bi-directional shifter that outputs one of three possible strings:
 - the input shifted to the left by 2^i positions,
 - the input shifted to the right by 2^i positions, or
 - the input without shifting.
- We now formally define this circuit....

- p.20

$LBS(n, i)$ - definition

DEF: An $LBS(n, i)$ is a combinational circuit defined as follows:

Input: $x[n - 1 : 0]$ and $s, \ell \in \{0, 1\}$.

Output: $y[n - 1 : 0]$.

Functionality: Define $x'[n - 1 + 2^i : -2^i] \in \{0, 1\}^{n+2 \cdot 2^i}$ as follows:

$$x'[j] \triangleq \begin{cases} x[j] & \text{if } n < j \leq 0 \\ 0 & \text{otherwise.} \end{cases}$$

The value of the output $y[n - 1 : 0]$ is specified by

$$\forall j \in [n - 1 : 0] : y[j] = x'[j + (-1)^\ell \cdot s \cdot 2^i].$$


- p.21

$$y[j] = x'[j + (-1)^\ell \cdot s \cdot 2^i]$$

- $x'[n - 1 + 2^i : -2^i] = 0^{2^i} \cdot x[n - 1 : 0] \cdot 0^{2^i}$.
- ℓ - determines if the shift is a left shift or a right shift. If $\ell = 1$ then $(-1)^\ell = -1$, and the shift is a left shift (since increasing indexes from $j - 2^i$ to j has the effect of a left shift).
- s - determines if a shift (in either direction) takes place at all. If $s = 0$, then $y[j] = x[j]$, and no shift takes place.

- p.22

 
A bit-slice of an implementation of $LBS(n, i)$



 1. (3 : 1)-MUX. Implemented either by a "pruned" tree-like construction or we can simply consider a (3 : 1)-MUX as a basic gate. Simple circuit \Rightarrow best option can be easily determined based on the technology at hand.
2. decoding circuit - not a decoder! Decoding of s and ℓ causes the (3 : 1)-MUX to select the correct input.

- p.23

A bit-slice of an implementation of $LBS(n, i)$



Question: This question deals with various aspects and details concerning the design of a logical shifter.

1. Design a "pruned" tree-like (3 : 1)-MUX.
2. Design the decoding box.
3. Show how $LBS(n, i)$ circuits can be cascaded to obtain a LOG-SHIFT(n).
Hint: follow the design of a BARREL-SHIFTER(n).

- p.24

Arithmetic Shifters - motivation

- Used for shifting binary strings that represent signed integers in two's complement representation.
- logical left shifting = arithmetic left shifting.
- Arithmetic right shifting corresponds to dividing by a power of 2 (with sign extension).

- p.25

Arithmetic right shifter - definition

DEF: An $\text{ARITH-SHIFT}(n)$ is a combinational circuit defined as follows:

Input: $x[n-1:0] \in \{0,1\}^n$ and $sa[k-1:0] \in \{0,1\}^k$, where $k = \lceil \log_2 n \rceil$.

Output: $y[n-1:0] \in \{0,1\}^n$.

Functionality: The output \vec{y} is a (sign-extended) arithmetic right shift of \vec{x} by $\langle s\vec{a} \rangle$ positions. Formally,

$$y[n-1:0] \triangleq x[n-1]^{(s\vec{a})} \cdot x[n-1:\langle s\vec{a} \rangle].$$

Example: Let $x[3:0] = 1001$. If $sa[1:0] = 10$, then $\text{ARITH-SHIFT}(4)$ outputs $y[3:0] = 1110$.

- p.26

Arithmetic right shifter - implementation

Question: Consider the definitions of $\text{CLS}(n,i)$ and $\text{LBS}(n,i)$. Suggest an analogous definition $\text{ARS}(n,i)$ for arithmetic right shift (i.e., modify the definition of \vec{x}^i and use $(2:1)\text{-MUXs}$). Suggest an implementation of an arithmetic right shifter based on cascading $\text{ARS}(n,i)$ circuits.

- p.27

Further questions

Question: Design a bi-directional cyclic shifter. Such a shifter is like a cyclic left shifter but has an additional input $\ell \in \{0,1\}$ that indicates the direction of the required shift. Hint: Consider reducing a cyclic right shift to a cyclic left shifter. To simplify the reduction you may assume that $n = 2^k - 1$ (hint: use one's complement negation). Suggest a simple reduction in case $n = 2^k$ (hint: avoid explicit subtraction!).

- p.28

Further questions - cont.

Question: CPUs often support all three types of shifting: cyclic, logical, and arithmetic shifting.

1. Write a complete specification of a shifter that can perform all three types of shifts.
2. Propose an implementation of such a shifter.

- p.29

Summary

- $(n:1)$ -multiplexers:
 - definition.
 - two implementations: decoder based & tree-like.
 - both designs are optimal.
- three types of shifts: cyclic, logical, and arithmetic shifts.
- Design method: cascade a logarithmic number of shifters (with parameter i) that either perform a shift by 2^i positions or no shift at all.

- p.30