

Chapter 6: Priority Encoders

Computer Structure - Spring 2004

Dr. Guy Even

Tel-Aviv Univ.

Leading One

Consider a binary string $x[0 : n - 1]$ (ascending indexes!).

DEF: The **leading one** of a binary string $x[0 : n - 1]$ is defined by

$$\text{LEADING-ONE}(x[0 : n - 1]) \triangleq \begin{cases} \min\{i \mid x[i] = 1\} & \text{if } x[0 : n - 1] \neq 0^n \\ n & \text{otherwise.} \end{cases}$$

Example: Consider the string $x[0 : 6] = 0110100$. The leading one is the index [1]. Note that indexes are in ascending order and that $x[0]$ is the leftmost bit.

Claim: For every binary string $x[n - 1 : 0]$

$$\text{LEADING-ONE}(\vec{a}) = \text{LEADING-ONE}(\vec{a} \cdot 1).$$

Unary Representation

DEF: A binary string $x[0 : n - 1]$ represents a number in **unary representation** if $x[0 : n - 1] \in 1^* \cdot 0^*$. The **value represented in unary representation** by the binary string $1^i \cdot 0^j$ is i .

Example: The binary string 01001011 does not represent a number in unary representation. Only a string that is obtained by concatenating an all-ones string with an all-zeros string represents a number in unary representation.

Parallel Prefix Computation

DEF: A **parallel prefix computation OR circuit** of length n is a combinational circuit specified as follows.

Input: $x[0 : n - 1]$.

Output: $y[0 : n - 1]$.

Functionality:

$$y[i] = \text{OR}(x[0 : i]).$$

We denote parallel prefix computation OR circuit of length n by $\text{PPC-OR}(n)$.

Priority Encoders

- A priority encoder is a combinational circuit that computes the leading one.
- We consider two types of priority encoders:
 - A unary priority encoder - outputs the leading one in unary representation.
 - A binary priority encoder - outputs the leading one in binary representation.

Unary priority encoder

DEF: A **unary priority encoder** $\text{U-PENC}(n)$ is a combinational circuit specified as follows.

Input: $x[0 : n - 1]$.

Output: $y[0 : n - 1]$.

Functionality:

$$y[i] = \text{INV}(\text{OR}(x[0 : i])).$$

Example:

- If $x[0 : 6] = 0110100$, then $\text{PPC-OR}(7)$ outputs 0111111. $\text{U-PENC}(7)$ outputs 1000000.
- If $\vec{x} \neq 0^n$, then $\text{U-PENC}(n)$ outputs $y[0 : n - 1] = 1^j \cdot 0^{n-j}$, where $j = \min\{i \mid x[i] = 1\}$.
- If $\vec{x} = 0^n$, then $\vec{y} = 1^n$ and \vec{y} is a unary representation of n .

- p.1

- p.2

- p.3

- p.4

- p.5

- p.6

Binary Priority Encoder

DEF: A **binary priority encoder** $B\text{-PENC}(n)$ is a combinational circuit specified as follows.

Input: $x[0 : n - 1]$.

Output: $y[k : 0]$, where $k = \lfloor \log_2 n \rfloor$. (Note that if $n = 2^\ell$, then $k = \ell$.)

Functionality:

$$\langle \vec{y} \rangle = \text{LEADING-ONE}(\vec{x})$$

$n = 2^k \implies$ length of the output of a $B\text{-PENC}(n)$ is $k + 1$ bits; otherwise, the number n could not be represented by the output.

Example: Given input $x[0 : 5] = 000101$, a $B\text{-PENC}(6)$ outputs

$y[0 : 5] = 000111$, and $B\text{-PENC}(6)$ outputs $y[2 : 0] = 011$.

- p.7


$U\text{-PENC}(n)$ - Implementation

- Invert the outputs of a $PPC\text{-OR}(n)$.
- Brute force design of $PPC\text{-OR}(n)$:
 - separate OR-tree for each output bit.
 - delay = $O(\log n)$
 - cost = $O(n^2)$.
- How can we efficiently combine these trees? To be discussed in detail when we discuss fast addition.
- We now present a (non-optimal) design based on divide-and-conquer.

divide & conquer $PPC\text{-OR}(n)$

If $n = 1$, then $y[0] \leftarrow x[0]$.


If $n > 1$:

 

- p.8

- p.9

 divide & conquer $PPC\text{-OR}(n)$ - cont.



Question:

1. Prove the correctness of the design.
2. Extend design for values of n that are not powers of 2.
3. Analyze the delay and cost of the design.
4. Prove the asymptotic optimality of the delay of the design.

- p.10

divide & conquer $PPC\text{-OR}(n)$ - cost analysis

$$c(n) = \begin{cases} 0 & \text{if } n=1 \\ 2 \cdot c\left(\frac{n}{2}\right) + (n/2) \cdot c(\text{OR}) & \text{otherwise.} \end{cases}$$

It follows that

$$\begin{aligned} c(n) &= 2 \cdot c\left(\frac{n}{2}\right) + \Theta(n) \\ &= \Theta(n \cdot \log n). \end{aligned}$$

Question: Prove a lower bound on $c(PPC\text{-OR}(n))$.

Promise: In the chapter on fast addition we will present a cheaper implementation of $PPC\text{-OR}(n)$ (with logarithmic delay).

- p.11


Implementation of a binary priority encoder

We present two designs for a binary priority encoder.

- design based on a reduction to $PPC\text{-OR}(n)$.
- design based on divide-and-conquer


- p.12

reduction of B-PENC(n) to PPC-OR(n)

 


- p.13

cost analysis

 


- p.14

delay analysis

 

- p.15

 B-PENC(n): a divide-and-conquer design for $n = 2^k$




- p.16

correctness

We prove correctness by induction.

- Induction basis: $n = 1$ is trivial.
- Induction step deals with 3 cases:
 - leading one is in left half $x[0 : \frac{n}{2} - 1]$.
 - leading one is in right half $x[\frac{n}{2} : n - 1]$.
 - $\vec{x} = 0^n$.

 
correctness: case $x[0 : \frac{n}{2} - 1] \neq 0^{n/2}$



- p.17

- p.18

 
correctness: case $x[0 : \frac{n}{2} - 1] = 0^{n/2}$ & $x[\frac{n}{2} : n - 1] \neq 0^{n/2}$



- Ind. Hyp. \Rightarrow index of the leading one is $n/2 + \langle y_R \rangle$.
- \Rightarrow required output is $0 \cdot 1 \cdot y_R[k-2:0]$.
- Ind. Hyp. $\Rightarrow y_L[k-1] = 1$ and $y_R[k-1] = 0$.
- $\Rightarrow y[k] = 0$ & $y[k-1] = 1$.
- $y_L[k-1] = 1 \Rightarrow y[k-2:0] = y_R[k-2:0]$.

- p.19

 
correctness: case $x[0 : \frac{n}{2} - 1] = 0^{n/2}$ & $x[\frac{n}{2} : n - 1] = 0^{n/2}$



- required output is $1 \cdot 0^k$.
- Ind. Hyp. $\Rightarrow y_L[k-1:0] = y_R[k-1:0] = 1 \cdot 0^{k-1}$.
- $y_L[k-1] = y_R[k-1] = 1 \Rightarrow y[k] = 1$.
- $y_L[k-1] = y_R[k-1] = 1 \Rightarrow y[k-1] = 0$.
- $y_L[k-1] = 1 \Rightarrow y[k-2:0] = y_R[k-2:0] = 0^{k-1}$.

- p.20

cost analysis

 


$$c(B\text{-PENC}(n)) = \begin{cases} c(\text{NOR}) & \text{if } n=2 \\ 2 \cdot c(B\text{-PENC}(n/2)) + 2 \cdot c(\text{AND}) \\ + (k-1) \cdot c(\text{MUX}) & \text{otherwise.} \end{cases}$$

Solution is $c(n) = O(n)$, same recurrence as for ENCODER''(k) with substitution $k = \log n$.

- p.21

delay analysis

 

$$d(B\text{-PENC}(n)) = \begin{cases} t_{pd}(\text{NOR}) & \text{if } n=2 \\ d(B\text{-PENC}(n/2)) + \max\{d(\text{MUX}), d(\text{AND})\} & \text{otherwise.} \end{cases}$$

$\Rightarrow d(B\text{-PENC}(n)) = O(\log n)$

- p.22

Summary - priority encoders

- Two types of priority encoders: U-PENC(n) & B-PENC(n).
- Implementation of U-PENC(n):
 - brute force (separate OR-trees): cost $O(n^2)$, delay $O(\log n)$.
 - divide-&-conquer: cost $O(n \log n)$, delay $O(\log n)$.
 - to be shown: cost $O(n)$ and delay $O(\log n)$.
- Implementation of B-PENC(n):
 - reduction to U-PENC: overhead in cost - $O(n)$ & delay - $O(\log n)$.
 - divide-&-conquer: cost $O(n)$, delay $O(\log n)$.

- p.23