

Chapter 6: Addition

Computer Structure - Spring 2004

©Dr. Guy Even

Tel-Aviv Univ.

- p.1

Goals

- Binary addition - definition
- Ripple Carry Adder - definition, correctness, cost, delay
- Carry bits - definition, properties
- (*) Conditional Sum Adder - definition, correctness, cost, delay
- (*) Compound Adder - definition, correctness, cost, delay

- p.2

Binary Addition

DEF: A **binary adder** with input length n is a combinational circuit specified as follows.

Input: $A[n-1:0], B[n-1:0] \in \{0,1\}^n$, and $C[0] \in \{0,1\}$.

Output: $S[n-1:0] \in \{0,1\}^n$ and $C[n] \in \{0,1\}$.

Functionality:

$$\langle \vec{S} \rangle + 2^n \cdot C[n] = \langle \vec{A} \rangle + \langle \vec{B} \rangle + C[0]$$

- \vec{A}, \vec{B} - binary representations of the addends.
- $C[0]$ - the **carry-in bit**.
- \vec{S} - binary representation of the sum.
- $C[n]$ - the **carry-out bit**.

Question: is the functionality of $\text{ADDER}(n)$ is well defined?

- p.3

Lower bounds

Prove that for every $\text{ADDER}(n)$:

- $c(\text{ADDER}(n)) = \Omega(n)$
- $d(\text{ADDER}(n)) = \Omega(\log n)$

- p.4

Full Adder


A **Full-Adder** is a combinational circuit with 3 inputs $x, y, z \in \{0,1\}$ and 2 outputs $c, s \in \{0,1\}$ that satisfies:

$$2c + s = x + y + z.$$

- A Full Adder computes a binary representation of the sum of 3 bits.
- s - called the **sum output**.
- c - called the **carry-out output**.
- We denote a Full-Adder by FA .

- p.5

Ripple Carry Adder - $\text{RCA}(n)$

 

- carry-out output of FA_i is denoted by $c[i+1]$.
- weight of every signal is two to the power of its index.
- $\text{RCA}(n)$ - algorithm that we use for adding numbers by hand.

- p.6


Correctness proof

To facilitate the proof, we use an equivalent recursive definition of $RCA(n)$.

The recursive definition is as follows.

■ Basis: an $RCA(1)$ is simply a Full-Adder.

■ Step:

 

- p.7

Correctness - cont.

The proof is by induction on n .

The induction basis, for $n = 1$, follows directly from the definition of a Full-Adder.

- p.8

Induction Step

The induction hypothesis, for $n - 1$, is

$$(1) \quad \langle A[n-2:0] \rangle + \langle B[n-2:0] \rangle + C[0] = 2^{n-1} \cdot C[n-1] + \langle S[n-2:0] \rangle.$$

Full-Adder definition

$$(2) \quad A[n-1] + B[n-1] + C[n-1] = 2 \cdot C[n] + S[n-1].$$

Multiply (2) by 2^{n-1} to obtain

$$(3) \quad 2^{n-1} \cdot A[n-1] + 2^{n-1} \cdot B[n-1] + 2^{n-1} \cdot C[n-1] = 2^n \cdot C[n] + 2^{n-1} \cdot S[n-1].$$

- p.9

$$(1) \quad \langle A[n-2:0] \rangle + \langle B[n-2:0] \rangle + C[0] = 2^{n-1} \cdot C[n-1] + \langle S[n-2:0] \rangle.$$

$$(3) \quad 2^{n-1} \cdot A[n-1] + 2^{n-1} \cdot B[n-1] + 2^{n-1} \cdot C[n-1] = 2^n \cdot C[n] + 2^{n-1} \cdot S[n-1].$$

Note that $2^{n-1} \cdot A[n-1] + \langle A[n-2:0] \rangle = \langle A[n-1:0] \rangle$.

(1) + (3) \implies

$$2^{n-1} \cdot C[n-1] + \langle A[n-1:0] \rangle + \langle B[n-1:0] \rangle + C[0] = 2^n \cdot C[n] + 2^{n-1} \cdot C[n-1] + \langle S[n-1:0] \rangle.$$

Cancel out $2^{n-1} \cdot C[n-1]$. QED.

- p.10

Cost & Delay Analysis

The cost of an $RCA(n)$ satisfies:

$$c(RCA(n)) = n \cdot c(FA) = \Theta(n).$$

The delay of an $RCA(n)$ satisfies

$$d(RCA(n)) = n \cdot d(FA) = \Theta(n).$$

- p.11


Is $RCA(n)$ good enough?

- Clock rate = $1GHz = 10^9Hz$
 \implies clock period = $10^{-9}sec = 1ns$.
- Delay of gate $\approx 100ps = 0.1ns$.
- $d(FA) \approx 2 \cdot d(gate) \approx 0.2ns$.
- \implies Within a clock period we can only add 5-bit numbers...
- Question: How are > 100 bits added in one clock cycle?

- p.12

Carry bits

 DEF: The **carry bits** associated with an addition $\langle \vec{A} \rangle + \langle \vec{B} \rangle + C[0]$ are the signals $C[n : 0]$ in an $RCA(n)$.



- p.13

remark 1: redundant & non-redundant representations

Functionality of an adder:

$$\langle A[n-1 : 0] \rangle + \langle B[n-1 : 0] \rangle + C[0] = 2^n \cdot C[n] + \langle S[n-1 : 0] \rangle.$$

- Let $x = \langle \vec{A} \rangle + \langle \vec{B} \rangle + C[0]$.
- x admits two representations (left-hand side, right-hand side)
- $C[n] \cdot S[n-1 : 0]$ - binary representation of x .
- Binary representation is **non-redundant**:
 - Every value has a unique representation.
 - $\langle \vec{X} \rangle = \langle \vec{Y} \rangle \iff X = Y$.

- p.14

remark 1 - cont

Functionality of an adder:

$$\langle A[n-1 : 0] \rangle + \langle B[n-1 : 0] \rangle + C[0] = 2^n \cdot C[n] + \langle S[n-1 : 0] \rangle.$$

- $x = \langle A[n-1 : 0] \rangle + \langle B[n-1 : 0] \rangle + C[0]$.
- many possible combinations of $\langle \vec{A} \rangle$, $\langle \vec{B} \rangle$ and $C[0]$. For example: $8 = 4 + 3 + 1$, and also $8 = 5 + 3 + 0$.
- \rightarrow **redundant representation**.
- in redundant representation:

$$X \neq Y \not\iff \text{value}(X) \neq \text{value}(Y).$$
- \Rightarrow in redundant representation: comparison is complicated.
- **ADDER**(n) - translates a redundant representation to a non-redundant binary representation.

- p.15

remark 2: cones

The correctness proof of $RCA(n)$ implies that, for every $0 \leq i \leq n-1$,

$$\langle A[i : 0] \rangle + \langle B[i : 0] \rangle + C[0] = 2^{i+1} \cdot C[i+1] + \langle S[i : 0] \rangle.$$

This equality means that:

$$\text{cone}(C[i+1]), \text{cone}(S[i : 0]) \subseteq A[i : 0] \cup B[i : 0] \cup C[0].$$

Question: Prove that

$$\text{cone}(S[i]), \text{cone}(C[i+1]) = A[i : 0] \cup B[i : 0] \cup C[0].$$

- p.16

remark 3

$$\langle A[i : 0] \rangle + \langle B[i : 0] \rangle + C[0] = 2^{i+1} \cdot C[i+1] + \langle S[i : 0] \rangle.$$

\implies for every $0 \leq i \leq n-1$,

$$\langle S[i : 0] \rangle = \text{mod}(\langle A[i : 0] \rangle + \langle B[i : 0] \rangle + C[0], 2^{i+1}).$$

- p.17

remark 4: reductions sum-bits \longleftrightarrow carry-bits

The correctness of $RCA(n)$ implies that, for every $0 \leq i \leq n-1$,

$$S[i] = \text{XOR}(A[i], B[i], C[i]).$$

\implies for every $0 \leq i \leq n-1$,

$$C[i] = \text{XOR}(A[i], B[i], S[i]).$$

\implies constant-time linear-cost reductions:

$$S[n-1 : 0] \mapsto C[n-1 : 0]$$

$$C[n-1 : 0] \mapsto S[n-1 : 0]$$

\implies if *Circuit* computes $C[n-1 : 0]$ with $O(n)$ cost and $(\log n)$ delay, then we know how to add with same asymptotic cost & delay.

- p.18

Chapter 7: Fast Addition: parallel prefix computation

Computer Structure - Spring 2004

©Dr. Guy Even

Tel-Aviv Univ.

- p.40

Goals

- Design an adder with $O(\log n)$ delay and $O(n)$ cost.
- Learn some interesting methods along the way...

- p.41

reminder: reduction sum-bits \mapsto carry-bits

The correctness of $RCA(n)$ implies that, for every $0 \leq i \leq n - 1$,

$$S[i] = \text{xor}(A[i], B[i], C[i]).$$

\implies constant-time linear-cost reduction:

$$S[n - 1 : 0] \mapsto C[n - 1 : 0]$$

\implies if **Circuit** computes $C[n - 1 : 0]$ with $O(n)$ cost and $O(\log n)$ delay, then we know how to add asymptotically optimally.

- p.42

Computing the carry bits - preliminary

Functionality of Full-Adder (i th FA in $RCA(n)$):

$$C[i + 1] = \begin{cases} 0 & \text{if } A[i] + B[i] + C[i] \leq 1 \\ 1 & \text{if } A[i] + B[i] + C[i] \geq 2. \end{cases}$$

Claim:

$$A[i] + B[i] = 0 \implies C[i + 1] = 0$$

$$A[i] + B[i] = 2 \implies C[i + 1] = 1$$

$$A[i] + B[i] = 1 \implies C[i + 1] = C[i]$$

\implies

- if $A[i] + B[i] \in \{0, 2\}$, then easy to compute $C[i + 1]$.
- if $A[i] + B[i] = 1$, then "ripple effect" of carry.

- p.43

definition of $\sigma[n - 1 : -1]$

DEF: for $i = -1, 0, \dots, n - 1$

$$\sigma[i] \triangleq \begin{cases} 2 \cdot C[0] & \text{if } i = -1 \\ A[i] + B[i] & \text{if } i \in [0, n - 1]. \end{cases}$$

Note that $\sigma[i] \in \{0, 1, 2\}$.

Claim: for every $-1 \leq i \leq n - 1$,

$$C[i + 1] = 1 \iff \exists j \leq i : \sigma[i : j] = 1^{i-j} \cdot 2.$$

- p.44

example with $\sigma[n - 1 : -1]$

$$\sigma[i] \triangleq \begin{cases} 2 \cdot C[0] & \text{if } i = -1 \\ A[i] + B[i] & \text{if } i \in [0, n - 1]. \end{cases}$$

Claim: for every $-1 \leq i \leq n - 1$,

$$C[i + 1] = 1 \iff \exists j \leq i : \sigma[i : j] = 1^{i-j} \cdot 2.$$

Example: $A[3 : 0] = 0110, B[3 : 0] = 0011, C[0] = 0$.

position	4	3	2	1	0	-1
A		0	1	1	0	
B		0	0	1	1	
S		1	0	0	1	
C	0	1	1	0	0	
σ		0	1	2	1	0

- p.45

Proof: $\sigma[i : j] = 1^{i-j} \cdot 2 \Rightarrow C[i + 1] = 1$

- By induction on $i - j$.
- Basis $i - j = 0$: in this case $\sigma[i] = 2$.
 - If $i = -1$, then $C[0] = 1$.
 - If $i \geq 0$, then $A[i] + B[i] = 2$. Hence $C[i + 1] = 1$.
- Ind. Step: note that $\sigma[i - 1 : j] = 1^{i-j-1} \cdot 2$.
- Ind. Hyp. $\Rightarrow C[i] = 1$.
- Since $\sigma[i] = 1$, we conclude that

$$\underbrace{A[i] + B[i] + C[i]}_{\sigma[i]=1} = 2.$$

- Hence, $C[i + 1] = 1$.

- p.46

Proof: $C[i + 1] = 1 \Rightarrow \exists j \leq i : \sigma[i : j] = 1^{i-j} \cdot 2$

- By induction on i .
- Basis $i = -1$: in this case $C[0] = 1$, hence $\sigma[-1] = 2$. Set $j = i$.
- Ind. Step: Assume $C[i + 1] = 1$. Hence,

$$\underbrace{A[i] + B[i]}_{\sigma[i]} + C[i] \geq 2.$$

- $\sigma[i] = 0$: contradiction.
- $\sigma[i] = 2$: set $j = i$.
- $\sigma[i] = 1$: $\Rightarrow C[i] = 1$.

$$C[i] = 1 \xrightarrow{\text{Ind. Hyp.}} \exists j \leq i : \sigma[i - 1 : j] = 1^{i-j-1} \cdot 2$$

$$\xrightarrow{\sigma[i]=1} \exists j \leq i : \sigma[i : j] = 1^{i-j} \cdot 2.$$

- p.47

Corollary: method for computing $C[i + 1]$

$$C[i + 1] = 1 \iff \exists j \leq i : \sigma[i : j] = 1^{i-j} \cdot 2.$$

Corollary:

$$C[i + 1] = \text{OR}((\sigma[i : -1] == 1^{i+1} \cdot 2),$$

$$(\sigma[i : 0] == 1^i \cdot 2),$$

$$(\sigma[i : 1] == 1^{i-1} \cdot 2),$$

$$\vdots$$

$$(\sigma[i : i - 1] == 1 \cdot 2),$$


$$(\sigma[i] == 2)$$

$$)$$

- p.48

Carry-Lookahead Generator
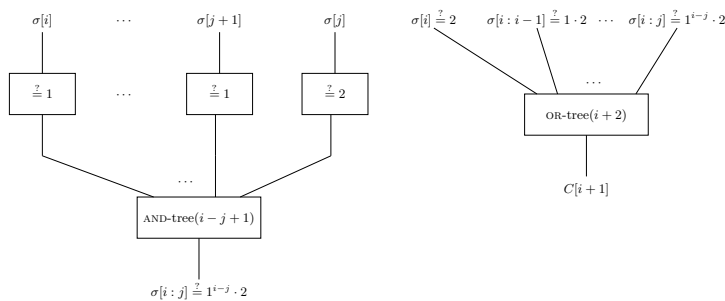
$$C[i + 1] = 1 \iff \exists j \leq i : \sigma[i : j] = 1^{i-j} \cdot 2.$$



- p.49

Carry-Lookahead Generator: cost & delay

- constant cost & depth comparison gates for deciding if :
 - $\sigma[i] = 1$
 - $\sigma[i] = 2$
- Use a row of comparison gates for $\sigma[i : j]$.
- Feed outputs of comparison gates to $\text{AND-tree}(i - j + 1)$.
- Cost of test $\sigma[i : j] = 1^{i-j} \cdot 2$

$$c(\text{AND-tree}(i - j + 1)) + (i - j + 1) \cdot c(\text{comparison}) = \Theta(i - j).$$

- Delay of test $\sigma[i : j] = 1^{i-j} \cdot 2$

$$d(\text{comparison}) + (\text{AND-tree}(i + j + 1)) = \Theta(\log(i - j)).$$

- p.50

Carry-Lookahead Generator: cost & delay - cont.

- Test if $\sigma[i : j] = 1^{i-j} \cdot 2$ for $j = -1, 0, \dots, i$.
- Cost of computing $C[i + 1]$:

$$\sum_{j=-1}^i c(\text{testing if } \sigma[i : j] = 1^{i-j} \cdot 2) = \sum_{j=-1}^i \Theta(i - j) = \Theta(i^2).$$

- Delay of computing $C[i + 1]$:

$$\max_{j=-1 \dots i} \Theta(\log(i - j)) = \Theta(\log i).$$

- \Rightarrow cost of computing $C[n : 1] : \sum_{i=0}^{n-1} \Theta(i^2) = \Theta(n^3)$.
- ...usually applied only to short blocks (e.g. 4 bits)

- p.51

Carry-Lookahead Adder: typical description

SWITCHING EXPRESSIONS

• INTERMEDIATE CARRIES:

$$c_{i+1} = g_i + p_i \cdot c_i$$

BY SUBSTITUTION,

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 c_1$$

$$= g_1 + p_1 g_0 + p_1 p_0 c_0$$


$$c_3 = g_2 + p_2 c_2$$

$$= g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$$

$$c_4 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c_0$$


from: Introduction to Digital Systems, M.D. Ercegovac, T. Lang, and J.H. Moreno, Wiley and Sons, 1998. - p.52

 Carry-Lookahead Adder: typical description



from: Introduction to Digital Systems, M.D. Ercegovac, T. Lang, and J.H. Moreno, Wiley and Sons, 1998. - p.53

 Carry-Lookahead Adder: typical description



from: Introduction to Digital Systems, M.D. Ercegovac, T. Lang, and J.H. Moreno, Wiley and Sons, 1998. - p.54

Two-level Carry-Lookahead Adder

 


Figure 10.7: 32-BIT CARRY-LOOKAHEAD ADDER USING CLA-4 AND CLG-4 MODULES.

from: Introduction to Digital Systems, M.D. Ercegovac, T. Lang, and J.H. Moreno, Wiley and Sons, 1998. - p.55

Definition of $*$: $\{0, 1, 2\} \times \{0, 1, 2\} \rightarrow \{0, 1, 2\}$

*	0	1	2
0	0	0	0
1	0	1	2
2	2	2	2

Remark: for every $a \in \{0, 1, 2\}$:

$$0 * a = 0$$

$$1 * a = a$$

$$2 * a = 2.$$

Claim: (homework) $*$ is an associative function. Namely,

$$\forall a, b, c \in \{0, 1, 2\} : (a * b) * c = a * (b * c).$$

Question: Is $*$ commutative?

- p.56

$*$ -products

For $j \geq i$:

$$\pi[j : i] \triangleq \sigma[j] * \dots * \sigma[i].$$

Associativity of $*$ implies that for every $i \leq j < k$:

$$\pi[k : i] = \pi[k : j + 1] * \pi[j : i].$$

- p.57

A stronger claim

Claim: For every $-1 \leq i \leq n-1$,

$$C[i+1] = 1 \iff \pi[i : -1] = 2.$$

Corollary: Can compute $C[i+1]$ using a $*$ -tree($i+2$).

■ \Rightarrow

$$\begin{aligned} c(\text{compute } C[i+1]) &= O(i) \\ d(\text{compute } C[i+1]) &= O(\log i). \end{aligned}$$

■ \Rightarrow

$$\begin{aligned} c(\text{compute } C[n : 1]) &= \sum_{i=1}^n O(i) = O(n^2) \\ d(\text{compute } C[n : 1]) &= O(\log n). \end{aligned}$$

explains carry-lookahead generator... still too expensive!

- p.58

Proof: $C[i+1] = 1 \iff \pi[i : -1] = 2$

From previous claim, it suffices to prove that

$$\exists j \leq i : \sigma[i : j] = 1^{i-j} \cdot 2 \iff \pi[i : -1] = 2.$$

- p.59

Proof: $\sigma[i : j] = 1^{i-j} \cdot 2 \Rightarrow \pi[i : -1] = 2$

■ Assume that $\sigma[i : j] = 1^{i-j} \cdot 2$.

■ \Rightarrow

$$\pi[i : j] = 2.$$

■ If $j = -1$ we are done.

■ Otherwise,

$$\begin{aligned} \pi[i : -1] &= \underbrace{\pi[i : j]}_{=2} * \pi[j-1 : -1] \\ &= 2. \end{aligned}$$

- p.60

Proof: $\pi[i : -1] = 2 \Rightarrow \exists j \leq i : \sigma[i : j] = 1^{i-j} \cdot 2$

■ Assume that $\pi[i : -1] = 2$.

■ If, for every $\ell \leq i$, $\sigma[\ell] \neq 2$, then $\pi[i : -1] \neq 2$, a contradiction. Hence

$$\{\ell \in [-1, i] : \sigma[\ell] = 2\} \neq \emptyset.$$

■ Let

$$j \triangleq \max \{\ell \in [-1, i] : \sigma[\ell] = 2\}.$$

■ $\pi[j : -1] = 2$ (since $2 * a = 2$).

■ We claim that $\sigma[\ell] = 1$, for every $j < \ell \leq i$.

- p.61

Proof: $\pi[i : -1] = 2 \Rightarrow \exists j \leq i : \sigma[i : j] = 1^{i-j} \cdot 2$

Let

$$j \triangleq \max \{\ell \in [-1, i] : \sigma[\ell] = 2\}.$$

We claim that $\sigma[\ell] = 1$, for every $j < \ell \leq i$.

■ max. of $j \Rightarrow$ for every $j < \ell \leq i$: $\sigma[\ell] \neq 2$.

■ if $\sigma[\ell] = 0$, for $j < \ell \leq i$, then $\pi[i : \ell] = 0$.

\Rightarrow

$$\pi[i : -1] = \pi[i : \ell] * \pi[\ell-1 : -1] = 0,$$

a contradiction.

■ since $\sigma[i : j+1] = 1^{i-j}$, we conclude that $\sigma[i : j] = 1^{i-j} \cdot 2$, QED.

- p.62

Prefix Computation Problem

DEF: Let Σ denote a finite alphabet. Let $\text{OP} : \Sigma^2 \rightarrow \Sigma$ denote an associative function. A **prefix computation** over Σ with respect to OP is defined as follows.

Input $x[n-1 : 0] \in \Sigma^n$.

Output: $y[n-1 : 0] \in \Sigma^n$ defined recursively as follows:

$$\begin{aligned} y[0] &\leftarrow x[0] \\ y[i+1] &= \text{OP}(x[i+1], y[i]). \end{aligned}$$

Note that $y[i]$ can be also expressed simply by

$$y_i = \text{OP}_{i+1}(x[i], x[i-1], \dots, x[0]).$$

- p.63

Reduction: $C[n : 1] \mapsto$ Prefix Computation Prob.

The Claim

$$C[i + 1] = 1 \iff \pi[i : -1] = 2$$

implies a reduction of the problem of computing $C[n : 1]$ to a Prefix Computation Problem:

- $\Sigma = \{0, 1, 2\}$
- $OP = *$
- input: $\sigma[-1 : n]$
- output: $y[i] = \pi[i : -1]$.

- p.64

Prefix Computation Problem - example

- $\Sigma = \{0, 1\}$
- $OP = OR$

\implies PPC-OR(n) used to design a Unary Priority Encoder
U-PENC(n).

- p.65

Parallel Prefix Circuit

DEF: A **Parallel Prefix Circuit**, PPC-OP(n), is a combinational circuit that computes a prefix computation. Namely, given input $x[n - 1 : 0] \in \Sigma^n$, it outputs $y[n - 1 : 0] \in \Sigma^n$, where

$$y_i = OP_{i+1}(x[i], x[i - 1], \dots, x[0]).$$

- representation of values in Σ - not addressed.
- assume: some fixed representation is used.
- OP-gate: given representations of $a, b \in \Sigma$, outputs a representation of $OP(a, b)$.

- p.66

PPC-OP(n) - questions

Question: Design a PPC-OP(n) circuit with linear delay and cost.

Question: Design a PPC-OP(n) circuit with logarithmic delay and quadratic cost.

Question: Assume that a design $C(n)$ is a PPC-OP(n). This means that it is comprised only of OP-gates and works correctly for every alphabet Σ and associative function $OP : \Sigma^2 \rightarrow \Sigma$. Can you prove a lower bound on its cost and delay?


- p.67

PPC-OP - implementation

- A recursive design.
- We already saw a divide-and-conquer design for PPC-OR(n) with cost $\Theta(n \cdot \log n)$.
- Aim for $O(n)$ cost.
- "odd-even" divide-and-conquer (as opposed to left/right side divide-and-conquer).
- basis $n = 2$: an OP-gate.
- recursion step...

- p.68

PPC-OP(n) - recursion step

 

- p.69

PPC-OP(n) - correctness


- By induction. Basis: holds trivially for $n = 2$. We now prove the induction step.
- $x'[n/2 - 1 : 0], y'[n/2 - 1]$ - inputs/outputs of PPC-OP($n/2$).
- $x'[i] \leftarrow \text{OP}(x[2i + 1], x[2i])$.
- Induction hypothesis:

$$y'[i] = \text{OP}_{i+1}(x'[i], \dots, x'[0])$$

$$= \text{OP}_{2i+2}(x[2i + 1], \dots, x[0]).$$
- $y[2i + 1] \leftarrow y'[i] \Rightarrow$ odd indexed outputs $y[1], y[3], \dots, y[n - 1]$ are correct.
- $y[2i] \leftarrow \text{OP}(x[2i], y'[i - 1]) \Rightarrow y[2i] = \text{OP}(x[2i], y[2i - 1])$.
- \Rightarrow even indexed outputs are also correct. QED

- p.70

PPC-OP(n) - delay analysis ($n = 2^k$)

 


$$d(\text{PPC-OP}(n)) = \begin{cases} d(\text{OP-gate}) & \text{if } n = 2 \\ d(\text{PPC-OP}(n/2)) + 2 \cdot d(\text{OP-gate}) & \text{otherwise.} \end{cases}$$

It follows that

$$d(\text{PPC-OP}(n)) = (2 \log n - 1) \cdot d(\text{OP-gate}).$$

- p.71

PPC-OP(n) - cost analysis ($n = 2^k$)

 

$$c(\text{PPC-OP}(n)) = \begin{cases} c(\text{OP-gate}) & \text{if } n = 2 \\ c(\text{PPC-OP}(n/2)) + (n - 1) \cdot c(\text{OP-gate}) & \text{otherwise.} \end{cases}$$

It follows that

$$\begin{aligned} c(\text{PPC-OP}(n)) &= \sum_{i=2}^k (2^i - 1) \cdot c(\text{OP-gate}) + c(\text{OP-gate}) \\ &= (2n - 4 - (k - 1) + 1) \cdot c(\text{OP-gate}) \\ &= (2n - \log n - 2) \cdot c(\text{OP-gate}). \end{aligned}$$

- p.72

PPC-OP(n) - corollary

Corollary: If the delay and cost of an OP-gate is constant, then

$$d(\text{PPC-OP}(n)) = \Theta(\log n)$$

$$c(\text{PPC-OP}(n)) = \Theta(n).$$


\Rightarrow

- $\Sigma = \{0, 1\}$ & OP = OR
 \Rightarrow asymptotically optimal U-PENC(n).
- $\Sigma = \{0, 1, 2\}$ & OP = *
 \Rightarrow compute carry-bits $C[n : 1]$ with $O(n)$ cost and $O(\log n)$ delay.

- p.73

PPC-OP(n) - fanout

 - Insert a buffer in every branching point of the PPC-OP(n) design.
- \Rightarrow constant fanout.
- Question:** What is the maximum fanout in the PPC-OP(n) design. Analyze the effect of inserting buffers to the cost and delay of PPC-OP(n).



- p.74

putting it all together

Compute $\sigma[n - 1 : -1]$: Cost & delay are constant per $\sigma[i]$.
 \Rightarrow total cost is $O(n)$ & the total delay is $O(1)$.

PPC-* (n): Compute product $\pi[i : -1]$ from $\sigma[i : -1]$, for every $i \in [n - 1 : 0]$.
The cost $O(n)$ and delay $O(\log n)$.

Extraction of $C[n : 1]$: Recall $C[i + 1] = 1$ iff $\pi[i : -1] = 2$. Compare each $\pi[i : -1]$ with 2. The result of this comparison equals $C[i + 1]$.

The cost and delay is constant per carry-bit $C[i + 1]$. Total cost of this step is $O(n)$ and the delay is $O(1)$.

Computation of sum-bits: The sum bits are computed by

$$S[i] = \text{XOR}_3(A[i], B[i], C[i]).$$

Cost of this step is $O(n)$ and the delay is $O(1)$.

- p.75

Fast Addition

By combining the cost and delay of each stage we obtain the following result.

Theorem: The adder based on parallel prefix computation is asymptotically optimal; its cost is linear and its delay is logarithmic.

- p.76

Summary

- Presented an adder with asymptotically optimal cost and delay.
- Design based on two reductions:
 - reduction of the task of computing the sum-bits to the task of computing the carry bits.
 - reduction of the task of computing the carry bits to a prefix computation problem.
- A prefix computation problem is the problem of computing $\text{OP}_i(x[i-1:0])$, for $0 \leq i \leq n-1$, where OP is an associative operation.
- $\text{PPC-OP}(n)$ - a linear cost logarithmic delay circuit for the prefix computation problem.
- Can use $\text{PPC-OP}(n)$ for asymptotically optimal $\text{U-PENC}(n)$.

- p.77