

מבנה מחשבים

תרגול מספר 5


Brute force decoder(n)

- **Input:** A string $\{0,1\}^n$.
- **Output:** A string $\{0,1\}^{2^n}$.
- **Functionality:** For every string s , returns 1 in the bit which is the binary representation of s .
- **Implementation:**
 - Construct a device with n inputs and 1 output, that returns 1 when its input is the number k .
 - The device is implemented using up to n NOT gates, and one AND gate of fan-in n .


Brute force decoder(n) (cont.)

- **Implementation (cont.):**
 - For every output bit k , connect the device that implements k .
- **Correctness:** Trivial, it is the implementation of the required boolean function.
- **Size:** $O(n2^n)$.
- **Delay:** $O(1)$, if we use and gates with non-restricted fan-in. If we need to implement with and gates with fan-in = 2, requires $O(\log n)$.


Decoder'(n)

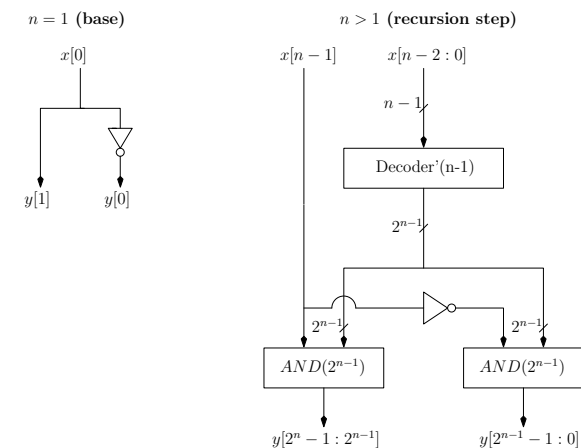

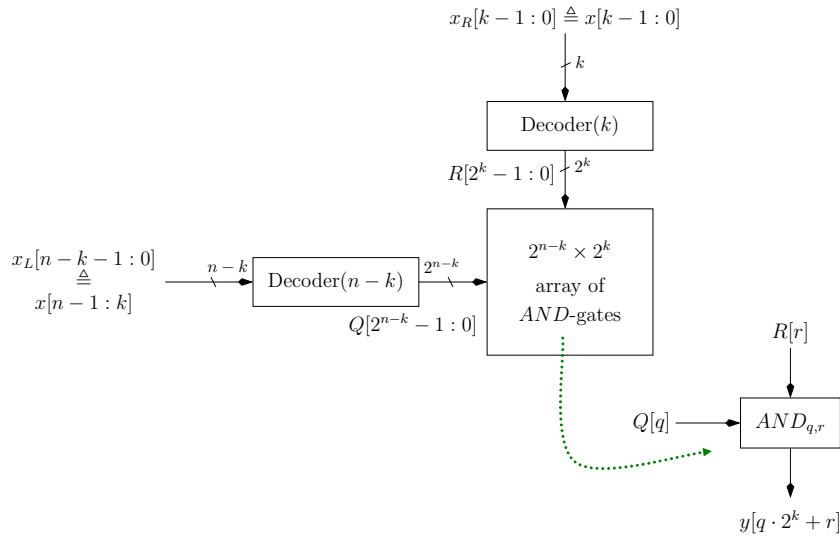Decoder(n) design shown and proven in class:



for $k = n-1$:

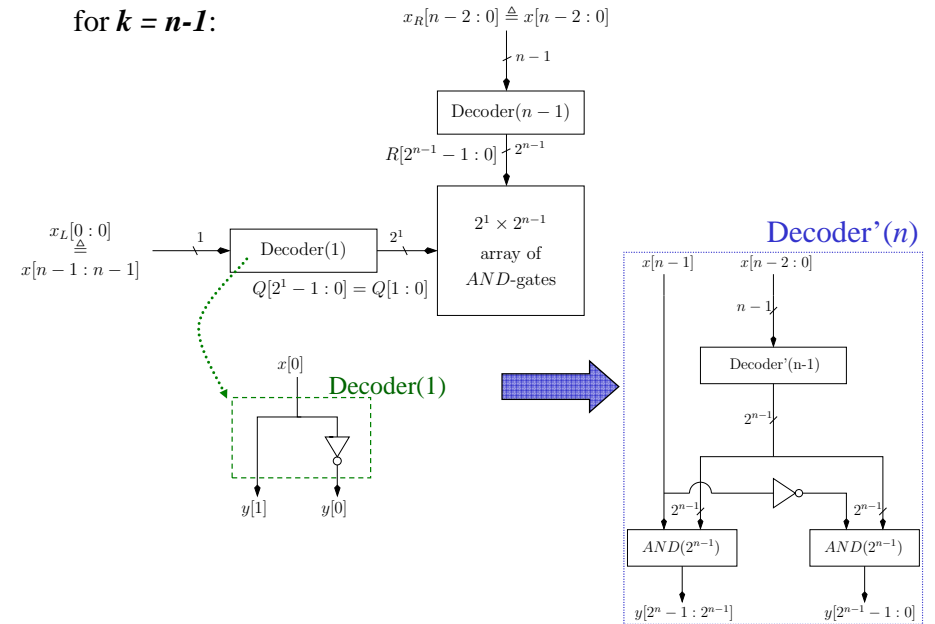

Decoder'(n) is a private case of Decoder(n) design. ($k = n-1$ or $k = 1$)

Decoder'(n) is a correct implementation of a decoder.

Cost analysis:

$$c(n) = \begin{cases} c(INV) & \text{if } n = 1 \\ c(n-1) + 2 \cdot 2^{n-1} \cdot c(AND) + c(INV) & \text{otherwise} \end{cases}$$

Solving the recurrence:

$$\begin{aligned} n > 1: \quad c(n) &= c(n-1) + 2^n \cdot c(AND) + c(INV) \\ &= c(1) + (2^n + 2^{n-1} + \dots + 2^2) \cdot c(AND) + (n-1) \cdot c(INV) \\ &= n \cdot c(INV) + 2^2 \frac{2^{n-1} - 1}{2 - 1} \cdot c(AND) \\ &= n \cdot c(INV) + (2^{n+1} - 4) \cdot c(AND) \\ &= \Theta(2^n) \end{aligned}$$

asymptotics

Delay analysis:


$$d(n) = \begin{cases} d(INV) & \text{if } n = 1 \\ \max\{d(INV), d(n-1)\} + d(AND) & \text{otherwise} \end{cases}$$

Solving the recurrence:

$$\begin{aligned} n > 1: \quad d(n) &= \max\{d(INV), d(n-1)\} + d(AND) \\ &= d(n-1) + d(AND) \\ &= d(1) + (n-1)d(AND) \\ &= d(INV) + (n-1)d(AND) \\ &= \Theta(n) \end{aligned}$$

Linear Delay!!!

Decoder(n) for k = n/2

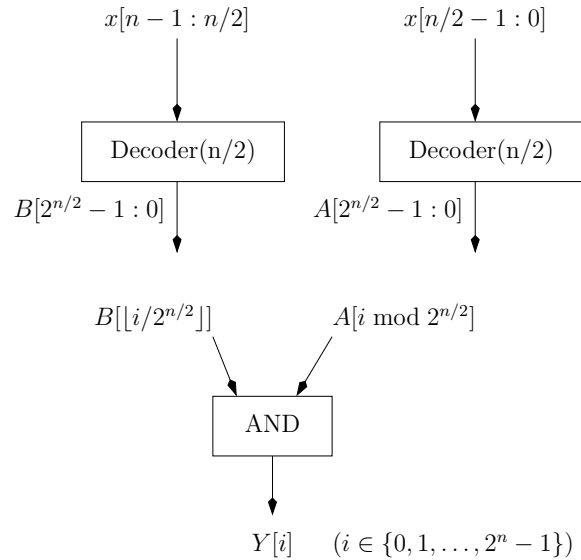

Consider the top two recursion steps:

each AND-gate in the “AND-gates array” of the second recursion step, i.e. Decoder(n/2), feeds $2^{n/2}$ AND-gates in the “AND-gates array” of the primary recursion step, i.e. Decoder(n).

➡ Maximum fanout of a net = $2^{\frac{n}{2}}$

$$c(n) = \begin{cases} c(INV) & \text{if } n = 1 \\ 2 \cdot c(\frac{n}{2}) + 2^n \cdot c(AND) & \text{otherwise} \end{cases} = \Theta(2^n)$$

$$d(n) = \begin{cases} d(INV) & \text{if } n = 1 \\ d(\frac{n}{2}) + d(AND) & \text{otherwise} \end{cases} = \Theta(\log n)$$


Cost

n \ Design	Decoder(n) k=n/2	Decoder'(n)
1	1	1
2	10	10
4	52	60
8	616	1024
16	132304	262152

Delay

n \ Design	Decoder(n) k=n/2	Decoder'(n)
1	1	1
2	3	3
4	5	7
8	7	15
16	9	31

Buffers

 

fanout ≤ 2

A balanced tree structure minimizes the delay and cost.

The tree is a binary tree due to fan-out limitations.

Notice: * The leaves of the tree feed the gate outputs.

* The root of the tree is fed by the gate input.

* The first branching is free \rightarrow no need for a “root” gate.




$$d(n) = (\lceil \log_2 n \rceil - 1) \cdot d(1-buffer)$$

$$c(n) = (n - 2) \cdot c(1-buffer)$$

Fanout limitation effect on design

$$\text{fanout} \leq 2$$

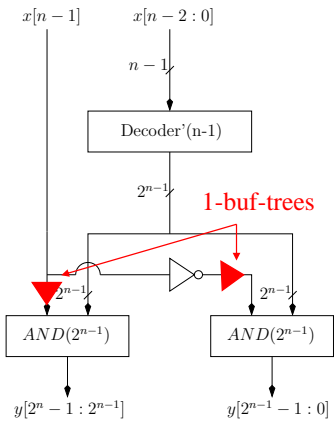


Cost analysis:

$$n = 1:$$

$$c(1) = c(INV)$$

$$n > 1:$$
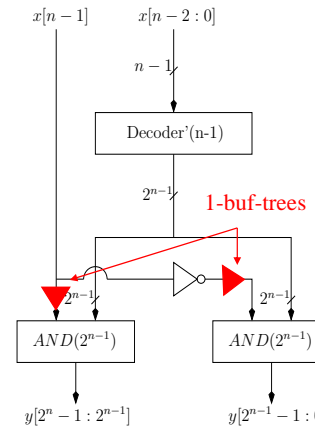
$$\begin{aligned} c(n) &= c(n-1) + 2^n \cdot c(AND) + c(INV) \\ &\quad + 2 \cdot c(1-buf-tree(2^{n-1})) + c(1-buf) \\ &= c(n-1) + 2^n \cdot c(AND) + c(INV) \\ &\quad + (2^n - 3) \cdot c(1-buf) \end{aligned}$$




Delay analysis:

$$n = 1:$$

$$d(1) = d(INV)$$

$$n > 1:$$
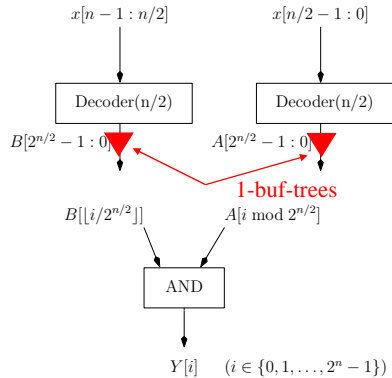
$$\begin{aligned} d(n) &= \max \left\{ \begin{aligned} &d(INV) + d(1-buf-tree(2^{n-1})) \\ &d(1-buf) + d(1-buf-tree(2^{n-1})) \end{aligned} \right\} \\ &\quad + d(AND) \\ &= \max \left\{ \begin{aligned} &d(INV) + (n-1) \cdot d(1-buf) \\ &n \cdot d(1-buf) \end{aligned} \right\} \\ &\quad + d(AND) \end{aligned}$$



Cost analysis:

$$n = 1: c(1) = c(INV)$$

$$\begin{aligned} n > 1: c(n) &= 2 \cdot c\left(\frac{n}{2}\right) + 2^n \cdot c(AND) \\ &\quad + 2 \cdot 2^{\frac{n}{2}} \cdot c(1-buf-tree(2^{\frac{n}{2}})) \\ &= 2 \cdot c\left(\frac{n}{2}\right) + 2^n \cdot c(AND) \\ &\quad + 2^{\frac{n}{2}+1} \cdot (2^{\frac{n}{2}} - 2) \cdot c(1-buf) \end{aligned}$$

Delay analysis:

$$n = 1: d(1) = d(INV)$$

$$n > 1: d(n) = d\left(\frac{n}{2}\right) + d(1-buf-tree(2^{\frac{n}{2}})) + d(AND)$$

$$= d\left(\frac{n}{2}\right) + \left(\frac{n}{2} - 1\right) d(1-buf) + d(AND)$$

Cost Decoder(n):

n=1:	1
n=2:	10
n=4:	52
n=8:	616
n=16:	132304
n=32:	8.5902e+009
n=64:	3.68935e+019
n=128:	6.80565e+038

Cost Decoder(n), Fanout<=2:

n=1:	1
n=2:	10
n=4:	68
n=8:	1096
n=16:	263312
n=32:	1.71801e+010
n=64:	7.3787e+019
n=128:	1.36113e+039

Cost Decoder'(n):

n=1:	1
n=2:	10
n=4:	60
n=8:	1024
n=16:	262152
n=32:	1.71799e+010
n=64:	7.3787e+019
n=128:	1.36113e+039

Cost Decoder'(n), Fanout<=2:

n=1:	1
n=2:	11
n=4:	79
n=8:	1511
n=16:	393175
n=32:	2.57698e+010
n=64:	1.1068e+020
n=128:	2.04169e+039

Delay Decoder(n):

n=1: 1
n=2: 3
n=4: 5
n=8: 7
n=16: 9
n=32: 11
n=64: 13
n=128: 15

Delay Decoder(n), Fanout<=2:

n=1: 1
n=2: 3
n=4: 6
n=8: 11
n=16: 20
n=32: 37
n=64: 70
n=128: 135

Delay Decoder'(n):

n=1: 1
n=2: 3
n=4: 7
n=8: 15
n=16: 31
n=32: 63
n=64: 127
n=128: 255

Delay Decoder'(n), Fanout<=2:

n=1: 1
n=2: 4
n=4: 8
n=8: 16
n=16: 32
n=32: 64
n=64: 128
n=128: 256

Brute force encoder(n)

- **Input:** A string $\{0,1\}^{2^n}$.
- **Output:** A string $\{0,1\}^n$.
- **Functionality:** For every string s with weight 1, returns the binary representation of s .
- **Implementation:**
 - Connect bits $1,3,\dots,2^n-1$ with an OR gate of size 2^{n-1} , this gate sets bit 1 of the output.
 - Connect bits $2,3,6,7,\dots$ with an OR gate of size 2^{n-1} , this gate sets bit 2 of the output.
 - And so on for each power of 2.

Brute force encoder(n) (cont.)

- **Correctness:** Trivial, bit j of the output is 1 if and only if any of the inputs in the set S_j is 1. The set S_j is the set of all input bits whose index is such that 2^j is 1 in its binary representation.
- **Size:** $O(n2^n)$.
- **Delay:** $O(1)$, if we use OR gates with non-restricted fan-in. If we need to implement with and gates with fan-in = 2, requires $O(n)$.