

## Adders, PPC



### Lower Bounds – Adder( $n$ )


$$Cost(Adder(n)) = \Omega(n)$$

$$Delay(Adder(n)) = \Omega(\log n)$$

תורה למחוש

### On the moon...

- RCA

 


- Linear Delay
- Linear Cost



2

### First shot


- Split the numbers to LSB and MSB

 


- What is the problem with this solution?

4

## Second Shot :Dancing on both weddings

 


## White box

 

6

## Conditional Sum Adder – CSA( $n$ )

 

7

## Delay & Cost

### • Delay

$$D(n) = D(n/2) + T_{MUX}$$


$$\Rightarrow D(n) = T_{MUX} \cdot \log n$$

8

בינהיים הכל בודר..

- Cost
  - $\log n$  recursive stages
  - In each stage we triple the number of FA's
  - How many full adders?
 
$$\begin{aligned}
 & 3^{\log n} = n^{\log 3} = n^{1.5} \\
 \bullet \text{ How many MUX's?} \\
 & n/2 + (3/2) \cdot (n/2) + (3/2)^2 \cdot (n/2) + \dots = \\
 & = (n/2) \cdot [1 + (3/2)^2 + (3/2)^3 + \dots] = \\
 & = n \cdot (3/2)^{\log n} \\
 & = n^{1.58}
 \end{aligned}$$



Assume that  $n = 2^l$  and set  $k = n/2$ ,

$$d(\text{CSA}(n)) = \begin{cases} d(\text{FA}) & \text{if } n=1 \\ d(\text{CSA}(\frac{n}{2})) + \log(\frac{n}{2}) \cdot d(\text{buf}) + d(\text{MUX}) & \text{otherwise} \end{cases}$$

$$c(\text{CSA}(n)) = \begin{cases} c(\text{FA}) & \text{if } n=1 \\ 3 \cdot c(\text{CSA}(\frac{n}{2})) + \Theta(n) \cdot c(\text{buf}) + (\frac{n}{2} + 1) \cdot c(\text{MUX}) & \text{otherwise} \end{cases}$$

## CSA( $n$ ) - Delay and Cost analysis under fan-out limitations



**Question 8.6 (effect of fanout on CSA( $n$ ))** The fanout of the carry-bit  $C[k]$  is  $n/2+1$  if  $k = n/2$ . Suppose that we associate a delay of  $\log_2(f)$  with a fanout  $f$ . How would taking the fanout into account change the delay analysis of a CSA( $n$ )?

Suppose that we associate a cost  $O(f)$  with a fanout  $f$ . How would taking the fanout into account change the cost analysis of a CSA( $n$ )?

9

10

$$\begin{aligned}
 n &= 2^l, \\
 \text{for simplicity: } d(\text{FA}) &= d(\text{MUX}) = d(\text{buf}) = 1
 \end{aligned}$$

$$\begin{aligned}
 d(n) &= d\left(\frac{n}{2}\right) + \log\left(\frac{n}{2}\right) + 1 \\
 &= d\left(\frac{n}{2}\right) + \log(n) - \log(2) + 1 \\
 &= d\left(\frac{n}{2}\right) + \log(n) \\
 &= d(1) + (\log(n) + \log(\frac{n}{2}) + \log(\frac{n}{4}) + \dots + \log(\frac{n}{2^l}) + \dots + \log(\frac{n}{2^l})) \\
 &= 1 + (l + (l-1) + \dots + 1 + 0) \\
 &= \Theta(l^2) \\
 &= \Theta(\log^2(n))
 \end{aligned}$$

12

$$c(n) = 3 \cdot c\left(\frac{n}{2}\right) + \left(\frac{n}{2} + 1\right) \cdot c(MUX) + \Theta(n) \cdot c(buf)$$

$$c(n) = 3 \cdot c\left(\frac{n}{2}\right) + \Theta(n)$$

Master Theorem for recurrences provides:

$$c(n) = \Theta(n^{\log_2 3}) \approx \Theta(n^{1.58})$$

To conclude, in CSA( $n$ ) design:

- No change in cost asymptotics due to fan-out limitations.
- Quadratic increase in delay asymptotics due to fan-out limitations.




13

## The PPC-OP Circuit

**Definition 9.5** A Parallel Prefix Circuit,  $PPC-OP(n)$ , is a combinational circuit that computes a prefix computation. Namely, given input  $x[n-1 : 0] \in \Sigma^n$ , it outputs  $y[n-1 : 0] \in \Sigma^n$ , where

$$y_i = OP_{i+1}(x[i], x[i-1], \dots, x[0]).$$

 

**Corollary 9.7** If the delay and cost of an OP-gate is constant, then

$$\begin{aligned} d(PPC-OP(n)) &= \Theta(\log n) \\ c(PPC-OP(n)) &= \Theta(n). \end{aligned}$$

Copyright by Dr.Guy Even

$y[n-1]$   $y[n-2]$   $y[n-3]$   $y[n-4]$   $y[3]$   $y[2]$   $y[1]$   $y[0]$

14

## PPC-OR



**Definition 6.3** A parallel prefix OR circuit of length  $n$  is a combinational circuit specified as follows.

**Input:**  $x[0 : n - 1]$ .

**Output:**  $y[0 : n - 1]$ .

**Functionality:**

$$y[i] = OR(x[0 : i]).$$

We denote parallel prefix OR circuit of length  $n$  by  $PPC-OR(n)$ .

15

Copyright by Dr.Guy Even

## PPC-OR



**Definition 6.4** A unary priority encoder U-PENC( $n$ ) is a combinational circuit specified as follows.

**Input:**  $x[0 : n - 1]$ .

**Output:**  $y[0 : n - 1]$ .

**Functionality:**

$$y[i] = INV(OR(x[0 : i])).$$

**Example 6.3** Consider the string  $x[0 : 6] = 0110100$ . The output of a  $PPC-OR(7)$  is 0111111. The output of a U-PENC(7) is 1000000.

16

Copyright by Dr.Guy Even

## PPC-OR



A brute force design of a PPC-OR( $n$ ) uses a separate OR-tree for each output bit. The delay of such a design is  $O(\log n)$  and the cost is  $O(n^2)$ . The issue of efficiently combining these trees will be discussed in detail when we discuss parallel prefix computation in the context of fast addition. In the meantime, we present here a (non-optimal) design based on divide-and-conquer.

The method of divide-and-conquer is applicable for designing a PPC-OR( $n$ ). We apply divide-and-conquer in the following recursive design. If  $n = 1$ , then PPC-OR(1) is the trivial design in which  $y[0] \leftarrow x[0]$ . A recursive design of PPC-OR( $n$ ) for  $n > 1$  that is a power of 2 is depicted in Figure 6.1.

 


Figure 6.1: A recursive implementation of PPC-OR( $n$ ).

Copyright by Dr.Guy Even

17

## PPC-OR



**Question 6.1** This question deals with the recursive design of the PPC-OR( $n$ ) circuit depicted in Figure 6.1.

1. Prove the correctness of the design.
2. Extend the design for values of  $n$  that are not powers of 2.
3. Analyze the delay of the design.

 


Figure 6.1: A recursive implementation of PPC-OR( $n$ ).

Copyright by Dr.Guy Even

## Correctness of PPC-OR


 


Figure 6.1: A recursive implementation of PPC-OR( $n$ ).

19

Copyright by Dr.Guy Even

## Correctness of PPC-OR (cont.)

 

### The correctness of the design:

- Note the design is given for  $n = 2^k$ .
- Prove by induction on  $k$ .
- Basis:  $k = 1$ , Trivial (correctness of OR).
- Hypothesis: Assume correct for all  $j < k+1$ .
- Step: Prove for  $k+1$ .
- Observation: If  $y[s] = 1$ , then  $y[t] = 1$  for  $t \geq s$ .

20

## Correctness of PPC-OR (cont.)

Separate into two cases:

If the leading one is on the  $[n/2:n-1]$

→ The leading  $x$  values are 0, and hence  $y[0:n/2-1] = 0$  (as should be).

$y[n/2:n-1]$  are correct by the induction.

If the leading one is on the  $[0:n/2-1]$

→ All the trailing outputs should be 1(observation). So  $y[n/2:n-1] = 1$ .

$y[0:n/2-1]$  are correct by the induction.



21

## Non $2^k$ PPC-OR

- For this case, we use the padding idea.

- We pad the number of bits to be a whole power of 2.

- Question: What should it be padded with?

- Answer: Doesn't matter for the PPC-OR as long as you pad at the end of the input and ignore the relevant bits in the output.

22

## Delay analysis of PPC-OR

- $d(n) = d(n/2) + 1$ .

- →  $d(n) = \log(n)$ .

- For  $n \neq 2k$ , the padding leads to  $d(n) = \lceil \log(n) \rceil$ .



23

## Q1 from Exam 2000a

- Input:  $x[0:n-1]$

- Output  $y[0:n-1]$

- Functionality:

- Let  $s[j] = \sum x[k]$  ( $k=0..j$ )


- Let  $t[j] = \sum s[k]$  ( $k=0..j$ )

- $y[j] = 1$  if and only if  $s[j]$  and  $t[j]$  are even.



24

## First Shot

 

25

## Q1 from Exam 2000a (cont.)

- Note that:

- $s[0] = x[0]$ .
- $s[1] = x[0] + x[1]$ .
- $s[2] = x[0] + x[1] + x[2]$ .
- $s[3] = x[0] + x[1] + x[2] + x[3]$ .
- $t[0] = x[0]$ .
- $t[1] = 2x[0] + x[1]$ .
- $t[2] = 3x[0] + 2x[1] + x[2]$ .
- $t[3] = 4x[0] + 3x[1] + 2x[2] + x[3]$ .

26

## Q1 from Exam 2000a (cont.)

- Note that:

- Parity( $s[0]$ ) =  $\text{XOR}(x[0])$ .
- Parity( $s[1]$ ) =  $\text{XOR}(x[0] + x[1])$ .
- Parity( $s[2]$ ) =  $\text{XOR}(x[0] + x[1] + x[2])$ .
- Parity( $s[3]$ ) =  $\text{XOR}(x[0] + x[1] + x[2] + x[3])$ .
- Parity( $t[0]$ ) =  $\text{XOR}(x[0])$ .
- Parity( $t[1]$ ) =  $\text{XOR}(x[1])$ .
- Parity( $t[2]$ ) =  $\text{XOR}(x[0] + x[2])$ .
- Parity( $t[3]$ ) =  $\text{XOR}(x[1] + x[3])$ .

- $s[0] = x[0]$ .
- $s[1] = x[0] + x[1]$ .
- $s[2] = x[0] + x[1] + x[2]$ .
- $s[3] = x[0] + x[1] + x[2] + x[3]$ .
- $t[0] = x[0]$ .
- $t[1] = 2x[0] + x[1]$ .
- $t[2] = 3x[0] + 2x[1] + x[2]$ .
- $t[3] = 4x[0] + 3x[1] + 2x[2] + x[3]$ .

28

## Q1 from Exam 2000a (cont.)

- $y[2k+1] = 1$  if and only if:

- The XOR of the odd bits is 0 (For  $t[2k+1]$ ).
- The XOR of all bits is 0 (For  $s[2k+1]$ ).

- In order that  $y[2k] = 1$  if and only if:

- The XOR of the even bits is 0 (For  $t[2k]$ ).
- The XOR of all bits is 0 (For  $s[2k]$ ).

- → Conclusion: The XOR of even bits and the XOR of odd bits should be 0.


## Q1 from Exam 2000a (cont.)

- Conclusion2:
  - We need to calculate the PPC-XOR of the odd bits.
  - We need to calculate the PPC-XOR of the even bits.
  - We combine them with NOR gate, for each j.
- Conclusion3: The circuit is composed of 2 PPC-XOR (n/2) and linear number of gates.



29

## Q1 from Exam 2000a (cont.)

 

30

## Q1 from Exam 2000a (cont.)

- Using the optimal Implementation of PPC-OP we will achieve:

$$Cost(n) = O(n)$$

$$Delay(n) = O(\log n)$$



31