

Digital Logic Design: a rigorous approach ©

Chapter 15: Addition

Guy Even Moti Medina

School of Electrical Engineering Tel-Aviv Univ.

May 21, 2020

Book Homepage:

<http://www.eng.tau.ac.il/~guy/Even-Medina>

Definition of a binary adder

Definition

ADDER(n) - a **binary adder** with input length n is a combinational circuit specified as follows.

Input: $A[n-1:0], B[n-1:0] \in \{0,1\}^n$, and $C[0] \in \{0,1\}$.

Output: $S[n-1:0] \in \{0,1\}^n$ and $C[n] \in \{0,1\}$.

Functionality:

$$\langle \vec{S} \rangle + 2^n \cdot C[n] = \langle \vec{A} \rangle + \langle \vec{B} \rangle + C[0]. \quad (1)$$

Addition terminology:

- addends: $\langle \vec{A} \rangle = \sum_{i=1}^{n-1} A[i] \cdot 2^i$, and $\langle \vec{B} \rangle = \sum_{i=1}^{n-1} B[i] \cdot 2^i$
- carry-in bit : $C[0]$
- sum: $\langle \vec{S} \rangle$
- carry-out bit: $C[n]$

binary adder definition (cont)

Definition

$\text{ADDER}(n)$ - a **binary adder** with input length n is a combinational circuit specified as follows.

Input: $A[n-1:0], B[n-1:0] \in \{0,1\}^n$, and $C[0] \in \{0,1\}$.

Output: $S[n-1:0] \in \{0,1\}^n$ and $C[n] \in \{0,1\}$.

Functionality:

$$\langle \vec{S} \rangle + 2^n \cdot C[n] = \langle \vec{A} \rangle + \langle \vec{B} \rangle + C[0]. \quad (2)$$

Claim ($\text{ADDER}(n)$ is well defined)

For every $A[n-1:0], B[n-1:0] \in \{0,1\}^n$, and $C[0] \in \{0,1\}$, there exist $S[n-1:0] \in \{0,1\}^n$ and $C[n] \in \{0,1\}$ such that

$$\langle \vec{S} \rangle + 2^n \cdot C[n] = \langle \vec{A} \rangle + \langle \vec{B} \rangle + C[0]$$

adder(n) well defined

$$0 \leq \langle a \rangle + \langle b \rangle + c[0] \leq 2 \cdot (2^n - 1) + 1 \\ = 2^{n+1} - 1$$

and $S[n-1:0]$, $c[n]$ can represent
all numbers in the range

$$\{0, 1, \dots, 2^{n+1} - 1\}$$



Full Adder

An ADDER(1) is called a **full adder**.

Definition (Full-Adder)

FA - a **Full-Adder** is a combinational circuit with 3 inputs $x, y, z \in \{0, 1\}$ and 2 outputs $c, s \in \{0, 1\}$ that satisfies:

$$2c + s = x + y + z.$$

Terminology: s -**sum output**, c -**carry-out output**.


Claim

(exercise)

$$s = x \oplus y \oplus z,$$

$$c = (x \cdot y) \vee (y \cdot z) \vee (x \cdot z).$$

Ripple Carry Adder RCA(n)

 

- same addition algorithm that we use for adding numbers by hand.
- row of n Full-Adders connected in a chain.
- the weight of every signal is two to the power of its index. (Do not confuse weight here with Hamming weight. Weight means here the value in binary representation.)

$$\langle \vec{a} \rangle \doteq \sum a[i] \cdot 2^i$$


weight of $a[i]$ is 2^i

Recursive definition of $RCA(n)$

(want to prove that $\langle \vec{S} \rangle + 2^n \cdot c[n] = \langle \vec{A} \rangle + \langle \vec{B} \rangle + c[0]$)


Basis: an $RCA(1)$ is simply a Full-Adder.

Reduction Step:

 

Claim

 RCA(n) is a correct implementation of ADDER(n).



correctness of RCA(n)

by ind. on n .

basis: $n=1$ (FA is correct).

hyp: RCA($n-1$) is correct.

step: $\langle A[n-1:0] \rangle + \langle B[n-1:0] \rangle + C[0]$

$$= 2^{n-1} \cdot (A[n-1] + B[n-1]) + \langle A[n-2:0] \rangle + \langle B[n-2:0] \rangle + C[0]$$

$$= 2^{n-1} \cdot (A[n-1] + B[n-1]) + 2^{n-1} \cdot C[n-1] + \langle S[n-2:0] \rangle$$

$$= 2^{n-1} \cdot (A[n-1] + B[n-1] + C[n-1]) + \langle S[n-2:0] \rangle$$

$$= 2^{n-1} \cdot (S[n-1] + 2 \cdot C[n]) + \langle S[n-2:0] \rangle$$

$$= 2^n \cdot C[n] + \langle S[n-1:0] \rangle \quad \square$$

Delay and cost analysis

The cost of an $RCA(n)$ satisfies:

$$c(RCA(n)) = n \cdot c(FA) = \Theta(n).$$

The delay of an $RCA(n)$ satisfies

$$d(RCA(n)) = n \cdot d(FA) = \Theta(n).$$

Clock rates in modern microprocessors correspond to the delay of 15-20 gates (in more aggressive designs, the critical paths are even shorter). Most microprocessors easily add 32-bit numbers within one clock cycle (high-end microprocessors even add 100-bit number in a cycle). Obviously, adders in such microprocessors are not Ripple Carry Adders.


Carry bits

We now define the carry bits associated with the addition

$$\langle A[n-1:0] \rangle + \langle B[n-1:0] \rangle + C[0] = \langle S[n-1:0] \rangle + 2^n \cdot C[n]$$

Definition

 The carry bits $C[n:0]$ are defined as the values of the stable signals $C[n:0]$ in an $RCA(n)$.



This definition is well defined in light of the Simulation Theorem of combinational circuits.

Cone of adder outputs

The correctness proof of $\text{RCA}(n)$ implies that, for every $0 \leq i \leq n - 1$,

$$\langle A[i : 0] \rangle + \langle B[i : 0] \rangle + C[0] = 2^{i+1} \cdot C[i + 1] + \langle S[i : 0] \rangle.$$

Hence, for every $0 \leq i \leq n - 1$:

$$\begin{aligned} C[i + 1] = 1 &\iff \langle A[i : 0] \rangle + \langle B[i : 0] \rangle + C[0] \geq 2^{i+1} \\ &\quad \langle S[i : 0] \rangle = \text{mod}(\langle A[i : 0] \rangle + \langle B[i : 0] \rangle + C[0], 2^{i+1}). \end{aligned}$$

Claim

For each $0 \leq i \leq n - 1$, the cone of Boolean functions corresponding to $C[i + 1]$ and $S[i]$ consists of $2i + 3$ inputs corresponding to $A[i : 0]$, $B[i : 0]$, and $C[0]$.

cone of addition

proof that $c[0] \in \text{cone}(c[n])$

(similar proof shows that all inputs are in the cone of $c[n]$ & $S[n-1]$.)

$$\begin{array}{rcccccc} & & & & 0 & c[0] \\ + & 1 & 1 & \dots & 1 & A \\ & 0 & 0 & \dots & 0 & B \\ \hline 0 & 1 & 1 & \dots & 1 & \\ c[n] & & & & & \end{array}$$

$$\begin{array}{rcccccc} & & & & & 1 \\ + & 1 & 1 & \dots & 1 & \\ & 0 & 0 & \dots & 0 & \\ \hline 1 & 0 & 0 & \dots & 0 & \\ c[n] & & & & & \end{array}$$

Claim

Let A denote a combinational circuit that implements an $\text{ADDER}(n)$. If the fan-in in C is at most 2, then

$$c(A) \geq 2n,$$


$$d(A) \geq \log_2(2n + 1).$$

Compare with the cost and delay of $\text{RCA}(n)$.



$$c(\text{RCA}(n)) = \Theta(n) \quad \checkmark$$

$$d(\text{RCA}(n)) = \Theta(n) \quad ?$$

Conditional Sum Adder - motivation

 


Conditional Sum Adder - motivation

  



Conditional Sum Adder - motivation



Alice,
Let's have some fun!

 


Conditional Sum Adder - motivation

  



Conditional Sum Adder - motivation



Never done that before!
Let's try...

 

Conditional Sum Adder - motivation

  


Conditional Sum Adder - motivation

It's lots of fun!
I'll hold:
 $A[k-1:0]$
 $B[k-1:0]$
 $C[0]$





and I'll hold:
 $A[n-1:k]$
 $B[n-1:k]$

 


Conditional Sum Adder - motivation

  The rules are:
-at the end we must
know the sum.
-it doesn't matter who
has which sum bits.




Conditional Sum Adder - motivation

 
-communication is costly,
and
-our goal is to compute the
sum asap.




Conditional Sum Adder - motivation

 


Conditional Sum Adder - motivation

 

Conditional Sum Adder - motivation

 


Conditional Sum Adder - motivation

 

Conditional Sum Adder - motivation



$c[k]$
 \rightarrow
 m
 $\{0,1\}$

 


*I have an idea:
Her message will be
either zero or one...*


Conditional Sum Adder - motivation



 *So I will compute my
answers for both cases...*




Conditional Sum Adder - motivation

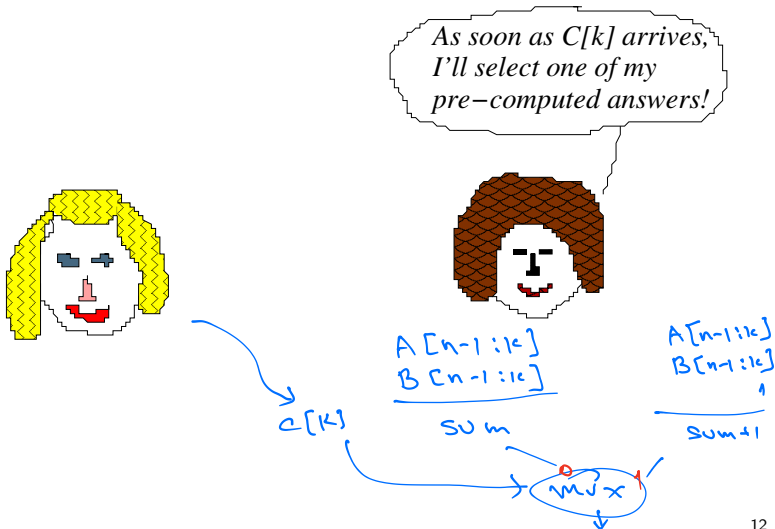


Conditional Sum Adder - motivation



 
Alice,
I have to tell you,
This game is FUN!!!



Conditional Sum Adder - motivation

 

 
It reminds me of this
course I took once...



Conditional Sum Adder $CSA(n)$

basis: A $CSA(1)$ is simply a Full-Adder.

reduction step:

 

Claim

The $CSA(n)$ is a correct $ADDER(n)$ design.

correctness CSA(n)

ind. on n. we show the ind. step:

Alice
 $C[k] \cdot 2^k + \langle S[k-1:0] \rangle = \langle A[k-1:0] \rangle + \langle B[k-1:0] \rangle + C[0]$

Bob
 $2^{n-k} \cdot C[n] + \langle S[n-1:k] \rangle = \langle A[n-1:k] \rangle + \langle B[n-1:k] \rangle + C[k]$

\Rightarrow

$$2^n \cdot C[n] + \langle S[n:0] \rangle + \cancel{C[k] \cdot 2^k} = \langle A[n-1:0] \rangle + \langle B[n-1:0] \rangle + \cancel{C[k] \cdot 2^k} + C[0]$$



Delay analysis

To simplify the analysis we assume that $n = 2^\ell$. To optimize the delay, we use $k = n/2$.

Let $d(\text{FA})$ denote the delay of a Full-Adder. The delay of a $\text{CSA}(n)$ satisfies the following recurrence:

$$d(\text{CSA}(n)) = \begin{cases} d(\text{FA}) & \text{if } n = 1 \\ d(\text{CSA}(n/2)) + d(\text{MUX}) & \text{otherwise.} \end{cases}$$

Hence, the delay of a $\text{CSA}(n)$ is

$$\begin{aligned} d(\text{CSA}(n)) &= \ell \cdot d(\text{MUX}) + d(\text{FA}) \\ &= \Theta(\log n). \end{aligned}$$

Cost analysis.

Let $c(\text{FA})$ denote the cost of a Full-Adder. The cost of a $\text{CSA}(n)$ satisfies the following recurrence:

$$c(\text{CSA}(n)) = \begin{cases} c(\text{FA}) & \text{if } n = 1 \\ 3 \cdot c(\text{CSA}(n/2)) + (n/2 + 1) \cdot c(\text{MUX}) & \text{otherwise.} \end{cases}$$

the solution of this recurrence is $c(\text{CSA}(n)) = \Theta(n^{\log_2 3})$.

- $\log_2 3 \approx 1.58$, so a $\text{CSA}(n)$ is costly.
- but delay is logarithmic!
- the $\text{CSA}(n)$ design uses three half-size adders (easy to use).

$$\begin{aligned} f(n) &= 3 \cdot f\left(\frac{n}{2}\right) + \Theta(n) \\ f(n) &= \Theta(n^{\log_2 3}) \approx \Theta(n^{1.58}) \end{aligned}$$

Definition

COMP-ADDER(n) - a **Compound Adder** with input length n is a combinational circuit specified as follows.

Input: $A[n-1:0], B[n-1:0] \in \{0, 1\}^n$.

Output: $S[n:0], T[n:0] \in \{0, 1\}^{n+1}$.



Functionality:

$$\langle \vec{S} \rangle = \langle \vec{A} \rangle + \langle \vec{B} \rangle + \odot$$

$$\langle \vec{T} \rangle = \langle \vec{A} \rangle + \langle \vec{B} \rangle + 1.$$

Note that a Compound Adder does not have carry-in input. To simplify notation, the carry-out bits are denoted by $S[n]$ for the sum and by $T[n]$ for the incremented sum.


alternative view of comp. adder

 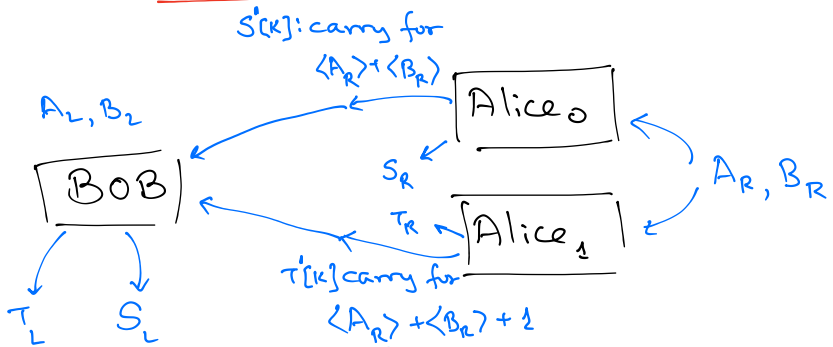

COMP-ADDER(n) - Implementation

basis: $n = 1$, we simply use a Full-Adder and a Half-Adder.


reduction step:

 

COMP-ADDER(n) - example

A 0110
 B 1001


 S 0111
 T 10000

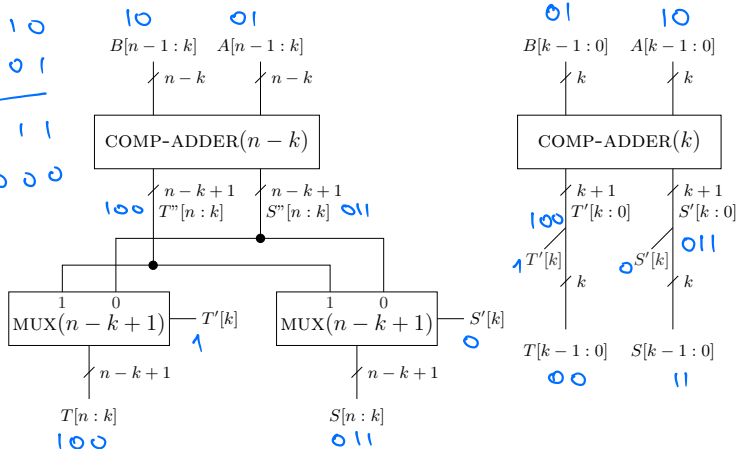

Example

Consider a COMP-ADDER(4) with input $A[3:0] = 0110$ and $B[3:0] = 1001$.

COMP-ADDER(n) - example

 

Claim

The $\text{COMP-ADDER}(n)$ design is a correct adder.

comp-adder (n) correctness

can be proved directly. (see book)
we will use a reduction to CSA (n).

for S: argue that comp-adder output
same as CSA with $c[0] = 0$.

for T: argue that comp-adder output
same as CSA with $c[0] = 1$.

Delay analysis

To simplify the analysis we assume that $n = 2^\ell$. To optimize the delay, we use $k = n/2$.

The delay of a $\text{COMP-ADDER}(n)$ satisfies the following recurrence:

$$d(\text{COMP-ADDER}(n)) = \begin{cases} d(\text{FA}) & \text{if } n = 1 \\ d(\text{COMP-ADDER}(n/2)) + d(\text{MUX}) & \text{otherwise.} \end{cases}$$

Hence,

$$\begin{aligned} d(\text{COMP-ADDER}(n)) &= \ell \cdot d(\text{MUX}) + d(\text{FA}) \\ &= \Theta(\log n). \end{aligned}$$

The cost of a COMP-ADDER(n) satisfies the following recurrence:

$$c(\text{COMP-ADDER}(n)) = \begin{cases} c(\text{FA}) + c(\text{HA}) \\ 2 \cdot c(\text{COMP-ADDER}(n/2)) + (n/2 + 1) \cdot c(\text{MUX}) \end{cases} \quad 2.$$

Hence, $c(\text{COMP-ADDER}) = \Theta(n \log n)$.

SURPRISE!!! $c(\text{COMP-ADDER}(n)) \ll c(\text{CSA}(n))$.
 $n \cdot \lg n \quad \sim n^{1.58} \approx n^{1.58}$

$$f(n) = 2 \cdot f\left(\frac{n}{2}\right) + \Theta(n)$$
$$f(n) = \Theta(n \lg n)$$

Reductions between sum and carry bits

The correctness of $RCA(n)$ implies that, for every $0 \leq i \leq n - 1$,

$$\cancel{C[i] \oplus S[i]} \oplus S[i] = A[i] \oplus B[i] \oplus \cancel{C[i]} \oplus S[i] \oplus C[i] \quad (3)$$

By xoring $C[i] \oplus S[i]$ to both sides, we obtain,

$$C[i] = A[i] \oplus B[i] \oplus S[i]. \quad (4)$$

- defined binary addition.
- Three adder designs: Ripple Carry Adder, Conditional Sum Adder, Compound Adder.
- The problems of computing the sum bits and the carry bits are equivalent with respect to a constant-time linear-cost reduction. Since the cost of every adder is $\Omega(n)$ and the delay is $\Omega(\log n)$, we regard the problems of computing the sum bits and the carry bits as equivalently hard.
- Design methodology: divide & conquer.
- Surprise! $\text{COMP-ADDER}(n)$ is much cheaper asymptotically than a $\text{CSA}(n)$.
- Left to show: an adder with linear cost and logarithmic delay....