

# Digital Logic Design: a rigorous approach ©

## Chapter 20: Synchronous Modules

Guy Even   Moti Medina

School of Electrical Engineering Tel-Aviv Univ.

December 29, 2014

Book Homepage:

<http://www.eng.tau.ac.il/~guy/Even-Medina>

## Example: A two-state FSM

Consider the FSM  $\mathcal{A} = \langle Q, \Sigma, \Delta, \delta, \lambda, q_0 \rangle$  depicted in the next figure, where

$$Q = \{q_0, q_1\},$$

$$\Sigma = \Delta = \{0, 1\}.$$

 


Figure: A two-state FSM.

# Two-State FSMs: Synthesis

Given an FSM  $\mathcal{A} = \langle Q, \Sigma, \Delta, \delta, \lambda, q_0 \rangle$ , the synchronous circuit  $C$  that is obtained by executing the synthesis procedure is as follows. We encode  $Q, \Sigma$  and  $\Delta$  by binary strings. Formally, let  $f, g, h$  denote one-to-one functions, where

$$f : Q \rightarrow \{0, 1\}$$

$$g : \Sigma \rightarrow \Sigma$$

$$h : \Delta \rightarrow \Delta,$$

where

$$f(q_0) = 0, f(q_1) = 1,$$

and

$$\forall x \in \{0, 1\} : g(x) = h(x) = x.$$

## Two-State FSMs: Synthesis - $C_\delta$

We design a combinational circuit  $C_\delta$  that implements the Boolean function  $B_\delta : \{0, 1\}^2 \rightarrow \{0, 1\}$  defined by

$$B_\delta(f(x), g(y)) \triangleq f(\delta(x, y)), \text{ for every } (x, y) \in Q \times \Sigma.$$

$f(x)$	$g(y)$	$f(\delta(x, y))$
0	0	1
1	0	1
0	1	0
1	1	0

Table: The truth table of  $B_\delta$ .

It follows that  $B_\delta(f(x), g(y)) = \text{NOT}(g(y))$ .

We design a combinational circuit  $C_\lambda$  that implements the Boolean function  $B_\lambda : \{0, 1\}^2 \rightarrow \{0, 1\}$  defined by

$$B_\lambda(f(x), g(y)) \triangleq h(\lambda(x, y)), \text{ for every } (x, y) \in Q \times \Sigma.$$

$f(x)$	$g(y)$	$h(\lambda(x, y))$
0	0	1
1	0	1
0	1	0
1	1	1

**Table:** The truth table of  $B_\lambda$ .

It follows that  $B_\lambda(f(x), g(y)) = f(x) \vee \overline{g(y)}$ .

# Two-State FSMs: Synthesis - the Synch. circuit $C$

The synchronous circuit in canonic form constructed from a flip-flops and two combinational circuits is depicted in Figure ??.

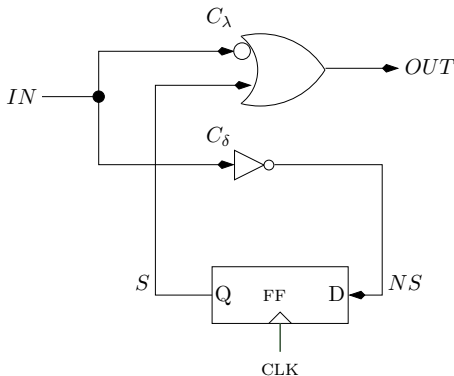


Figure: Synthesis of  $\mathcal{A}$ .

## Definition

A *sequential adder* is defined as follows.

**Inputs:**  $A, B, \text{reset}$  and a clock signal  $\text{CLK}$ , where  
 $A_i, B_i, \text{reset}_i \in \{0, 1\}$ .

**Output:**  $S$ , where  $S_i \in \{0, 1\}$ .

**Functionality:** The *reset* signal is an initialization signal that satisfies:

$$\text{reset}_i = \begin{cases} 1 & \text{if } i = 0, \\ 0 & \text{if } i > 0. \end{cases}$$

Then, for every  $i \geq 0$ ,

$$\langle A[i : 0] \rangle + \langle B[i : 0] \rangle = \langle S[i : 0] \rangle \pmod{2^{i+1}}.$$

## Sequential Adder (cont.)

What happens if the value of the input *reset* equals 1 in more than once cycle? The above definition means that if  $reset_i = 1$ , then we forget about the past, we treat clock cycle  $(t_i, t_{i+1})$  as the first clock cycle.

Formally, we define the last initialization  $r(i)$  as follows:

$$r(i) \triangleq \max\{j \leq i : reset_j = 1\}.$$

Namely,  $r(i)$  specifies the **last** time  $reset_j = 1$  not after cycle  $i$ . If  $reset_j = 0$ , for every  $j \leq i$ , then  $r(i)$  is not defined, and functionality is unspecified. If  $r(i)$  is well defined, then the specification is that, for every  $i \geq 0$ ,

$$\langle A[i : r(i)] \rangle + \langle B[i : r(i)] \rangle = \langle S[i : r(i)] \rangle \pmod{2^{i+1}}.$$



# Sequential Adder: Implementation

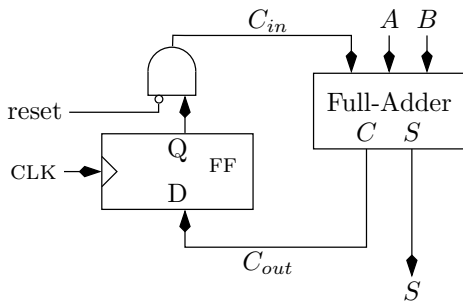


Figure: A synchronous circuit that implements a sequential adder.

# Sequential Adder: Implementation - correctness

## Theorem

$$\sum_{j=0}^i A_j \cdot 2^j + \sum_{j=0}^i B_j \cdot 2^j = \sum_{j=0}^i S_j \cdot 2^j + c_{out}(i) \cdot 2^{i+1} .$$

## Proof.

The proof is by induction on  $i$ . The induction basis for  $i = 0$  follows from the functionality of the full-adder:

$$A_0 + B_0 + C_{in}(0) = 2 \cdot C_{out}(0) + S_0 .$$




# Sequential Adder: Implementation - correctness (cont.)

## Proof.

We now prove the induction step for  $i > 0$ .

$$\begin{aligned}\sum_{j=0}^i A_j \cdot 2^j + \sum_{j=0}^i B_j \cdot 2^j &= (A_i + B_i) \cdot 2^i + \sum_{j=0}^{i-1} A_j \cdot 2^j + \sum_{j=0}^{i-1} B_j \cdot 2^j \\ &= (A_i + B_i) \cdot 2^i + \sum_{j=0}^{i-1} S_j \cdot 2^j + C_{out}(i-1) \cdot 2^i \\ &= (C_{in}(i) + A_i + B_i) \cdot 2^i + \sum_{j=0}^{i-1} S_j \cdot 2^j \\ &= (S_i + 2 \cdot C_{out}(i)) \cdot 2^i + \sum_{j=0}^{i-1} S_j \cdot 2^j \\ &= \sum_{j=0}^i S_j \cdot 2^j + C_{out}(i) \cdot 2^{i+1}.\end{aligned}$$

# Sequential Adder: Analysis

 

**Figure:** an FSM of a sequential adder (each transition is labeled by a pair: the condition that the input satisfies and the value of the output).

## Sequential Adder: Executing $\text{Min-}\Phi(C)$ .

Let  $C$  denote the Sequential Adder that we have just implemented.

Assume that all the parameters equal to '1'. Assume that a full adder is implemented by a single gate.

Execute the  $\text{Min-}\Phi(C)$  algorithm. **Note** that the *reset* signal is also an input signal, hence we should assign a weight to the input gate that feeds it as well.

The “heaviest” path is of weight 5 (*reset* input gate  $\rightarrow$  NOT gate  $\rightarrow$  AND gate  $\rightarrow$  Full adder gate  $\rightarrow$  the output gate the corresponds to the D port), hence  $\varphi^* = 5$ .

# Adding the initialization signal to an FSM

- $C$  is a synchronous circuit without an initialization signal (but we assume FFs output a specific value in  $t = 0$ ).
- Introduce an initialization signal *reset* that initializes the outputs of all flip-flops (namely, it cause the outputs of the flip-flops to equal a value that encodes the initial state).
- How? Replace each edge triggered  $D$ -flip-flop by an edge triggered  $D$ -flip-flop with a reset input. The *reset* signal is fed to the reset input port of each flip-flop.
- Denote the new synchronous circuit by  $\hat{C}$ .
- Let  $\mathcal{A}$  and  $\hat{\mathcal{A}}$  denote the FSMs that model the functionality of  $C$  and  $\hat{C}$ , respectively.
- What is the relation between  $\mathcal{A}$  and  $\hat{\mathcal{A}}$ ?

## Theorem

Let  $\mathcal{A} = \langle Q, \Sigma, \Delta, \delta, \lambda, q_0 \rangle$  denote the FSM that models the functionality of the synchronous circuit  $C$ . Let

$\hat{\mathcal{A}} = \langle Q', \Sigma', \Delta', \delta', \lambda', q'_0 \rangle$  denote the FSM that models the synchronous circuit  $\hat{C}$ . Then,

$$Q' \triangleq Q,$$

$$q'_0 \triangleq q_0,$$

$$\Sigma' \triangleq \Sigma \times \{0, 1\},$$

$$\Delta' \triangleq \Delta,$$

$$\delta'(q, (\sigma, \text{reset})) \triangleq \begin{cases} \delta(q, \sigma), & \text{if } \text{reset} = 0, \\ \delta(q_0, \sigma), & \text{if } \text{reset} = 1, \end{cases}$$

$$\lambda'(q, (\sigma, \text{reset})) \triangleq \begin{cases} \lambda(q, \sigma), & \text{if } \text{reset} = 0, \\ \lambda(q_0, \sigma), & \text{if } \text{reset} = 1. \end{cases}$$

## Definition

A *counter*( $n$ ) is defined as follows.

**Inputs:** a clock  $\text{CLK}$ .

**Output:**  $\{N_i\}_i$ , where  $N_i \in \{0, 1\}^n$ .

**Functionality:** For every  $i$ , the number of clock cycles (mod  $2^n$ ) since the last *reset* equals  $N_i$ .

No input?! Input is “implied”: it is the (missing) reset signal!



# Synthesis and Analysis


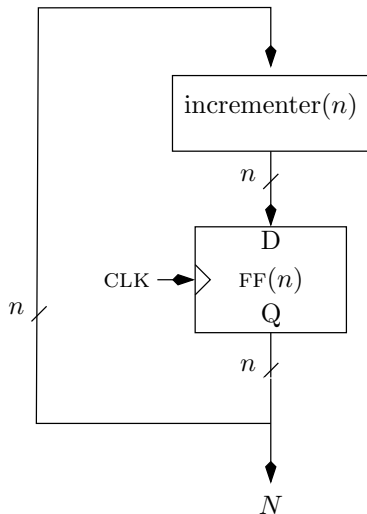


Figure: A synchronous circuit that implements a counter.

 

**Figure:** An FSM of a counter(2). The output always equals the state from which the edge emanates.

# Revisiting Shift Registerers

Recall the definition of a a shift register of  $n$  bits, that is:

**Inputs:**  $D[0](t)$  and a clock  $CLK$ .

**Output:**  $Q[n - 1](t)$ .

**Functionality:**  $Q[n - 1](t + n) = D[0](t)$ .

# Synthesis and Analysis

 


Figure: A 4-bit shift register.

 


Figure: FSM of a 2-bit shift register, also called *De Bruijn Graph*.

## Definition

A RAM( $2^n$ ) is specified as follows.


**Inputs:**  $Address[n - 1 : 0](t) \in \{0, 1\}^n$ ,  $D_{in}(t) \in \{0, 1\}$ ,  
 $R/\overline{W}(t) \in \{0, 1\}$  and a clock CLK.

**Output:**  $D_{out}(t) \in \{0, 1\}$ .

**Functionality** : The functionality of a RAM is specified by the following program:

- ① data: array  $M[2^n - 1 : 0]$  of bits.
- ② initialize:  $\forall i : M[i] \leftarrow 0$ .
- ③ For  $t = 0$  to  $\infty$  do
  - ①  $D_{out}(t) = M[\langle Address \rangle](t)$ .
  - ② For all  $i \neq \langle Address \rangle$ :  $M[i](t + 1) \leftarrow M[i](t)$ .
  - ③

$$M[\langle Address \rangle](t + 1) \leftarrow \begin{cases} D_{in}(t) & \text{if } R/\overline{W}(t) = 0 \\ M[\langle Address \rangle](t) & \text{else.} \end{cases}$$

 

**Figure:** A (partial) FSM of a RAM( $2^1$ ) (the “legend” of the edge labels:  $((D_{in}, \text{address}, R/\overline{W}), D_{out})$ ).

- We presented a few synchronous circuits and their corresponding FSMs. We started by synthesizing a two-state FSM. We then specified, implemented, and analyzed a few synchronous circuits such as: a sequential adder, a counter, a shift register, and a RAM.
- We presented a general method for introducing initialization to a synchronous circuit and to its corresponding FSM.
- When the number flip-flops in a synchronous circuit is large, such as  $\text{RAM}(2^n)$ , it is not very useful to model its functionality by an FSM.