

# Hardware Algorithms: circuits & networks

## Problem Set 4

submit by July 18th

Guy Even and Moti Medina

July 6, 2008

1. Consider the odd-even transposition algorithm. Give an example with  $n$  inputs for which  $n - 1$  levels do not suffice to sort the inputs.

2. Prove the 0-1 Principal for merging and bitonic merging.

Hint: use the follow lemma. A vector  $v$  is bi-sorted/bitonic iff  $f_t(v)$  is bi-sorted/bitonic for every threshold function  $f_t : R \rightarrow \{0, 1\}$  defined by  $f_t(x) = 1 \Leftrightarrow x \geq t$ .

3. Consider a variation of the odd-even merger in which the inputs  $A, B$  are connected to the two smaller mergers as follows:

- top merger is input  $odd(A)$  and  $even(B)$ , and
- bottom merger is input  $even(A)$  and  $odd(B)$ .

(a) Suggest a completion of the circuit using a column of comparison boxes fed by the outputs of the top and bottom mergers.

(b) Prove the correctness of the obtained merging circuit.

4. Bitonic merging. Given a bitonic vector  $\{x_i\}_{i=1}^{2n}$ , for  $i = 1 \dots n$ , let

$$a_i = \min\{x_i, x_{i+n}\}$$
$$b_i = \max\{x_i, x_{i+n}\}.$$

(a) Prove that either:

- $\{a_i\}_{i=1}^n = 0^n$  and  $\{b_i\}_{i=1}^n$  is bitonic, or
- $\{b_i\}_{i=1}^n = 1^n$  and  $\{a_i\}_{i=1}^n$  is bitonic.

(b) Use the above claim to prove the correctness of Batcher's bitonic merging circuit.