 


## Lecture 1

### מעגל צירופי – הגדרה


- אבני הבניין של מעגל צירופי הם שערי and, or, not. הכניסות של השערים הנ"ל סימטריות והם מהווים מערכת אוניברסלית.
- מעגל צירופי בנוי מעץ מכוון עם שורש. הקשתות מכוונות מהעלים לשורש. אין בו מעגלים.



- בכל צומת של העץ ממוקם שער – כך נקבעת הפונקציונליות של המעגל. המעגל מבצע חישוב של הפונקציות הבוליאניות שהשערים ממשים ופלט את ערך היציאה המחושב.
- השהיית המעגל – המסלול הארוך ביותר מעלה לשורש.
- מחיר המעגל – מספר הצמתים בעץ. כלומר, מספר השערים בעץ (במעגל).
- הערה: אנו מניחים שלכל השערים אותה השהייה ואותו מחיר. אפשר היה להוסיף משקל לכל שער. במקרה כזה המחיר היה המשקל הכולל וכו'.
- הערה: העלים יכולים להיות מוזנים על-ידי אותם קלטים.
- דרגת הכניסה – Fan in – מספר הכניסות לשער. בחרנו שיהיה 2 לכל היותר. (כדוגמא לכל הנ"ל נראה שער and מרובה כניסות)
 
### הגדרה חדשה (הרחבת ההגדרה הקודמת):

- נשתמש בדג במקום בעץ – DAG (Directed Acyclic Graph)



- דג אינו עץ. מה שנקרא עלה בעץ נקרא כאן מקור.
- מה שנקרא שורש בעץ נקרא כאן בור.
- לדג יכולים להיות מספר בורות.
- (נראה דוגמאות במהלך ההרצאה)

### 1.8 Gates

The basic building blocks which are used to implement a logic function are called gates. Any equation can be considered as a system having inputs (the variables) and outputs (the result of applying the functions on the variables). The equation  $Y = f(A, B, C)$  describes a system having 3 inputs  $A, B, C$  and a single output  $Y$ .

#### 1.8.1 An AND gate

Its equation is  $Y = A \cdot B$ . We draw it as in Figure 1.4. Its truth table is given below and is identical to the AND operation.

$A$	$B$	$Y$
0	0	0
0	1	0
1	0	0
1	1	1

 


Figure 1.4 – An AND gate

#### 1.8.2 An OR gate

Its equation is  $Y = A + B$ . We draw it as in Figure 1.5. Its truth table is given below and is identical to the OR operation.

$A$	$B$	$Y$
0	0	0
0	1	1
1	0	1
1	1	1

 


Figure 1.5 –An OR gate

### 1.8.3 A NOT gate (usually called an INVERTER)

Its equation is  $Y = \overline{A}$ . We draw it as in Figure 1.6. Its truth table is given below and is identical to the NOT operation.

$A$	$Y$
0	1
1	0

 


Figure 1.6 – An Inverter (a NOT gate)

### 1.8.4 A NAND gate

Its equation is  $Y = \overline{A \cdot B}$ . We draw it as in Figure 1.7. Its truth table is given below.

$A$	$B$	$Y$
0	0	1
0	1	1
1	0	1
1	1	0

 


Figure 1.7– A NAND gate

### 1.8.5 A NOR gate

Its equation is  $Y = \overline{A + B}$ . We draw it as in Figure 1.8. Its truth table is given below.

$A$	$B$	$Y$
0	0	1
0	1	0
1	0	0
1	1	0

 


Figure 1.8 – A NOR gate

## 1.8.6 A XOR gate

Its equation is  $Y = \bar{A} \cdot B + A \cdot \bar{B} = A \oplus B$ . We draw it as in Figure 1.9. Its truth table is given below.

$A$	$B$	$Y$
0	0	0
0	1	1
1	0	1
1	1	0



Figure 1.9 – A XOR gate

Figure 1.10 is a simple example of implementing a Boolean function using gates. We here build a XOR gate, using AND, OR and NOT gates (Note: a dot represents a connection of wires):

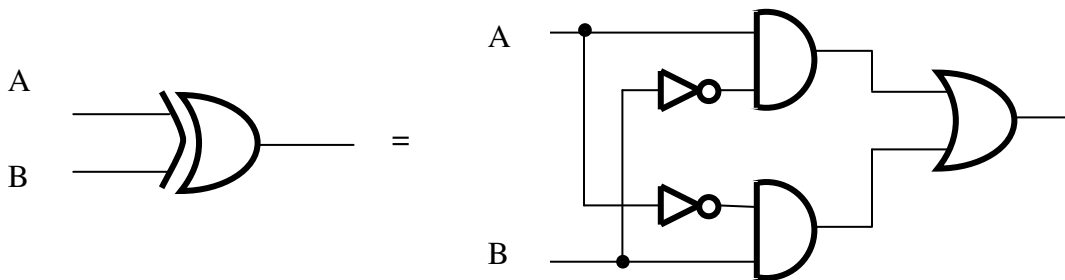


Figure 1.10– Building a XOR gate using AND, OR &amp; NOT gates

### 1.9 A Universal system

Note that since the only operators we defined in Boolean algebra are the AND, OR and NOT operators, it is clear that having these three kind of gates in our hands, enables us to build *any* desired function. Therefore, we call the set of AND, OR and NOT gates, a universal system.

A NAND gate is itself a universal system and so it is called a Universal Gate. In order to show that we can build *any* desired function using only NAND gates, we will show that we can implement all of the 3 operators AND, OR and NOT using only NAND gates. Let us start with the NOT operation. We want to implement  $Y = \overline{A}$  using a NAND gate whose function is  $Y = \overline{A \cdot B}$ . If we choose  $B$  to be 1 or connect the input  $A$  to the other input, we create an inverter since  $Y = \overline{A \cdot 1} = \overline{A}$  and also  $Y = \overline{A \cdot A} = \overline{A}$ :

 


Figure 1.11 – An inverter made of a NAND gate

Since a NAND gate is just an AND gate which is followed by an inverter, all we need in order to convert it “back” to a regular AND gate, is to add one more inverter:

 


Figure 1.12 – An AND gate made of NAND gates

Building the OR is a little bit more difficult. We need to use DeMorgan’s laws:

$Y = A + B = \overline{\overline{A + B}} = \overline{\overline{A} \cdot \overline{B}}$ . Now, it is easy to implement the OR using 3 NAND gates, two as inverters and the third one to perform the NAND operation on the first two’s outputs.


 



Figure 1.13 – An OR gate made out of NAND gates

Let us now try to implement a XOR gate using only NAND gates. The easiest way is to replace any inverter in Figure 1.10 with the inverter of Figure 1.11, and any AND gate with the AND gate of Figure 1.12, and finally, the OR gate with the OR of Figure 1.13:

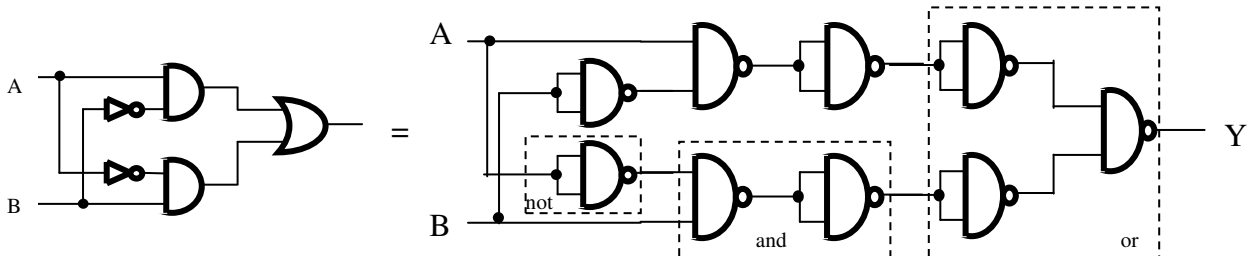

**Figure 1.14 – Building a XOR gate using only NAND gates**

We can reduce the gate count, if we delete the two redundant pairs of inverters. Those are redundant since  $\overline{\overline{X}} = X$ . Eventually we end with:

 

**Figure 1.15 – A XOR gate made of NAND gates**

### 1.10 Timing issues of gates

Let us first define some terms.


A signal is a continuous function of the time  $t$ .

A logic level “0” is a predefined voltage range that is recognized by a gate as a “0” level. In the well-known TTL 74xx logic family, a “0” level was defined as 0.0v to 0.2v.

A logic level “1” is another predefined voltage range that is recognized by a gate as a “1” level. In the 74xx logic family, a “1” level was defined as 2.0v to 5.0v.

The signal has a logic level when the value of the signal is in the range of logic level “0” or in the range of logic level “1”. A signal is called stable at a time interval if it stays in the same logic level along the entire time interval.


Let us explore the behavior of a simple gate. We input the signal  $A(t)$  to an inverter and receive the signal  $Y(t)$  at the inverter’s output.

 

**Figure 1.16 – Naming the signals of a NOT gate**

The input signal  $A(t)$  starts at “1” so  $Y(t)$  is “0”. At a certain point at time, i.e., at  $t_0$ , we change the input signal to be “0”. The gate does not respond immediately. Its response is depicted in Figure 1.17 below. We see that it takes some time till the output signal changes. The time period in which the output signal still stays in the initial logic level, i.e., the time in which the gate “does not response” to the input change, is called the **contamination delay** and is denoted by  $t_{cd}$ . The time required for the output to reach its “final”, i.e., stable level, is called the **propagation delay** and is denoted by  $t_{pd}$ . These two time intervals are described in Figure 1.17 below for the rising and falling of the signals  $A(t)$  and  $Y(t)$  where  $A(t)$  is changing at  $t_0$  and  $t_1$ .

When we implement a logical function using gates, we must consider the timing. When we want to know how soon will the output of a logical system be valid, i.e., in its stable logical level, we need to consider the worst case of all the gates. If this is a combinational system, we should take into account the sum of the delays of the maximal path (longest or slowest) between the input and the output signals. So, for our purposes, we can draw the signals as having valid logical values after the maximal  $t_{pd}$  of the gates involved.

 

**Figure 1.17 – The timing behavior of a NOT gate**

In Figure 1.17, we see the input signal  $A(t)$  at the top. The response of an ideal gate, i.e., without any delay, is described as  $Y_{ideal}(t)$ . The actual signal  $Y(t)$  at the output appears 2<sup>nd</sup> from the bottom. For our analysis of digital circuits we can use the “digital levels” picture shown at the bottom of Figure 1.17.


### 1.11 Multiple inputs gates

Now we know that gates have delays. We should take that into account when we build systems that are more complex than a single gate. In computer science, the analysis of an algorithm usually deals with its complexity or performance, expressed as the number of operations required,




and its cost in the memory units required. In analysis of hardware systems, we have similar measures. The performance is measured by the maximum delay of the system and the cost by the number of required gates.

Let us now build an  $n$  inputs AND gate using two inputs AND gates only. The simplest way is based on induction. When we want to build a three input AND gate using two inputs AND gate we'll use the rules saying that  $Y = A \cdot B \cdot C = (A \cdot B) \cdot C$ , i.e., we'll use one gate to produce  $A \cdot B$  and another gate to AND the result with  $C$ . Using induction, we can quite easily build an  $n$  inputs AND gate, adding a single input at a time. This is depicted in Figure 1.18:

 

**Figure 1.18 – Building an  $n$  inputs AND gate using 2 inputs AND gates**

We will define such a structure “recursively” by describing an  $n$  inputs gate built of an  $(n-1)$  input gate and a simple 2 inputs gate:

 

**Figure 1.19 – Building an  $n$  inputs AND recursively**

In this simple way, the recursive equations describing the cost and the delay of the multiple input gate are  $C(n)=C(n-1)+1$  and  $D(n)=D(n-1)+T$  respectively. In this case, it is easy to see that the cost of an  $n$  inputs AND gate is  $C(n)=n-1$ , i.e., we need  $n-1$  gates, 2 input AND gates, in order to build an  $n$  inputs AND gate. The delay is given by  $D(n)=(n-1)T$  where  $T$  is the delay of a single 2 inputs AND gate. The reason for this dependency of the delay on the number of inputs is the chaining of the gates. Because of this structure, a change in the  $I_0$  should “propagate” through  $n-1$  gated until it “reaches”, i.e., influences, the output  $Y$ . This seems a little exaggerated. There must

be a better way. That way is to use a binary tree structure. The depth of that tree will determine the maximal delay. This can be seen in Figure 1.20 below.


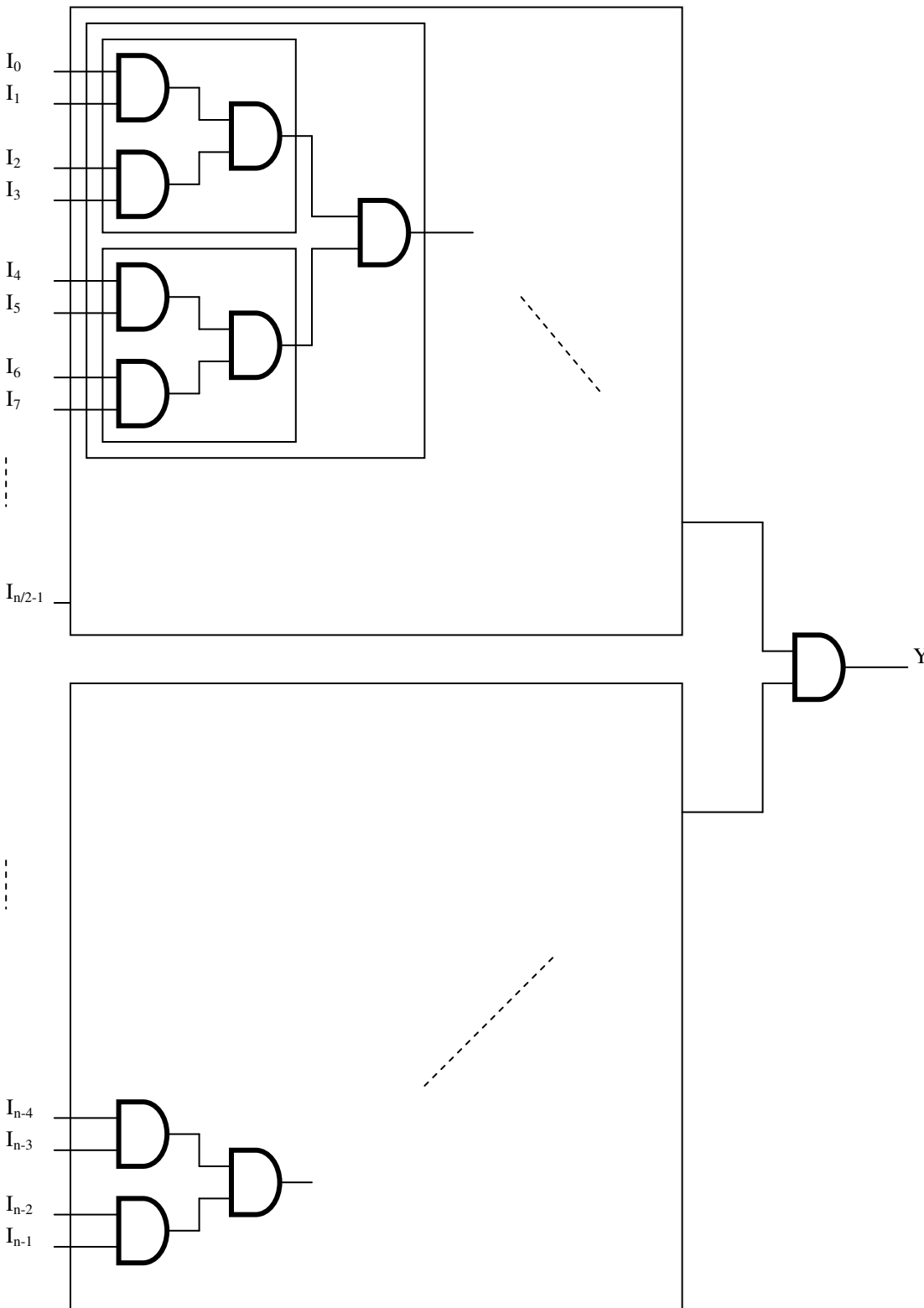


Figure 1.20 – Building an  $n$  inputs AND gate using a tree of inputs AND gates

We can define such a structure “recursively” by describing an  $n$  inputs gate built of two  $n/2$  input gates:

 

**Figure 1.21 –A recursive building of an  $n$  inputs AND gate**

The cost of such an  $n$  inputs gate stays  $C(n)=n-1$ . This is so since it really does not matter how we add the inputs, since every new input forces us to add a single gate. The recursive equation describing the cost is  $C(n)=2C(n/2)+1$  having  $n/2$  but also a factor of 2 certifies a linear cost.

It is quite clear from Figure 1.19 that the delay follows the recursive equations

$D(n) = D(n/2) + T$ . This immediately means that the delay is logarithmic, i.e.,

$D(n) = T \cdot \lg_2 n$ . This is so since we can write:

$D(n) = D(n/2) + T = D(n/4) + T + T = D(n/8) + T + T + T$ , etc., so we see that we

have to sum  $\lg_2 n$  times the delay  $T$ .

When  $n$  is not an exact power of 2, there are several optional trees, all with depth of  $\lceil \lg_2 n \rceil$ , to arrange the gates. The delay in such case is given by  $D(n) = T \cdot \lceil \lg_2 n \rceil$ .

We use basic gates of 2 inputs although in practice gates with more inputs are available.

Note that if we had a basic gate of 3 inputs we would get  $D(n) = T \cdot \lceil \lg_3 n \rceil$ .

## 1.12 Decoders

It is time now to get to our first useful system. We are going to build a Decoder. A decoder has  $n$  inputs and  $2^n$  outputs. Only one of its outputs is “1” at a given time. The combination of the  $n$  input lines, each can be “0” or “1”, determines which of the outputs is “on”, i.e., “1”. As a matter of fact, the combination at the input represents a binary number in which the rightmost digit has a value (or weight) of 1, the next digit has a value of 2, the next has a value of 4 and the next of 8 and so on. Thus the combination 0101 has a value of  $0 \cdot 8 + 1 \cdot 4 + 0 \cdot 2 + 1 \cdot 1 = 5$  and the combination 0111 has a value of 7 since  $0 \cdot 8 + 1 \cdot 4 + 1 \cdot 2 + 1 \cdot 1 = 7$ . We would like to build a decoder having only two inputs,  $I_0$  and  $I_1$ , forming together a two bit number  $[I_1, I_0]$  which can have the values 0,1,2 or 3. And so, the decoder has 4 outputs  $Y_0, Y_1, Y_2$ , and  $Y_3$ . We would like the  $i$ -th output to be “1” when the input has the combination that represent the number  $i$ .

How do we do that?

We use a truth table to describe the decoder and then find the equations of the outputs from that table;

$[I_1 I_0]$	$Y_0$	$Y_1$	$Y_2$	$Y_3$
00	1	0	0	0
01	0	1	0	0
10	0	0	1	0
11	0	0	0	1

We immediately see that the equations of the outputs are given by:

$$Y_0 = \overline{I_1} \cdot \overline{I_0}$$

$$Y_1 = \overline{I_1} \cdot I_0$$

$$Y_2 = I_1 \cdot \overline{I_0}$$

$$Y_3 = I_1 \cdot I_0$$

So the decoder can be built as described in Figure 1.22 below:

 


Figure 1.22 – A 2 inputs → 4 outputs decoder

Note that the procedure that we'll always use is: First, define the required device. Then, build its truth table. Then, find its equations from the truth table. Then implement it with gates.

We would now like to recursively build an  $n$  inputs decoder using  $(n-1)$  inputs decoders. When we design a VLSI chip, we want to get rid of all redundant parts. Another look at Figure 1.23 reveals that the two decoders produce similar outputs. Therefore, a better design is to use a single decoder and duplicate its output as shown in Figure 1.26.


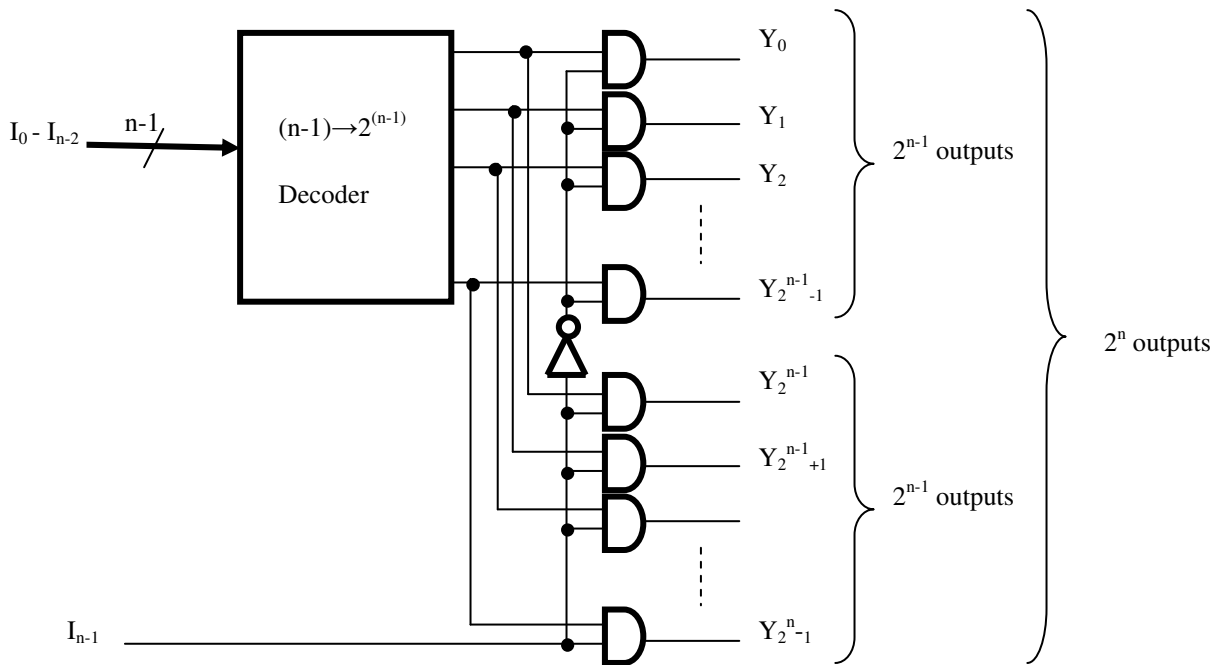


Figure 1.26 – A Recursive Decoder

In Figure 1.27 we show a 3→8 decoder built that way:

 

**Figure 1.27 – A complete 3→8 recursive decoder**

It is quite easy to see that the delay of such a decoder is given by  $D(n)=D(n-1)+T$  where  $T$  is the delay of a single gate. This means that we have  $D(n)=n \cdot T$ . Note that this structure is similar to the first way in which we built an  $n$  input AND gate (Figures 1.18 and 1.19). We can use a "tree style" approach to get a logarithmic delay. Try to do that as a homework exercise.


The cost of the system in Figure 1.26, is  $n$  inverters and much more AND gates so we just count the AND gates as the cost. Since we see that the cost follows the recursive equation  $C(n)=2 \cdot 2^{n-1}+C(n-1)=2^n + C(n-1)$ , we have a geometric sequence with  $q=2$ . Since  $C(1)=0$ ,  $C(2)=4$ , we have  $C(n)=2^2 + 2^3 + \dots + 2^n = 2^{n+1} - 4$ .

There are two more issues in designing such systems that we did not consider. One is the length of the lines, i.e., the connecting wires. This has to do with the area of silicon that is required in

order to implement the design on silicon. We will not discuss that issue. The other thing is the Fan out of the gates. The gates are electronic devices which have output and input currents. Since the output current of a gate is limited, it can “drive” only a limited number of gates. The number of gate inputs that can be driven by the output of a gate is called the Fan out of that gate. A typical value of the Fan out is 10 to 20. We would like to analyze a much severe case where the fan out of a gate is only 2. (Less than 2 means that we can connect the output of a gate only to a single input. This is too restrictive.)

In our decoder, we see that each AND gate drives two other gates, so there is no problem there. However, the inverters drive up to  $2^{n-1}$  inputs, i.e., the number of the inputs that should be driven by the inverters is exponential! How can we overcome such a problem when the allowed fan out is only two?

The answer is that we should build a “tree” of inverters to produce  $2^{n-1}$  inverted outputs and  $2^{n-1}$  non-inverted outputs from the  $I_{n-1}$  input:

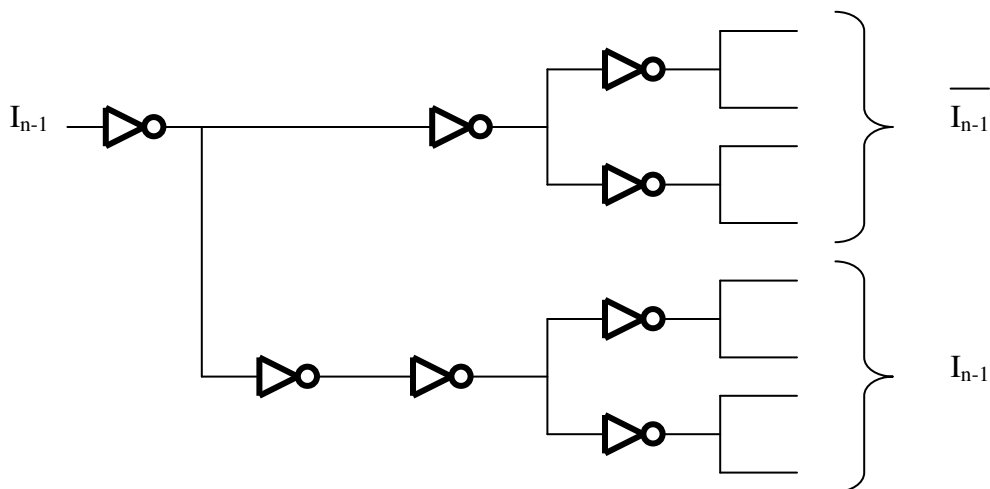

**Figure 1.28 – A fan out expansion tree**

Note that since the depth of such a tree is about  $n$ , we almost did not increase the delay of the decoder.

## 1.13 Multiplexers

A multiplexer (Mux), as a decoder, is one of the basic devices used in building computers. An  $n \rightarrow m$  multiplexer,  $n > m$ , is a device with  $n$  inputs and  $m$  outputs. It also has some select inputs that determine which of the inputs are transferred to the outputs.

### 1.13.1 A simple mux

We follow our design procedure: First, define the required device. Then, build its truth table. Then, find its equations from the truth table. Then implement it with gates. So, we first define the simplest multiplexer which is a  $2 \rightarrow 1$  multiplexer. It has two data inputs  $A$  and  $B$  (or  $I_0$  and  $I_1$ ) and a single data output,  $Y$ . It also has a single select input denoted by  $S$ . Its drawing and function is given in Figure 1.29.

 


Figure 1.29a – The schematic drawing of  $2 \rightarrow 1$  multiplexer

 


Figure 1.29b – A  $2 \rightarrow 1$  mux selects between the 2 inputs

As shown in Figure 1.29b, the multiplexer functions as a switch. The  $S$  input determines which of the two inputs is “connected” to the output  $Y$ . When  $S = '0'$ , we have  $Y = A$  (or  $Y = I_0$ ). When  $S = '1'$ , we have  $Y = B$  (or  $Y = I_1$ ). The function of the mux can be written as:

$$Y = \begin{cases} A & \text{if } S=0 \\ B & \text{if } S=1 \end{cases}$$



The truth table is therefore:

S	A (I <sub>0</sub> )	B (I <sub>1</sub> )	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

The logic function of a mux is very simple:

$$Y = A \cdot \bar{S} + B \cdot S \quad (\text{or if we use the other notation: } Y = I_0 \cdot \bar{S} + I_1 \cdot S).$$

The implementation using gates is also simple:

 
 


Figure 1.30 – The inside of 2→1 multiplexer

1.13.2 First expansion: A  $2n \rightarrow n$  mux , also called  $n^*(2 \rightarrow 1)$  mux

The  $2n \rightarrow n$  mux has  $2n$  inputs and  $n$  outputs as shown in Figure 1.31. The data inputs represent two  $n$  bit numbers and the  $S$  input determines which of them is transferred to the  $n$  outputs. We denote the  $A$  inputs by  $A[n-1:0]=[A_{n-1},A_{n-2},\dots,A_0]$ , the  $B$  inputs by  $B[n-1:0]=[B_{n-1},B_{n-2},\dots,B_0]$ , and the data outputs,  $Y$  by  $Y[n-1:0]=[Y_{n-1},Y_{n-2},\dots,Y_0]$ .

 


**Figure 1.31 – The schematic drawing of an  $n^*(2 \rightarrow 1)$  multiplexor**

The function of the mux can be given by:

$$Y[n-1:0] = \begin{cases} A[n-1:0] & \text{if } S=0 \\ B[n-1:0] & \text{if } S=1 \end{cases}$$

This can be implemented using  $n$  regular  $2 \rightarrow 1$  muxes, i.e., the  $A_i$ ,  $B_i$  and the  $Y_i$  are connected to a single  $2 \rightarrow 1$  mux. So, now we understand why we called that mux an  $n^*(2 \rightarrow 1)$  mux. In Figure 1.32 we see the internal structure of a  $3^*(2 \rightarrow 1)$  mux.



**Figure 1.32 – The inside of a  $3^*(2 \rightarrow 1)$  mux**

1.13.3 Second expansion: A  $2^k \rightarrow 1$  mux

The  $2^k \rightarrow 1$  mux has  $2^k$  inputs and a single output as shown in Figure 1.31. There are also  $k$  select inputs denoted  $S[k-1:0]=[S_{k-1},S_{k-2},\dots,S_1,S_0]$ . There are  $2^k$  combinations to the select lines. When  $S[k-1:0]=i$ , i.e., the combination of  $[S_{k-1},\dots,S_0]$  represents the number  $i$ , the  $i$ -th input is transferred to the output  $Y$ . Since there are  $2^k$  inputs we have chosen to denote those inputs by  $I_0, I_1, \dots, I_{2^k-1}$ . Note that the simple  $2 \rightarrow 1$  mux we studied before, is a particular case with  $k=1$ .


 


Figure 1.33 – The schematic drawing of a  $2^k \rightarrow 1$  multiplexor

We would like to build an  $8 \rightarrow 1$  (i.e., a  $2^3 \rightarrow 1$ ) mux using 2 muxes of  $4 \rightarrow 1$ . This is pretty easy. We have to add another select input,  $S_2$ , to the two select inputs,  $S_1$  and  $S_0$ , of the  $4 \rightarrow 1$  muxes (i.e.,  $2^2 \rightarrow 1$  muxes). This  $S_2$  input will choose between the two outputs of the two  $4 \rightarrow 1$  muxes, as in Figure 1.34 below.

 


The number represented by  $S[k-1:0]$  is the serial number of the input transferred to the output.

$S_2$	$S_1$	$S_0$	
0	0	0	= 0
0	0	1	= 1
0	1	0	= 2
0	1	1	= 3
1	0	0	= 4
1	0	1	= 5
1	1	0	= 6
1	1	1	= 7

Figure 1.34 – A  $2^3 \rightarrow 1$  mux build of two  $2^2 \rightarrow 1$  muxes

Since adding a select line exactly doubles the number of combinations, we can similarly build a  $2^k \rightarrow 1$  mux using two  $2^{k-1} \rightarrow 1$  muxes and a single  $2 \rightarrow 1$  mux. Thus, we can build a  $2^k \rightarrow 1$  mux recursively. In Figure 1.35 we see the recursive definition of such a mux.

 

**Figure 1.35 – Building a mux recursively**

The cost equation is  $C(k) = 2 \cdot C(k-1) + C(1)$ . This means that the cost is actually:  
 $C(k) = C(1) \cdot [1 + 2 + 4 + \dots + 2^{k-1}] = C(1) \cdot (2^k - 1)$ . Note that here we look at  $k$  instead of  $n$  where  $n$  is the number of the inputs and follows  $n = 2^k$ . So  $C(n) = C_{2 \rightarrow 1} \cdot (n - 1)$ .

The delay equation is  $D(k) = D(k-1) + D(1)$ . This means that the delay is given by  $D(k) = k \cdot D(1)$  or  $D(n) = \lg_2 n \cdot D_{2 \rightarrow 1}$ .

In Figure 1.36 we show the entire tree of an  $8 \rightarrow 1$  mux.


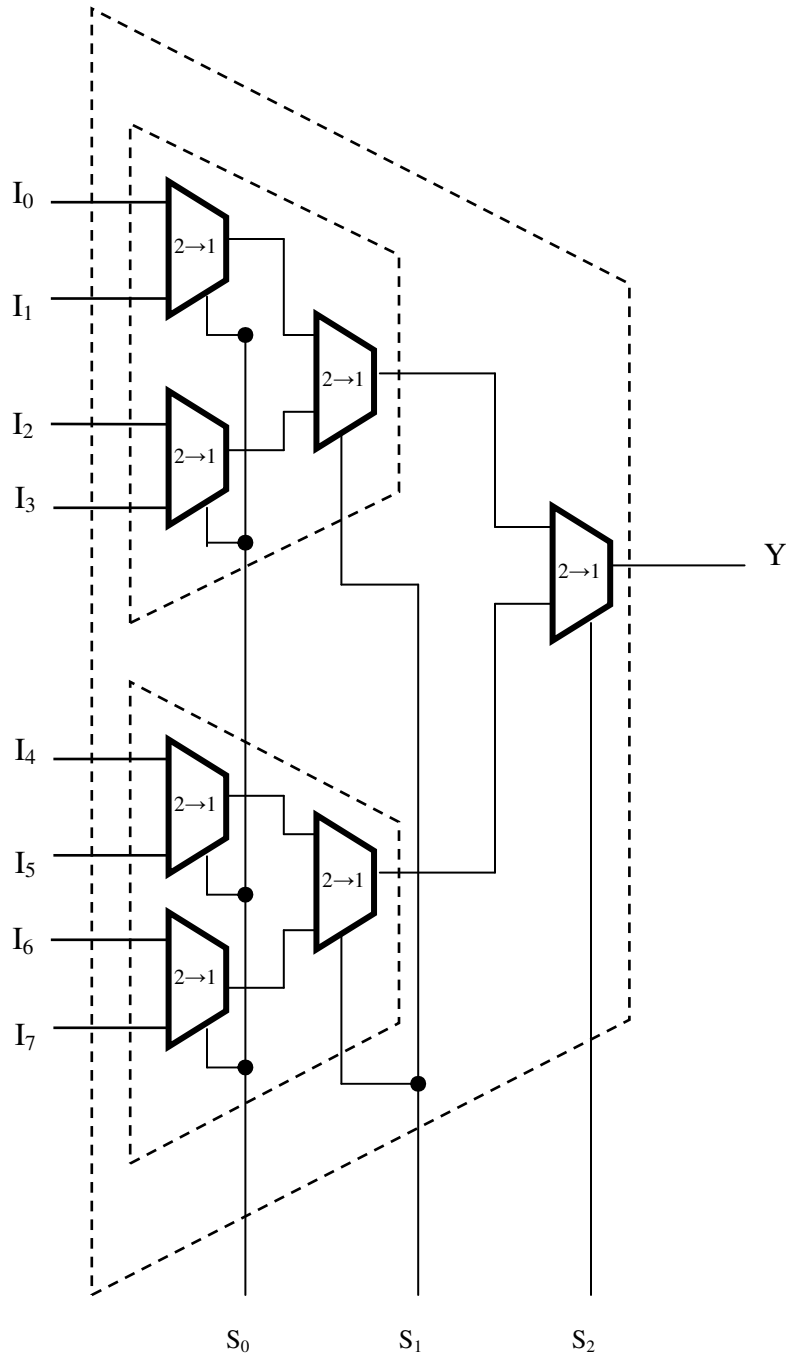


Figure 1.36 – The entire recursion depth in an 8→1 mux

1.13.4 Third expansion: An  $n \times (2^k \rightarrow 1)$  mux

The  $n \times (2^k \rightarrow 1)$  mux has  $2^k$  inputs,  $n$  bits each, i.e., each input represent an  $n$  bits binary number, and a single  $n$  bits output as shown in Figure 1.37. There are also  $k$  select inputs denoted  $S[k-1:0]=[S_{k-1},S_{k-2},\dots,S_1,S_0]$ . There are  $2^k$  combinations to the select lines. When  $S[k-1:0]=i$ , the  $i$ -th input is transferred to the output  $Y$ . Since there are  $2^k$  inputs we have choose to denote those inputs by  $I_0, I_1, \dots, I_{2^k-1}$ , sometimes denoted  $A,B,\dots,Z$ .

 

**Figure 1.37 – The schematic drawing of an  $n \times (2^k \rightarrow 1)$  multiplexer**

Similarly to the first expansion, the  $n \times (2^k \rightarrow 1)$  mux is built of  $n$  muxes of  $2^k \rightarrow 1$ , each of them takes care for one of the  $n$  bits. An example of a  $12 \rightarrow 3$  mux, i.e., a  $3 \times (2^2 \rightarrow 1)$  mux, is given in Figure 1.38 below.

 


Figure 1.38 – The inside of a  $3 \times (2^2 \rightarrow 1)$  mux

We can also take apart the  $4 \rightarrow 1$  muxes, which, as we already know, are built of  $2 \rightarrow 1$  muxes:

 


Figure 1.39 – The inside of a  $3 \times (2^2 \rightarrow 1)$  mux in detail

Figure 1.40 below shows the entire muxes family:



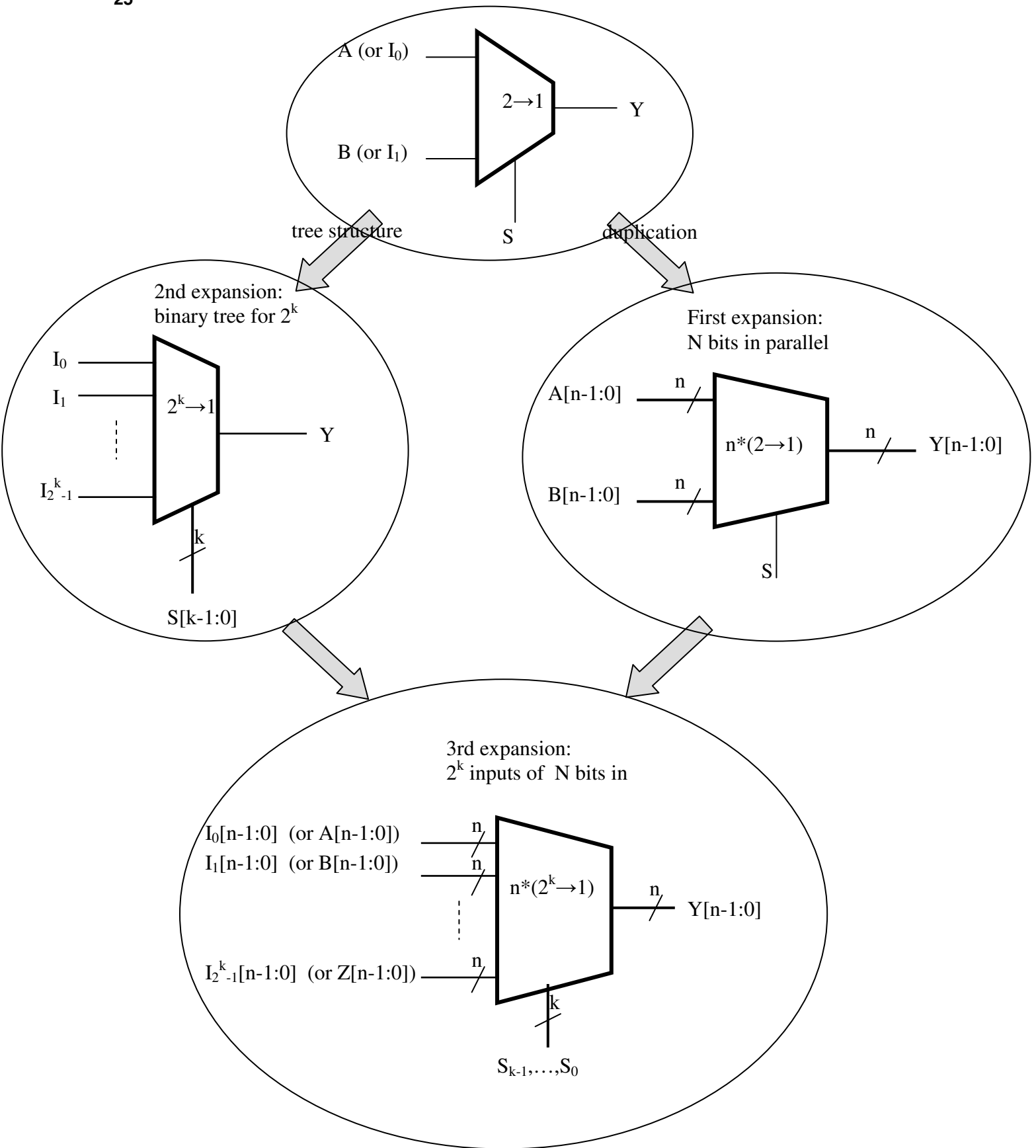


Figure 1.40 – The entire multiplexers family

We have only one last thing to say about muxes and decoders. They complement each other. A mux is the “inverse” of a decoder. To show that, we will change our interpretation of decoders. Let us look at a 2→4 decoder that has an enable input denoted E. If E=’0’ all outputs of the decoder are “0”. If E=’1’, then the output selected by the code, or combination, of the inputs is “1”. So, one can see the decoder as a switch controlled by the inputs that transfers the E data into one of the output as in Figure 1.41.

 


Figure 1.41 – A decoder as a controlled switch

We can use Muxes and Decoders to multiplex multiple data streams on a single line as in Figure 1.42. This is called TDM, Time Division Multiplexing, since when we sequentially change the selection code  $S[1:0]=0 \rightarrow 1 \rightarrow 2 \rightarrow 3 \rightarrow 0 \rightarrow 1 \rightarrow \dots$  etc., we have a different data stream appearing on the line at different times. Note that the rate of switching the select lines should be 4 times higher than the rate in which the data streams may change.

 


Figure 1.42 – 4 data lines sharing a single line


**Suggested homework:** 1) A “recursive” comparator 2) "ALT" detector 3) A “tree” decoder

### 3) Adders and ALU circuits

In this section we will use the knowledge we acquired in the previous two chapters to design Adders and ALU.

#### 3.1) A Half Adder

We begin with designing a component called a Half Adder. This component, depicted in Figure 3.1 below, as well as its truth-table, is capable of adding two one bit numbers.

 


**Figure 3.1 – A Half Adder**

The equations of a Half-Adder are easily found from its truth-table:

$$Y = \bar{A} \cdot B + A \cdot \bar{B} = A \oplus B$$


$$C_o = A \cdot B$$

So, the implementation of a Half-Adder (HA) is simple and involves only two gates:

 

**Figure 3.2 – The inside of a Half-Adder**

The reason that this device is called a Half-Adder is that we need two of these in order to add longer numbers. Let us demonstrate it. We'll try to build an Adder that will add two 6 bits numbers  $A[5:0]$  and  $B[5:0]$ . We connect the  $A_i$ -th and  $B_i$ -th bits to a Half-Adder that produces the  $Y_i$ -th output and hope for good:

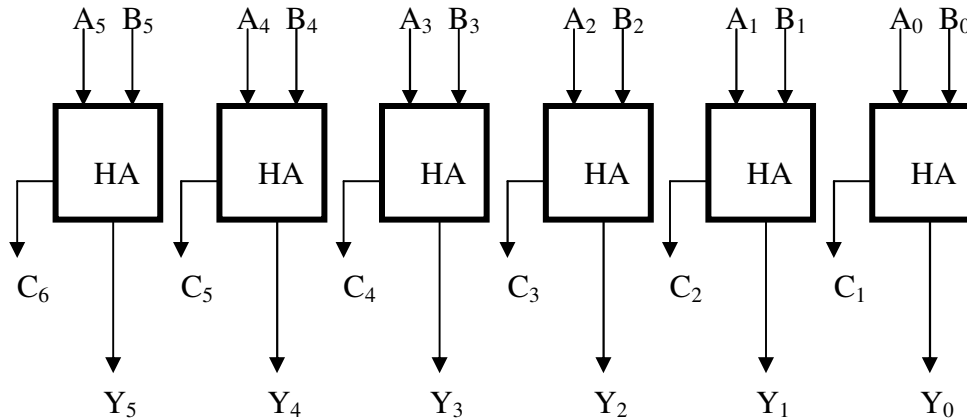

**Figure 3.3 – Trying to build an adder .:**

Let us now try to use the adder for adding some unsigned numbers. We do not have any problems in adding  $A=001100$  and  $B=010001$ . But we seem to have a problem adding  $A=001100$  and  $B=001010$ . The 4 LSBs of  $Y[5:0]$ , i.e.,  $Y_0, Y_1, Y_2,$  and  $Y_3$  are OK. But  $Y_4$  is not, since the addition of  $A_3$  and  $B_3$  produces a carry, given by the signal  $C_4$  which is “1”, but has no influence on  $Y_4$ . Such an adder cannot handle cases of carry. We need to do some modifications to this design as is explained below.

### 3.2) A Full Adder

Let us try to imitate the way we, humans, do the addition of two binary numbers. Let us add the two numbers  $A=0111100$  and  $B=0101010$ . We add the numbers bit by bit. When carry is produced, we add it to the next digit; (the result of each step is in red, older results are in blue)

$$\begin{array}{r} A = 0111100 \\ + B = 0101010 \\ \hline \end{array}$$

- Calculating  $Y_0$  and  $C_1$ :                    **00** we calc  $A_0+B_0=[C_1, Y_0]=0+0=[0,0]$
  - Calculating  $Y_1$  and  $C_2$ :                    **010** we calc  $A_1+B_1+C_1=[C_2, Y_1]=0+1+0=[0,1]$
  - Calculating  $Y_2$  and  $C_3$                     **0110** we calc  $A_2+B_2+C_2=[C_3, Y_2]=1+0+0=[0,1]$
  - Calculating  $Y_3$  and  $C_4$                     **10110** we calc  $A_3+B_3+C_3=[C_4, Y_3]=1+1+0=[1,0]$
  - Calculating  $Y_4$  and  $C_5$                     **100110** we calc  $A_4+B_4+C_4=[C_5, Y_4]=1+0+1=[1,0]$
  - Calculating  $Y_5$  and  $C_6$                     **1100110** we calc  $A_5+B_5+C_5=[C_6, Y_5]=1+1+1=[1,1]$
  - Calculating  $Y_6$  and  $C_7$                     **01100110** we calc  $A_6+B_6+C_6=[C_7, Y_6]=0+0+1=[0,1]$
- The final 6 bits result:                    **1100110**

We can build a device that first adds the two digits  $A_i$  and  $B_i$  and then adds the carry,  $C_i$ . The only issue we have left is how to calculate the carry to the next digit,  $C_{i+1}$ :

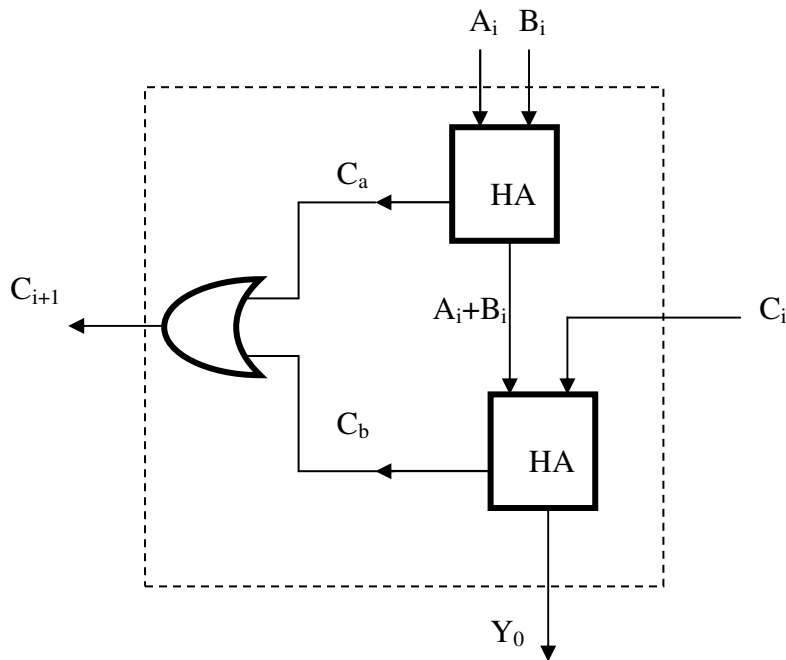


Figure 3.4 – A Full-Adder device .;

Such a device is called a Full-Adder (FA). In Figure 3.4 we demonstrate building a Full-Adder using two Half-Adders. We see that we first add the two digits and then add also the carry in. It is easy to see that we would have carry out only when two (or more) of the inputs  $A_i$ ,  $B_i$ ,  $C_i$  are “1”s (see the truth-table below). Let us now make sure that the circuit calculates  $C_{i+1}$  correctly:

When  $A_i=B_i=1$ , then  $C_a=1$ , and so  $C_{i+1}=1$ . This is the only case in which  $C_a=1$ .

When  $C_i=0$ , we have no problem since  $C_b=0$ , and so only  $C_a$  can cause  $C_{i+1}$  to be “1”. This of course happens only if  $A_i=B_i=1$ .

When  $C_i=1$ , we have to worry only about the case in which we have  $A_i \neq B_i$ , since if they are equal, then if they are “0”,  $A_i+B_i$  is also “0” and no carry is produced at all. If they are “1”s, then, although  $C_b=0$ , we have carry since  $C_a=1$ .


When  $C_i=1$  and  $A_i \neq B_i$ , we know that there must be carry. Since in this case we have  $A_i+B_i=1$ , we also have  $C_b=1$  and therefore  $C_{i+1}=1$  as desired.

Thus, the circuit depicted in Figure 3.4 satisfies the truth-table of a Full-Adder (FA) that is shown below.

By the way, note that the unsigned number  $[C_{i+1}, Y]$  actually represents the number of “1”s in the set  $\{A_i, B_i, C_i\}$ .

$C_i$	$A_i$	$B_i$	$C_{i+1}$	$Y_i$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

The schematic drawing of a Full-Adder is shown in Figure 3.5 below.

 


**Figure 3.5 – The schematic drawing .:**

We could have used the truth-table and Karnaugh maps to find the equations of  $Y$  and  $C_{i+1}$ . Those are:

$$\begin{aligned}
 Y &= \overline{A_i} \cdot B_i \cdot \overline{C_i} + A_i \cdot \overline{B_i} \cdot \overline{C_i} + \overline{A_i} \cdot \overline{B_i} \cdot C_i + A_i \cdot B_i \cdot C_i = \\
 &= (\overline{A_i} \cdot B_i + A_i \cdot \overline{B_i}) \cdot \overline{C_i} + (\overline{A_i} \cdot \overline{B_i} + A_i \cdot B_i) \cdot C_i = (A_i \oplus B_i) \cdot \overline{C_i} + \overline{(A_i \oplus B_i)} \cdot C_i = \\
 &= A_i \oplus B_i \oplus C_i \\
 C_{i+1} &= A_i \cdot B_i + A_i \cdot C_i + B_i \cdot C_i
 \end{aligned}$$

So we can draw the implementation of a Full-Adder using gates:

 


**Figure 3.6 – The inside of a Full-Adder**

We can use a slightly different equation for  $C_{i+1}$ :

$$C_{i+1} = A_i \cdot B_i + (A_i \oplus B_i) \cdot C_i$$

which changes the implementation slightly to:

 

**Figure 3.7 – Another implementation of a Full-Adder**


Note that this implementation has fewer gates than the previous one, but the delay from  $A_i$  or  $B_i$  to  $C_{i+1}$  is larger since an extra gate is included in this path (if a 3 input gate has the same delay). Note that this implementation is identical to Figure 3.4.

We are ready now to build our first Adder.

### 3.3) A Ripple Carry Adder

 A Ripple Carry Adder is an adder built of Full-Adders very similarly to our first try of Figure 3.3. This time we use Full-Adders instead of the Half-Adders and connect the carry-out of a digit to the carry-in of the next digit:

 




**Figure 3.8 – A Ripple Carry Adder .;**

This kind of an adder is called a Ripple Carry Adder (RCA) since the carry propagates through the Full-Adders like a wave.

Note that, as explained in the previous chapter, this adder is capable of adding two unsigned numbers, or two 2's Comp. numbers.



*Figure 3.9 - The schematic III*

The cost of a RCA with width of  $n$  bits, i.e., an adder capable of adding two  $n$  bits numbers, is  $n$  times the cost of a single Full-Adder. Let us choose the implementation of Figure 3.7, i.e., we have 5 gates in a Full-Adder. Thus, we have

$$C(n) = n \cdot C_{FA} = 5 \cdot n$$

This means that when we double the width of our processor word we will need to pay twice the price.

The delay of a RCA depends on the carry propagation. The first stage calculating  $Y_0$ , will have the correct result after the delay of the two XOR gates of the right-hand side FA. The second stage, calculating  $Y_1$ , will have the correct result later, since we have to wait for  $C_1$  and then wait another delay of a XOR gate till  $Y_1$  is ready. For  $Y_2$ , we have to wait for  $C_2$  which depends on  $C_1$ , and so on, as shown in Figure 3.10. Thus, a two gates delay should be added for every bit. Eventually we have:

$$D(n) = n \cdot 2 \cdot T + T, \text{ where } T \text{ is the delay of a single gate.}$$

This is so since in order to calculate  $C_n$ , which is required some times, we need to wait  $3T$  until we produce  $C_1$  and then,  $2(n-1)T$  until the carry propagates through the next  $(n-1)$  stages, i.e., the total delay of this adder is  $(2n+1)T$ .

The time required for  $Y_{n-1}$  to be ready is  $3T+(n-2) \cdot 2T+T=2nT$ .

 


Figure 3.10 – Delay in a RCA

In case we would have used the implementation of Figure 3.6, even only for the 1<sup>st</sup> stage, we would shorten the time by  $T$  to all outputs (except  $Y_0$ ), and so we would have  $D(n) = n \cdot 2 \cdot T$ , (for  $C_n$ ).

We definitely have  $D(n) = O(n)$ , i.e., a linear delay.

This is not a good result. It means that when we double the word width of our computer, we also double the calculation time, i.e., we make our computer two times slower than before. We will later try to improve the performance. We would like to have a linear cost and a logarithmic delay. This is the best we can hope for.

### 3.4) ALU

Although we are not satisfied with the performance of our adder (the RCA), we are now ready to design the heart of a CPU, the Arithmetic Logic Unit (ALU). The ALU is the part of the CPU that does all the computations.

First, we'll improve the functionality of our adder by adding the capability of performing subtraction.

Since, as we already know,  $A - B = A + \overline{B} + 1$ , all we have to do in order to subtract  $B$  from  $A$  is to invert its bits and add the inverted number to  $A$ , and also add 1. Adding 1 is very easy. We'll use  $C_0$  for that. This is actually the reason we used a Full-Adder in the 1<sup>st</sup> stage instead of a Half-Adder which is slightly faster and less expensive. Having the  $C_0$  input is also useful for "add with carry" operations.

The SUB input controls the function of the circuit. In case  $SUB="0"$ ,  $B$  is not inverted (the XOR gate actually means that each bit of  $B$  is XORed with SUB), and  $C_0="0"$ , thus the circuit calculates  $Y=A+B$ . In case  $SUB="1"$ ,  $B$  is inverted and  $C_0="1"$ , so the circuit calculates  $Y=A-B$ . (Note: try to prove that when this circuit is used for unsigned numbers subtraction, the result is negative if  $C_n="0"$  !! I.e.,  $C_n$  is definitely not equal to the borrow we expect when subtracting 2 unsigned numbers).

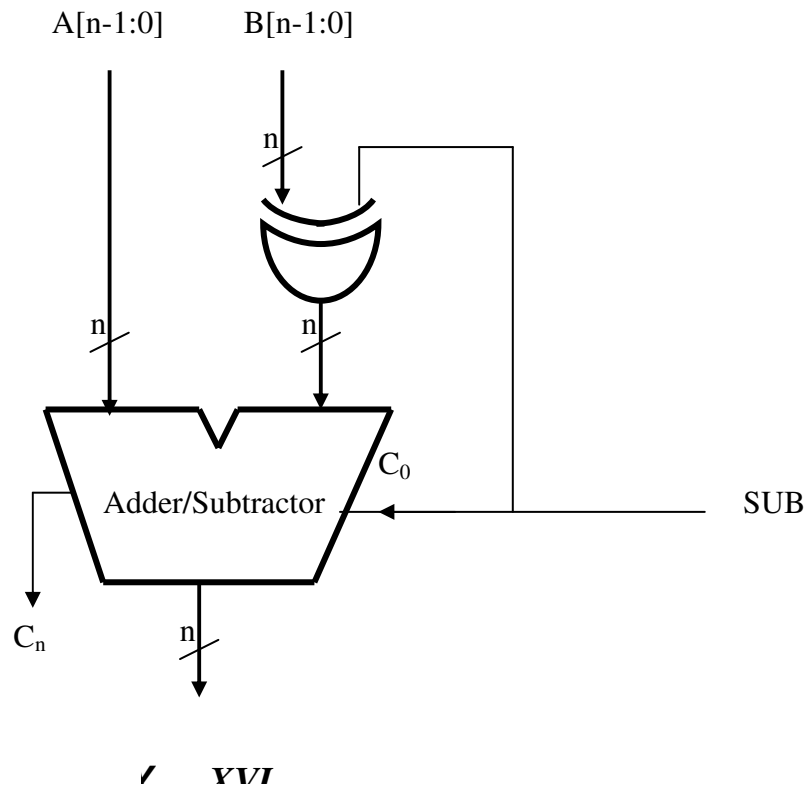


Figure 3.11 - An n-bit Adder/Subtractor

It is very simple to add some Logical operation to the Adder/Subtractor, and so, to form an ALU. Let us define the functionality of an ALU we want to design. We want the ALU to have two n bits inputs, the numbers  $A[n-1:0]$  and  $B[n-1:0]$ , and an n bit output called  $Y[n-1:0]$ . We need to have some control lines, say 3 select lines,  $S_2, S_1, S_0$ , that will determine the operation performed by the ALU. The following table shows the desired functionality of our ALU:

S[2:0] Code			The operation performed by the ALU	The name of the operation
S <sub>2</sub>	S <sub>1</sub>	S <sub>0</sub>		
0	0	0	Y = A plus B	Add
0	0	1	Y = A - B	Sub
0	1	0	Y = A · B	AND
0	1	1	Y = A + B	OR
1	0	0	Y = A ⊕ B	XOR
1	0	1	Y = $\overline{A}$	NOT
1	1	0	Y = A	
1	1	1	Y = B	

The way to get such functionality is to perform all those operations (almost) in parallel using 8 (actually 7) h/w units that perform those 8 operations. Some of the units are very simple, just n gates each (e.g., the AND, OR, XOR, NOT, i.e., all the logical operations). Some are much more complicated (e.g., the Adder/Subtractor). We use a multiplexer to select the appropriate output according to the select code. Since the Adder/Subtractor is used for two operations, its output is connected to two inputs of the multiplexer, the ones that are selected by [000] and [001].

We also add some special outputs. The ZR output is “1” if the ALU’s output is zero. The C<sub>n</sub> is “1” when there is a carry-out. We usually also add the NEG output which is the sign bit of Y, i.e., Y<sub>n-1</sub>, and the OVF output, which tells us if 2’s Comp overflow had occurred. (The last two outputs are not shown in Figure 3.12).

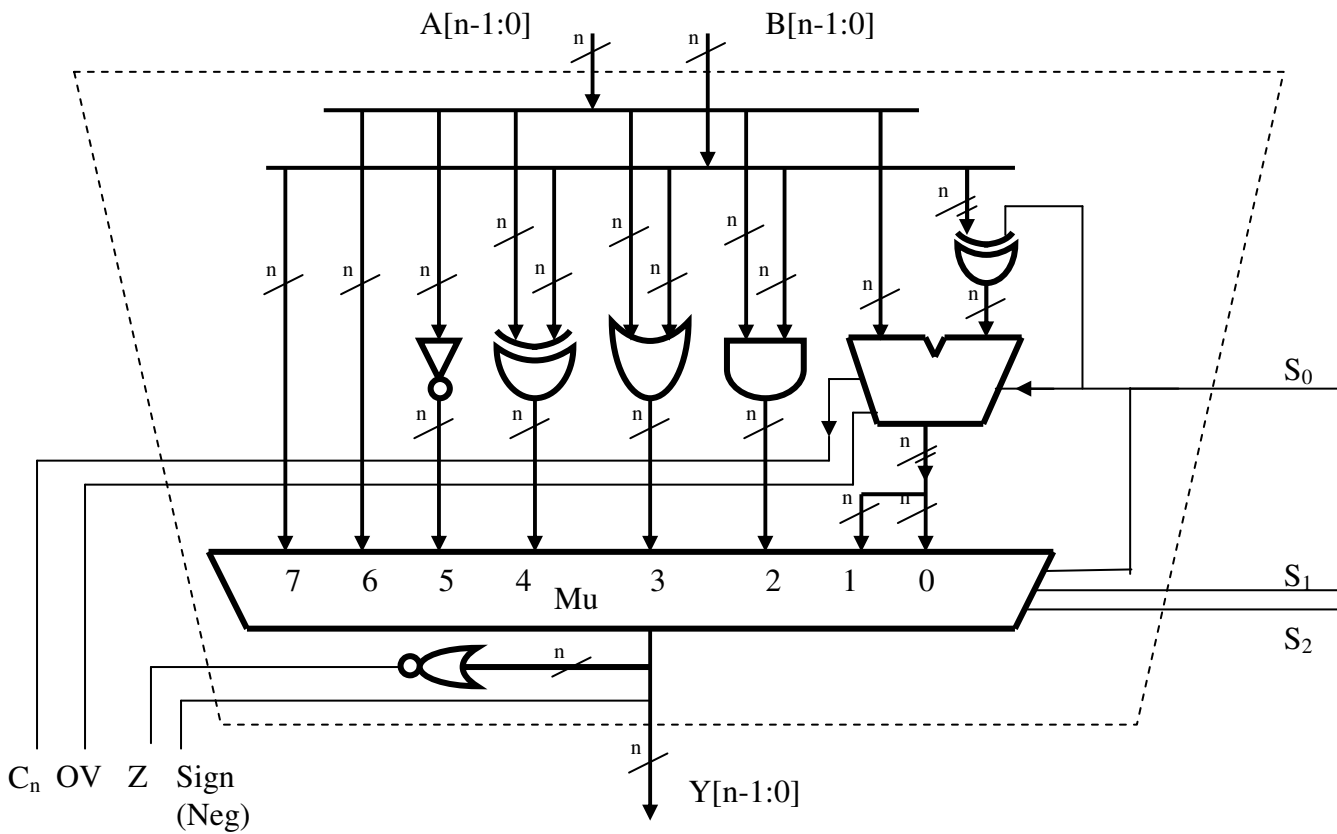


Figure 3.12 – The complete ALU

### 3.5) A Conditional Sum Adder

The idea in a Conditional Sum Adder (CSA) is to compute the addition of  $A[n-1:0]$  and  $B[n-1:0]$ , i.e., two numbers of  $n$  bits each, by parts. By that we mean that the lower half of the numbers (lets call it the LSB part of the numbers),  $A[n/2-1:0]$  and  $B[n/2-1:0]$  are added separately than the upper part of the numbers (the MSB part),  $A[n-1:n/2]$  and  $B[n-1:n/2]$ . If we split the operation into these two parts, we can use two separate adders (each adding  $n/2$  bits numbers). That way we do the computation faster since we do things in parallel (In both adders the carry propagates only half of the way, at the same time). Instead of having delay of  $D(n)$ , we'll have a delay of  $D(n/2)$ . However, there is a problem. For the MSB part, we should add  $A[n-1:n/2]$  and  $B[n-1:n/2]$  and  $C_{n/2}$ . But,  $C_{n/2}$  is available only after  $D(n/2)$ , i.e., when the LSB part calculation is finished. If we then start the calculation of the MSB part (adding the  $C_{n/2}$  takes also  $D(n/2)$ ), the total calculation time is  $D(n/2)+D(n/2)$ , and no improvement had been acquired. The solution is to calculate 3 calculations in parallel: The 1<sup>st</sup> is  $A[n/2-1:0]+B[n/2-1:0]$ . The 2<sup>nd</sup> is  $A[n-1:n/2]+B[n-1:n/2]$  and the 3<sup>rd</sup> is  $A[n-1:n/2]+B[n-1:n/2]+1$ . These 3 calculations last  $D(n/2)$ . After this time we have the 3 results and  $C_{n/2}$  as well. The result of  $A[n/2-1:0]+B[n/2-1:0]$  is  $Y[n/2-1:0]$ . We'll use  $C_{n/2}$  to select the appropriate result of  $Y[n-1:n/2]$ . If  $C_{n/2}$  is 0, we take the result of  $A[n-1:n/2]+B[n-1:n/2]$  as  $Y[n-1:n/2]$ . If  $C_{n/2}$  is 1, we take the result of  $A[n-1:n/2]+B[n-1:n/2]+1$  as  $Y[n-1:n/2]$ . This is done by adding a Mux as depicted in Figure 3.13 below. This is actually a recursive way of building a CSA.

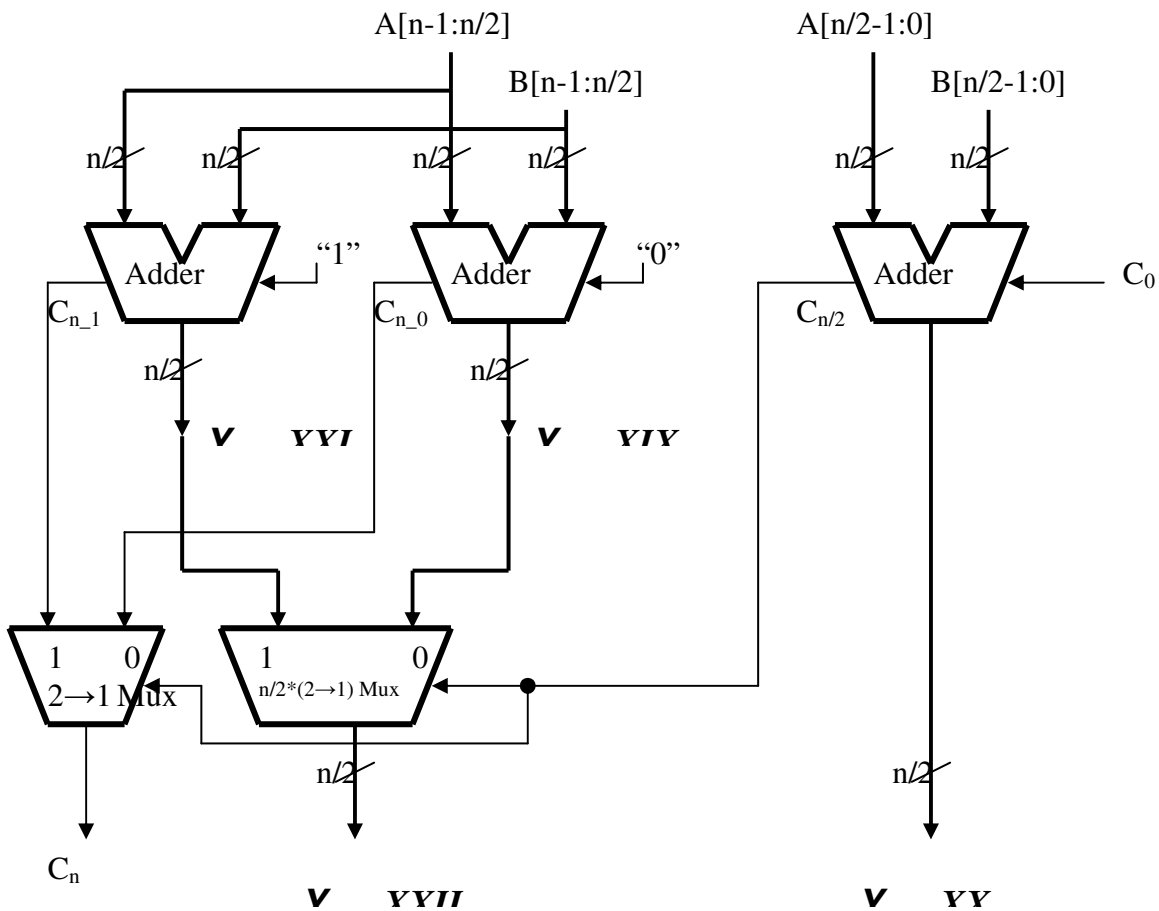


Figure 3.13 - Building a CSA YVIII

The delay is given by the recursive equation  $D(n) = D(n/2) + T_{\text{mux}}$ . This means that the delay is logarithmic:  $D(n) = T_{\text{mux}} \cdot \lg n$ . This is so since whenever we double the inputs we add a delay of a mux.

Figure 3.14 describes the entire recursion depth of a 4 bits CSA. The basic parts used are Full-Adders and Muxes.

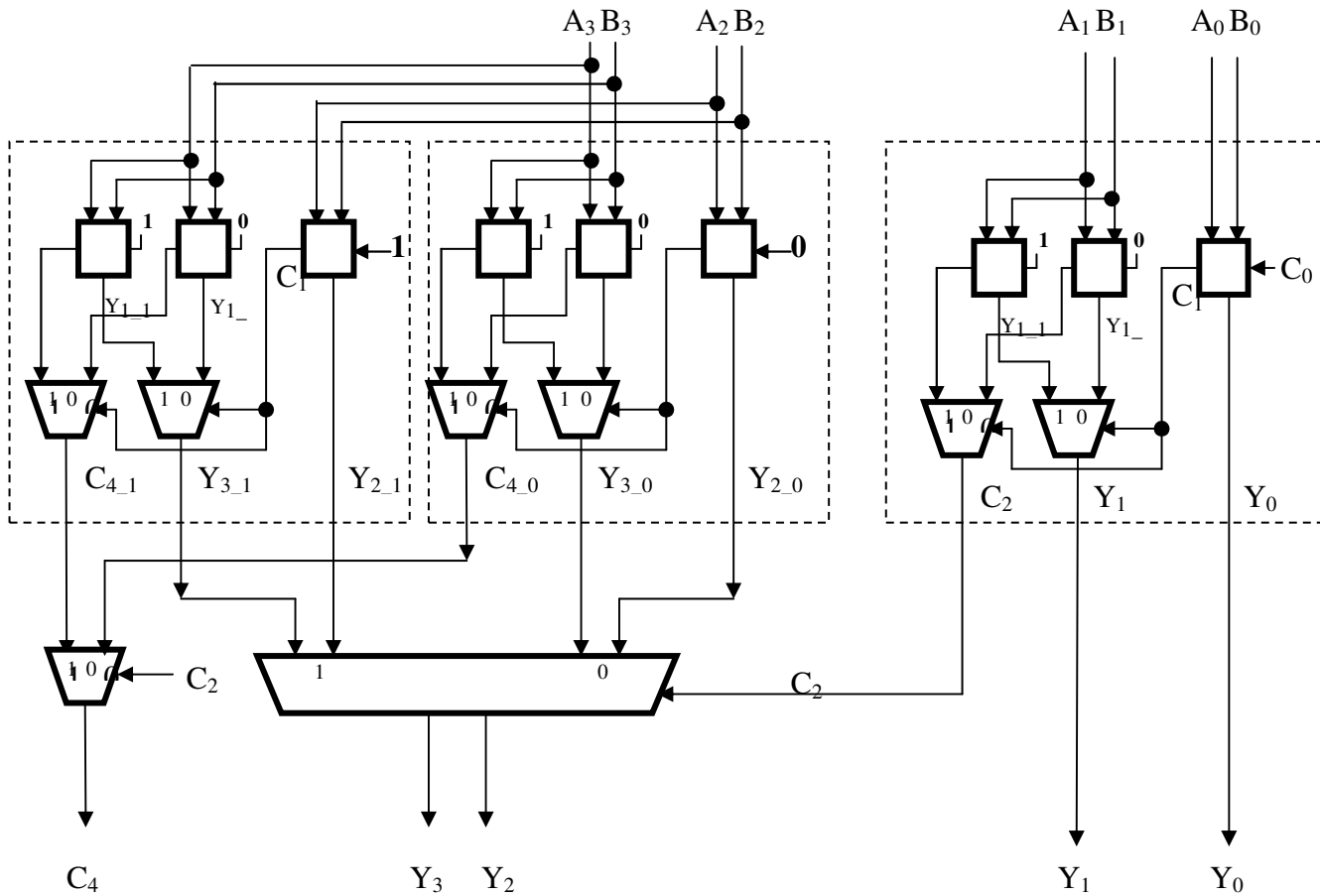


Figure 3.14 – The entire recursion in a 4 bits CSA .1

Since we have  $\lg n$  recursive stages, where in each , the number of Full-adders is tripled, we should have about  $3^{\lg n} = n^{\lg 3} = n^{1.58}$  Full-Adders in a CSA of  $n$  inputs. A similar count, reversing the order, i.e., about  $(n/2)$  Muxes at the last stage (not including the carry muxes),  $3 \cdot (n/4)$  Muxes at the one before,  $3^2 \cdot (n/8)$  Muxes before etc., which sums up to about  $n^{1.58}$  Muxes:

$$(n/2) + (3/2) \cdot (n/2) + (3/2)^2 \cdot (n/2) + \dots = (n/2) \cdot [1 + (3/2) + (3/2)^2 + \dots + (3/2)^{\lg n - 1}] = n \cdot [(3/2)^{\lg n} - 1] = 3^{\lg n} - n = n^{\lg 3} - n = n^{1.58} - n \approx n^{1.58}$$

$$\text{The carry muxes, } 1 \text{ for the last stage} + 3 \text{ for the one before the last} + 3^2 + \dots + 3^{\lg n - 1} = (3^{\lg n} - 1)/2 = (n^{\lg 3} - 1)/2 \approx n^{1.58}/2$$



Thus, the cost of such an adder is polynomial,  $C(n) = O(n^{1.58})$ . This is not a good result. We employ such a design when we need to build a fast adder using already existing smaller adders. The next adder we'll discuss has a logarithmic delay and a linear cost.

### 3.6) A Carry Look Ahead Adder

Let us try to calculate the carry of all the stages in a logarithmic time. We notice that there are two reasons for having a carry out from the  $i$ -th stage of an adder, i.e, from adding  $A_i$ ,  $B_i$  and  $C_i$ . (This addition produces a two bits number  $[C_{i+1}, Y_i]$ ). The carry  $C_{i+1}$  can be generated in the  $i$ -th stage or generated in a lower stage and propagate into  $C_{i+1}$  (through  $C_i$ ). Carry is generated only when  $A_i=B_i=1$ .  $C_i$  will propagate through the  $i$ -th stage only if  $A_i \neq B_i$ . If this is the case, we have  $C_{i+1}=C_i$ . Carry will not be generated or propagated when  $A_i=B_i=0$ . So we can write the carry equation as:

$$C_{i+1} = A_i \cdot B_i + (A_i \oplus B_i) \cdot C_i$$

We denote the AND of  $A_i$  and  $B_i$  by  $G_i$  which stands for generate. We denote the XOR of  $A_i$  and  $B_i$  by  $P_i$  which stands for propagate. So we have a new equation for the relation of  $C_i$  and  $C_{i+1}$ :

$$C_{i+1} = G_i + P_i \cdot C_i$$

Note that since  $G_i$  and  $P_i$  depend only on  $A_i$  and  $B_i$ , we can calculate all of them in parallel at the same time. Let us build a device, very similar to a Full-Adder, that calculates  $Y_i$ ,  $G_i$  and  $P_i$  (instead of  $Y_i$  and  $C_{i+1}$  calculated by a Full-Adder). Such a device is depicted in Figure 3.15 below.


 


Figure 3.15 – Y and G,P calculation

Let us now build an adder using this device.

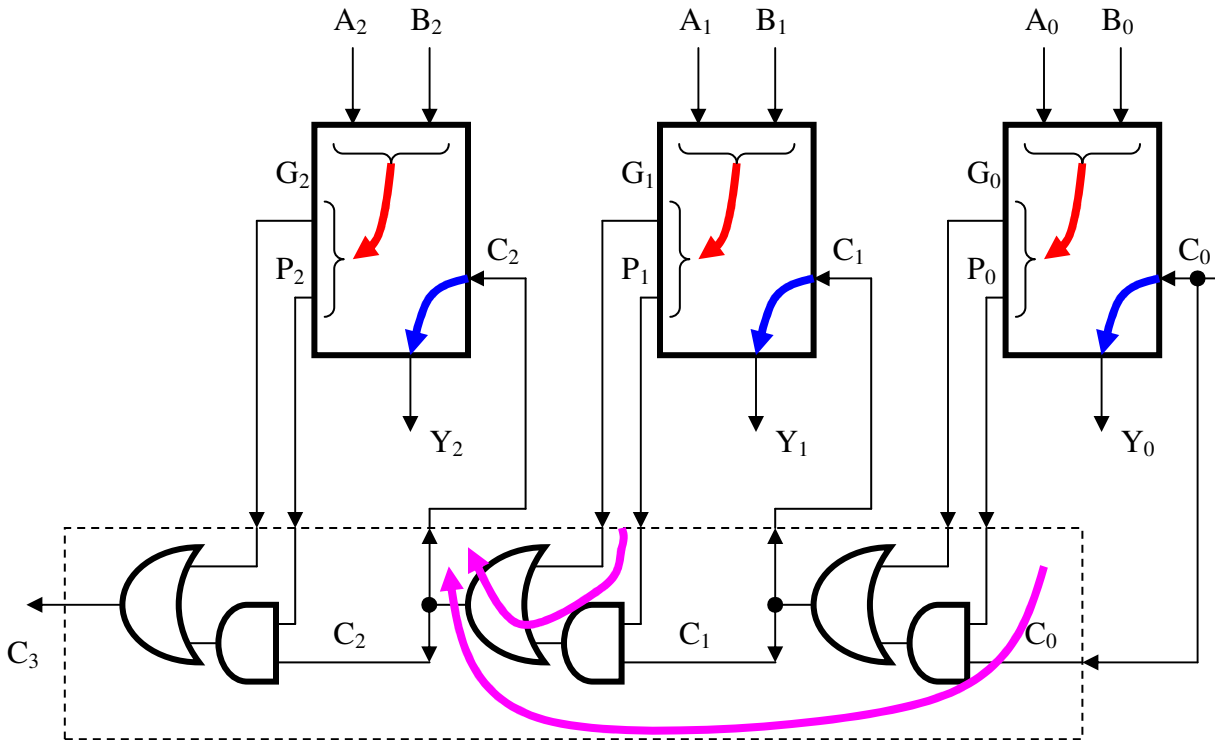

**Figure 3.16 – A Carry Look Ahead Adder**

Let us calculate the delay of such an adder. First, the  $G_i$ -s and  $P_i$ -s are all calculated in parallel (see the red lines in Figure 3.16). This takes  $T$  seconds, where  $T$  is the delay of a single gate. Then, we have to wait till the dotted box calculates all the  $C_i$ -s. Let's denote this time as  $T_{LA}$ . Following this, all the outputs become valid after an additional delay of a single gate (see the blue lines in Figure 3.16). So the delay of this adder is  $T_{total} = 2T + T_{LA}$ .

At a first glance, it seems that we earned nothing in this new design of an adder. We calculated  $C_1$  using the equation which gave:  $C_1 = G_0 + P_0 \cdot C_0$ . We calculated  $C_2$  similarly by  $C_2 = G_1 + P_1 \cdot C_1$  and  $C_3$  by  $C_3 = G_2 + P_2 \cdot C_2$ . As we see from Figure 3.16, this means that we connected the circuit in series. The delay from the minute all the  $G_i$ -s and  $P_i$ -s and  $C_0$  are ready till the time where all the  $C_i$ -s are valid, is the delay of two gates multiplied by the number of bits in the adder, i.e.,  $T_{LA} = 2nT$ . Thus the total delay of that adder is  $T_{total} = 2T + T_{LA} = (2n+2)T$ . (Actually  $T_{total} = (2n+1)T$  since  $C_n$  is calculated in parallel to  $Y_{n-1}$ ). Again we reached a situation where the delay of the adder is linear.

So, we should try to improve the performance of the dotted box. This box is called a Carry Look Ahead (CLA) circuit and this is the reason for calling this adder a CLA adder. We can easily see that it is possible to calculate the carry with a logarithmic delay:

We start with calculating  $C_1$  which is given by  $C_1 = G_0 + P_0 \cdot C_0$ .

Next, we deal with  $C_2$ . Here we have  $C_2 = G_1 + P_1 \cdot C_1$ . If we substitute  $C_1$  with the equation above, we get:

$$C_2 = G_1 + P_1 \cdot C_1 = G_1 + P_1 \cdot (G_0 + P_0 \cdot C_0) = G_1 + P_1 G_0 + P_1 P_0 C_0.$$

In the same way we get:

$$C_3 = G_2 + P_2 \cdot C_2 = G_2 + P_2 \cdot (G_1 + P_1 G_0 + P_1 P_0 C_0) = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_1 P_0 C_0$$

and:

$$C_4 = G_3 + P_3 \cdot C_3 = G_3 + P_3 \cdot (G_2 + P_2 G_1 + P_2 P_1 G_0 + P_1 P_0 C_0) = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_1 P_0 C_0$$

And eventually:

$$C_n = G_{n-1} + P_{n-1} G_{n-2} + P_{n-1} P_{n-2} G_{n-3} + \dots + P_{n-1} P_{n-2} \cdot \dots \cdot P_2 P_1 G_0 + \dots + P_{n-1} P_{n-2} \cdot \dots \cdot P_0 C_0$$

As we see from that equation, we have here AND and OR functions of up to  $n+1$  inputs. We already know that using binary trees, we can compute those in a logarithmic delay. Thus, we are sure that we can build a CLA adder having a logarithmic delay.

Note that there are many identical parts in the product terms of that equation. There is a chance that we can use this in order to produce all of the  $C_i$ -s by the same circuit (i.e., by a circuit that shares some partial products). Before we show that this can be done in linear cost, let us replace the “serial” CLA of Figure 3.16 with a “parallel” system which is possible if 3 and 4 input gates are available.

 


Figure 3.17 – A simple Carry Look Ahead circuit using multiple inputs gates

The algorithm enabling calculation of all of the carry outputs simultaneously, in a linear cost and a logarithmic delay, is called Parallel Prefix Computation (PPC).

We denote the unsigned number  $[G_{i-1}, P_{i-1}]$  as  $\sigma_i$ . Actually  $\sigma_i$  equals the sum of  $A_{i-1}$  and  $B_{i-1}$  and also equals to  $2G_{i-1}+P_{i-1}$ . (and  $\sigma_0=2C_0$ ).

We define the operation  $\otimes$  as follows:

$$\Pi_a = \sigma_a \otimes \sigma_b = \begin{cases} 0 & \text{if } \sigma_a=0 \\ \sigma_b & \text{if } \sigma_a=1 \\ 2 & \text{if } \sigma_a=2 \end{cases}$$

This operation helps us to detect whether the  $i$ -th stage has carry in its input. Let us look at  $\sigma_3$ . If it is 2, we definitely have carry at the input of the 3<sup>rd</sup> stage, i.e.,  $C_3=1$ . This is so since  $G_2=1$  (i.e., carry is generated in the 2nd stage). If  $\sigma_3=0$ , we are sure that there is no carry, i.e.,  $C_3=0$ , since  $G_2=P_2=0$  (no generation or propagation of carry in the 2nd stage). If  $\sigma_3=1$ , we do not know if we have carry or not. We know that  $P_2=1$ , i.e., carry will propagate through the 2nd stage. So we should look at  $\sigma_2$ . If  $\sigma_2=2$ , we have carry. If  $\sigma_2=0$ , we do not have carry. If  $\sigma_2=1$ , we must check  $\sigma_1$ . and so on. We therefore conclude that in order to determine  $C_i$ , the carry into the the  $i$ -th stage, we should actually look at  $\Pi_i$ , where  $\Pi_i$  is defined by:

$$\Pi_i = \sigma_i \otimes \sigma_{i-1} \otimes \sigma_{i-2} \otimes \dots \otimes \sigma_2 \otimes \sigma_1 \otimes \sigma_0$$

Since  $\sigma_0$  equals 0 or 2, all of the  $\Pi_i$ -s have values of 0 or 2. None of them can be equal to 1. Eventually, when converting back from  $\Pi_i$  to  $C_i$  the rule is therefore  $C_i="1"$  if  $\Pi_i=2$ .

Note that the operation  $\otimes$  is associative:

$$(\sigma_a \otimes \sigma_b) \otimes \sigma_c = \sigma_a \otimes (\sigma_b \otimes \sigma_c)$$

This means that the *order of computation* does not matter. Note *that the order of a, b, c* matters, i.e.,  $\sigma_a \otimes \sigma_b \otimes \sigma_c \neq \sigma_a \otimes \sigma_c \otimes \sigma_b$  !!! (e.g.,  $2 = 1 \otimes 2 \otimes 0 \neq 1 \otimes 0 \otimes 2 = 0$ ).

The operation  $\otimes$  is *not* commutative.

The associativity of the operation  $\otimes$  is easily proved by checking all of the possible cases.

Since this is so, we can calculate  $\Pi_{n-1}$  using pairs of  $\sigma$ -s:

$$\begin{aligned} \Pi_{n-1} &= \sigma_{n-1} \otimes \sigma_{n-2} \otimes \sigma_{n-3} \otimes \sigma_{n-4} \otimes \dots \otimes \sigma_3 \otimes \sigma_2 \otimes \sigma_1 \otimes \sigma_0 = \\ &= (\sigma_{n-1} \otimes \sigma_{n-2}) \otimes (\sigma_{n-3} \otimes \sigma_{n-4}) \otimes \dots \otimes (\sigma_3 \otimes \sigma_2) \otimes (\sigma_1 \otimes \sigma_0) \end{aligned}$$

Let us denote  $\sigma'_{i/2} = (\sigma_{i+1} \otimes \sigma_i)$ . So now we have:

$$\Pi_{n-1} = \sigma'_{n/2-1} \otimes \sigma'_{n/2-2} \otimes \sigma'_{n/2-3} \otimes \dots \otimes \sigma'_2 \otimes \sigma'_1 \otimes \sigma'_0$$

The following circuit uses the associativity to produce all  $\Pi_i$ -s from the  $\sigma_i$ -s recursively:

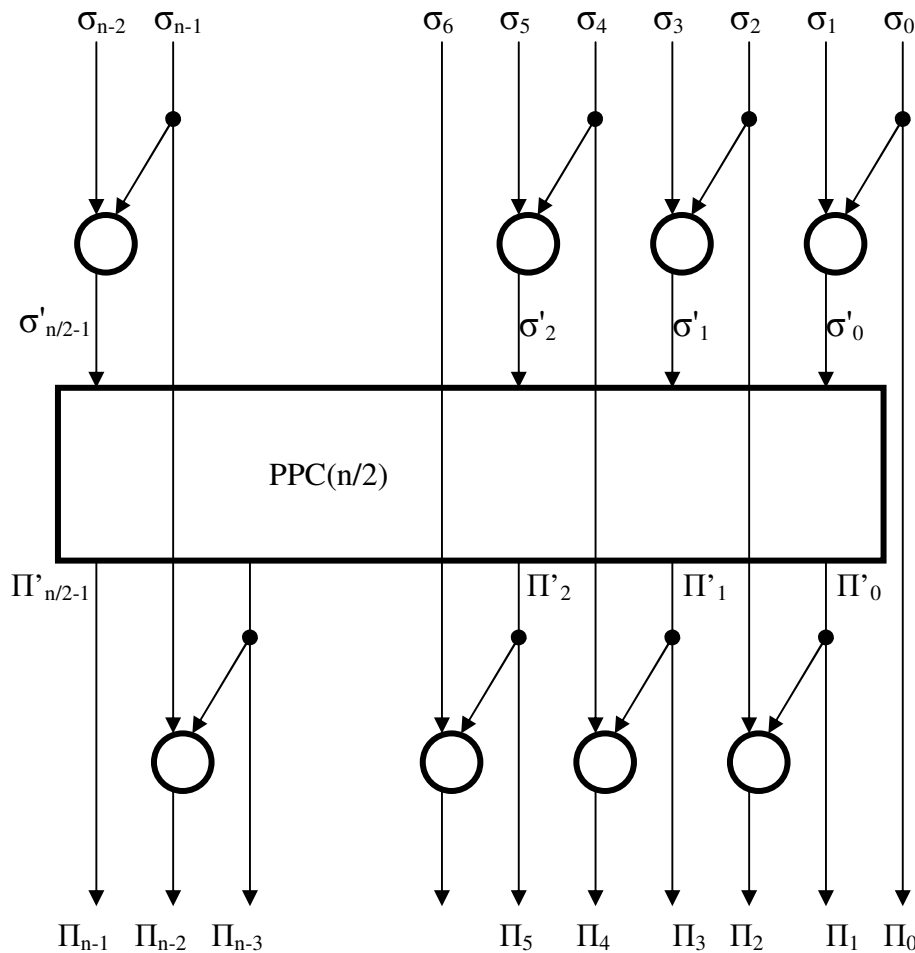


Figure 3.18 – Recursive PPC:  $\text{PPC}(n)$  built of  $\text{PPC}(n/2)$

This circuit calculates the right results since we can see that

$$\begin{aligned} \Pi_0 &= \sigma_0 \\ \Pi_1 &= \sigma'_0 = \sigma_1 \otimes \sigma_0 \\ \Pi_2 &= \sigma_2 \otimes \Pi_1 = \sigma_2 \otimes \sigma_1 \otimes \sigma_0 \\ \Pi_3 &= \sigma'_1 \otimes \sigma'_0 = (\sigma_3 \otimes \sigma_2) \otimes (\sigma_1 \otimes \sigma_0) = \sigma_3 \otimes \sigma_2 \otimes \sigma_1 \otimes \sigma_0 \end{aligned}$$

etc., and that we can also use the relation:  $\Pi_i = \sigma_i \otimes \Pi_{i-1}$ .

We immediately see that the delay follows the equation:  $D(n) = 2T + D(n/2)$  where  $T$  is the delay of the device performing the operation  $\otimes$ . Thus, we conclude that the delay is logarithmic:  $D(n) \approx 2 \cdot T \cdot \lg n$ .

We also see that adding  $n/2$  inputs caused addition of  $(n-1)$  devices which is about twice of the number of inputs we add. This means that the cost is given by  $C(n) \approx 2n$ .

This is so since  $C(n) \approx n + C(n/2) = 2(n/2) + C(n/2) \approx 2(n/2) + 2(n/4) + C(n/4) \approx 2[(n/2) + (n/4) + (n/8) + \dots + 2 + 1] = 2(n-1) \approx 2n$ .

[ The exact results are:  $D(n) = (2 \cdot \lg n - 1)T$  and  $C(n) = 2n - 2 \cdot \lg(n)$  ]

Thus, the PPC version of the carry look ahead has a logarithmic delay and a linear cost.

Calculating the  $C_i$ -s from the  $\Pi_i$ -s is easy:

$C_i = "0"$  if  $\Pi_i = 0$ , and  $C_i = "1"$  if  $\Pi_i = 2$ . As mentioned above,  $\Pi_i$  can never be 1, since  $\sigma_0$  can be 0 or 2. (I.e., if we have  $\Pi_i = 1$ , we "look" to the right and get the value of 0 or 2 from  $\Pi_{i-1}$ . Even if we get 1 and therefore should continue looking further to the right, eventually we reach  $\sigma_0$ , that by definition can be only 0 or 2).

Figure 3.19 below shows the entire recursion depth of a PPC(16).


 


Figure 3.19 – The entire recursion depth in a PPC(16)

The implementation of the  $\otimes$  operation is depicted in Figure 3.20 below.

 

**Figure 3.20 – The implementation of the  $\otimes$  operation**

Let us verify the correctness of the implementation:

- When  $\sigma_1=2$  (i.e.,  $G_1=1$ ), we have  $\Pi_1=2$  (i.e.,  $G=1$ ) as desired. (Note that in this case  $P_1$  must be 0 so  $P$  is also 0).
- When  $\sigma_1=0$  (i.e.,  $G_1=P_1=0$ ), we have  $\Pi_1=0$  as desired.
- When  $\sigma_1=1$  (i.e.,  $G_1=0, P_1=1$ ), we have  $\Pi_1= \sigma_0$  as required (since in this case we have  $G=G_0$  and  $P=P_0$ ).