 
 

Array Multipliers


Array of AND gates




Array of AND gates




Array of AND gates

 


RCA with and gates

 


RCA with and gates

 


RCA with and gates

 


RCA with and gates

 


RCA with and gates

 


RCA with and gates

 

RCA with and gates

 


RCA with and gates

 


RCA with and gates

Total delay =
 $2 \cdot n \cdot T_{FA}$


Area = n^2

 

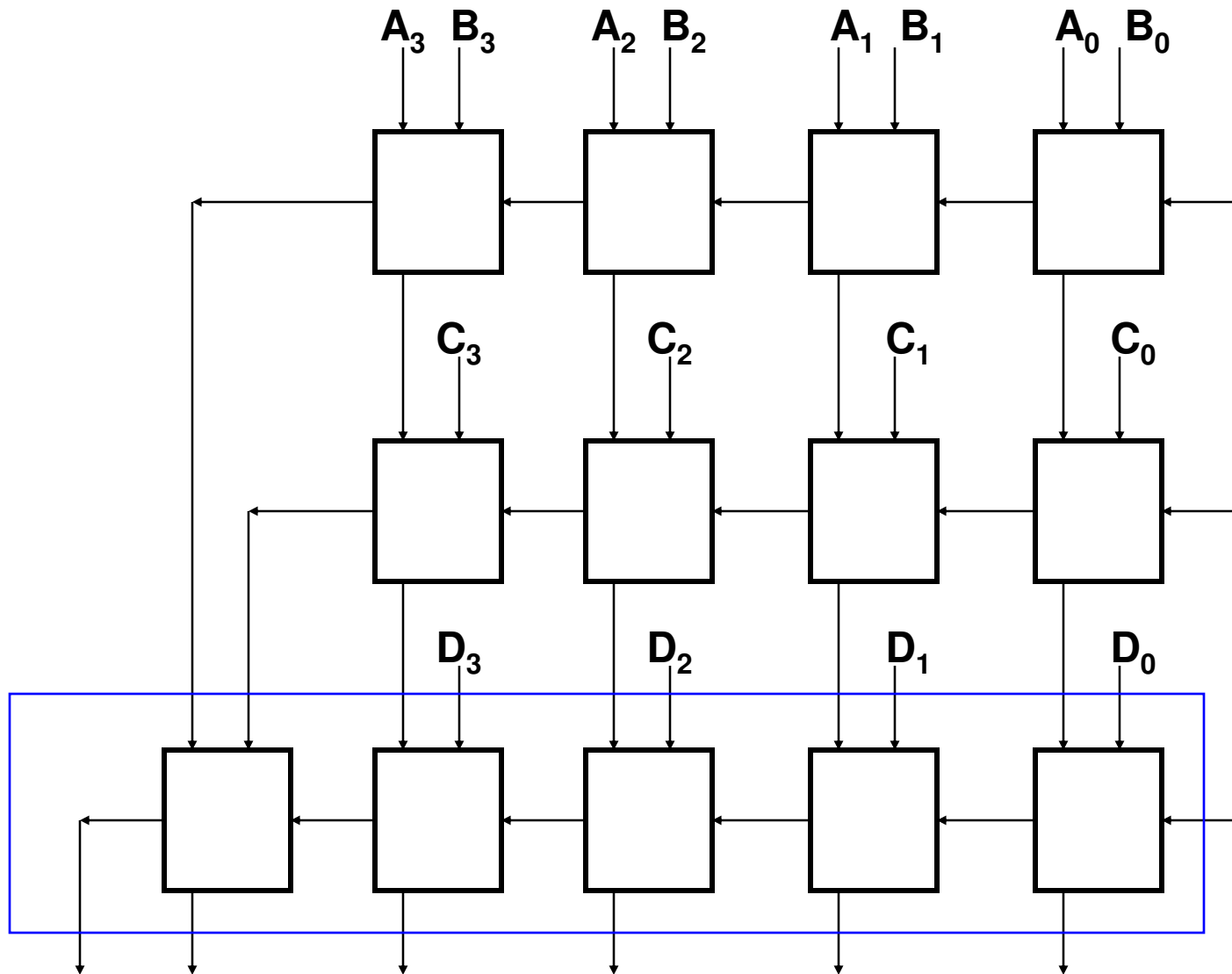Principle of CSA – add 4 numbers using a RCA





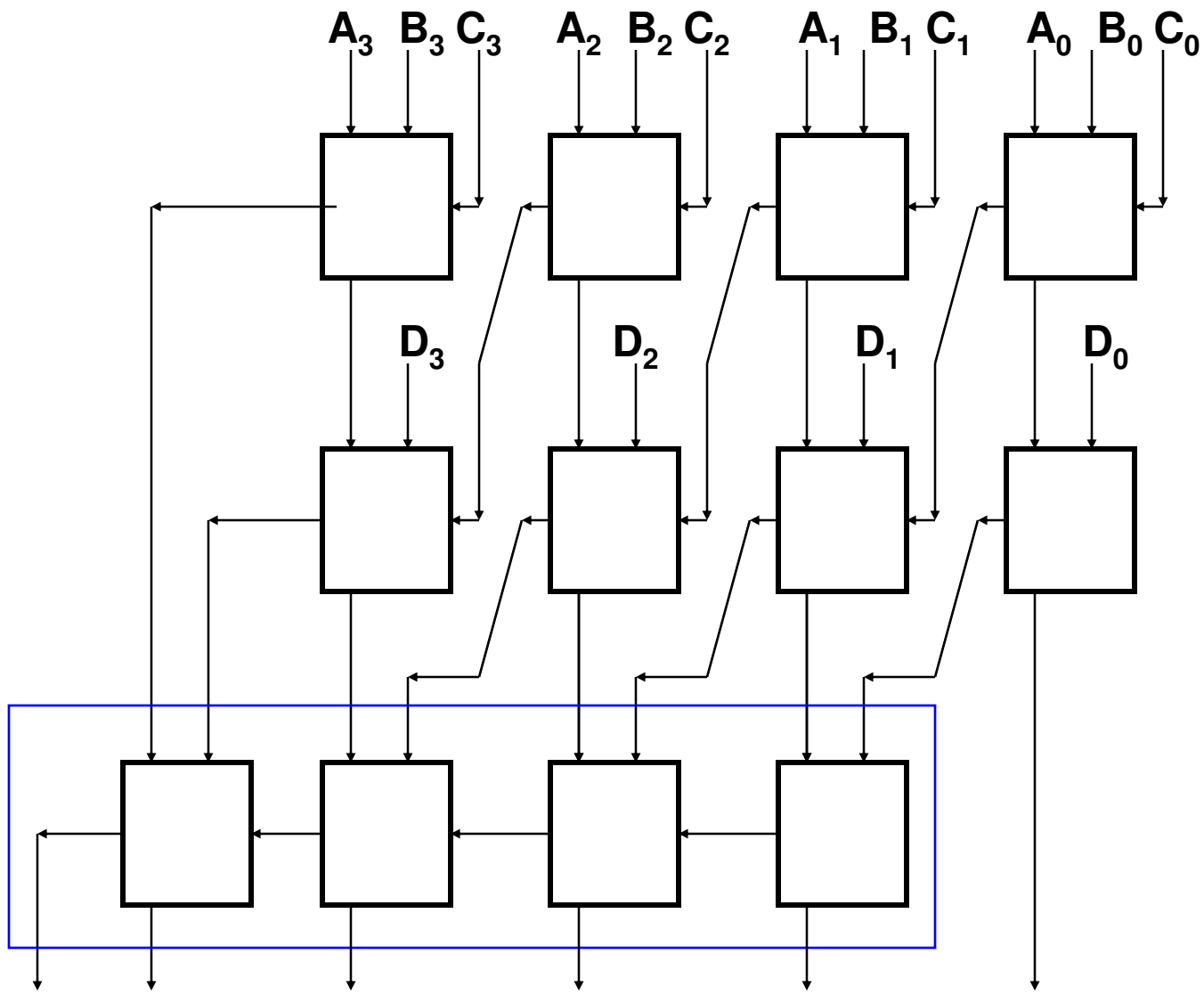Principle of CSA – add 4 numbers using a CSA





Principle of CSA


RCA delay = $2 \cdot n \cdot T_{FA}$

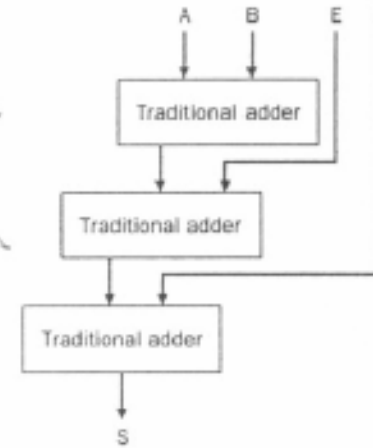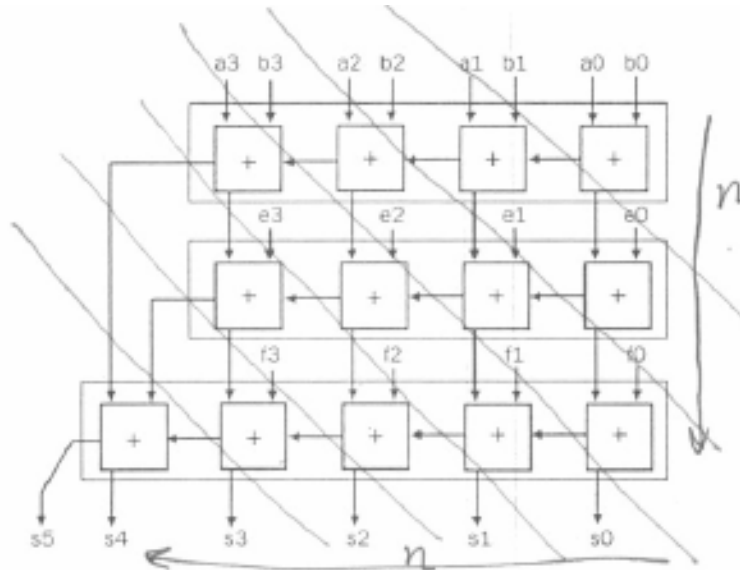


CSA delay = $(n + \lg_2 n) \cdot T_{FA}$

 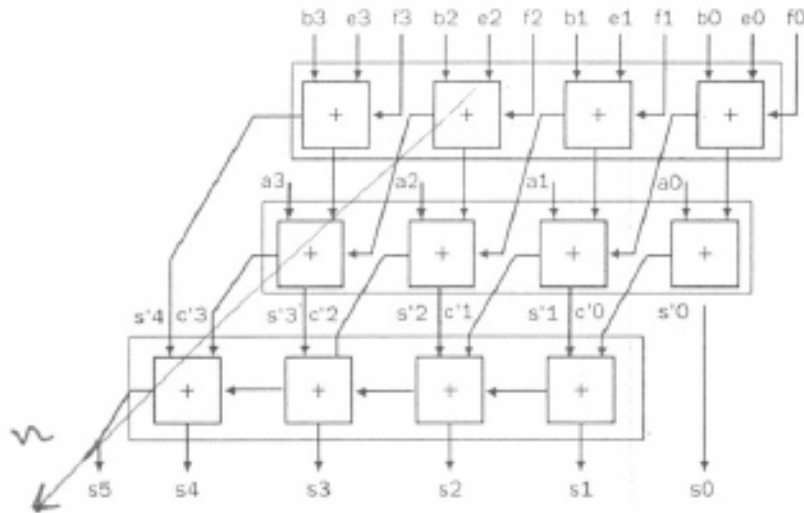


CSA based multiplier

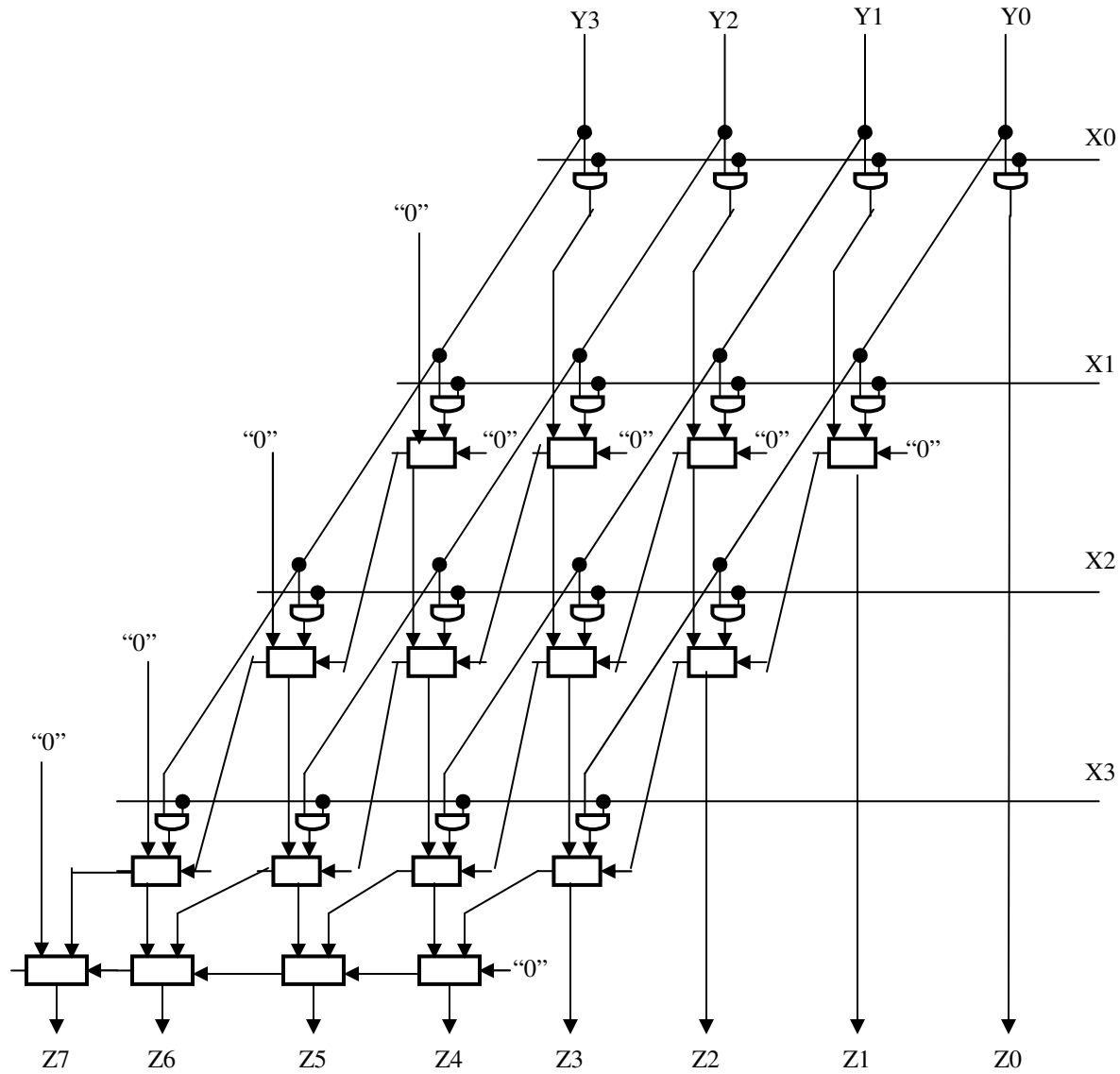


CSA based multiplier

 

CSA based multiplier

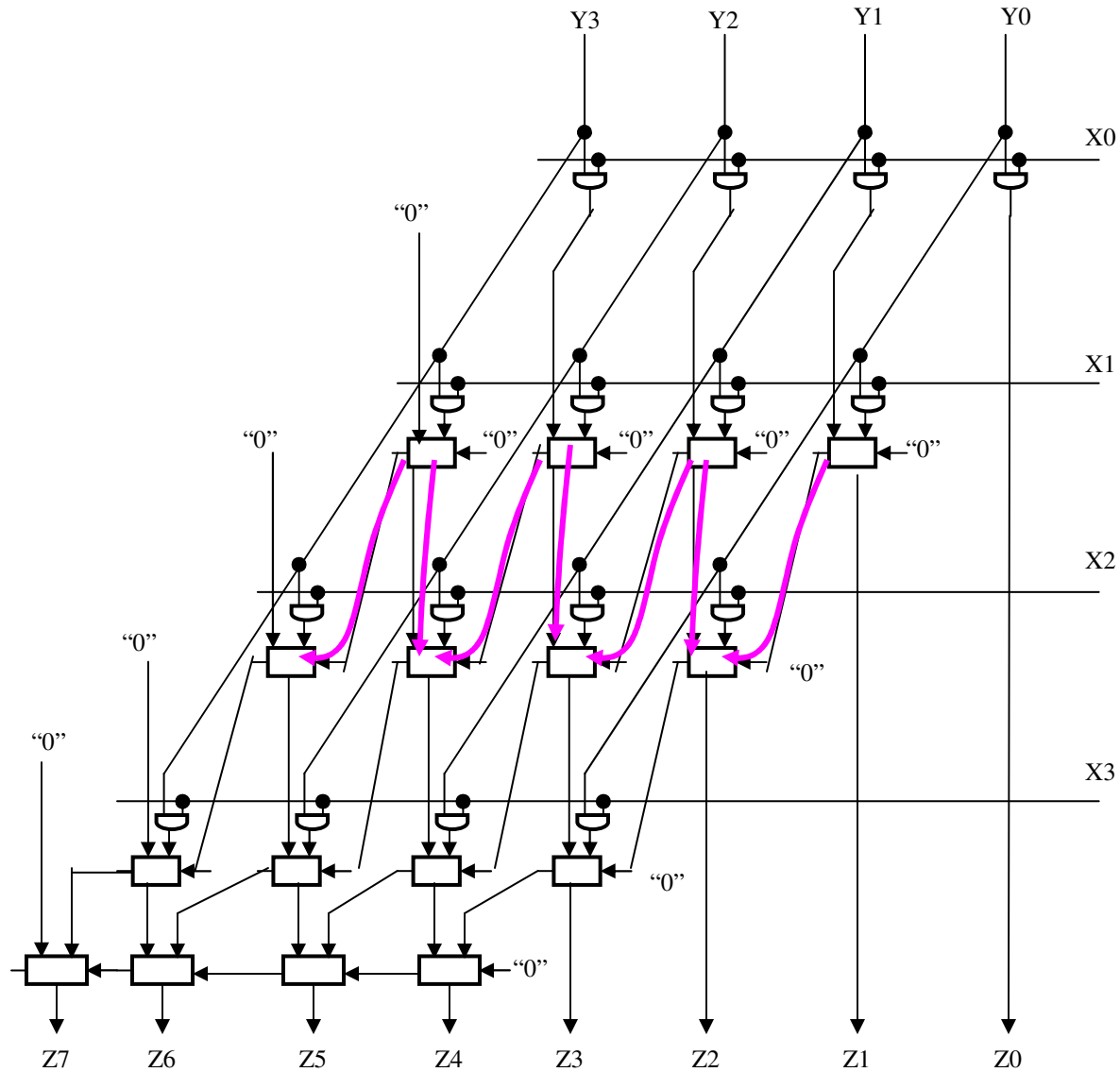

CSA based multiplier

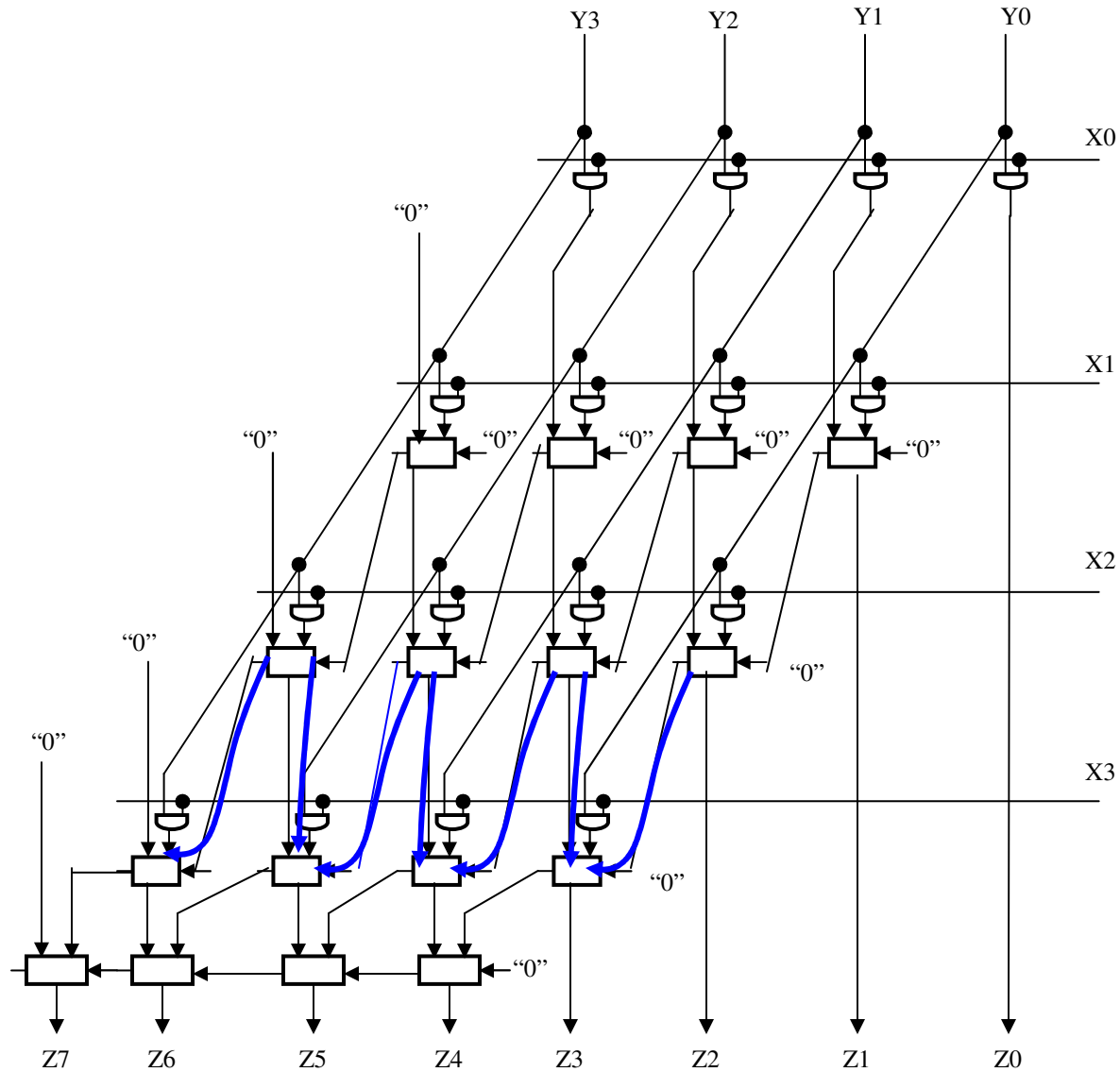

CSA based multiplier

Total delay =

$$(n-1) \cdot T_{FA} + T_{RCA} =$$


$$(2 \cdot n - 1) \cdot T_{FA}$$

Area = n^2


If CLA is used

for last step =>


$$(n + \lg_2 n) \cdot T_{FA}$$

 

CSA based multiplier

 

CSA based multiplier updated

 

Homework: $O((\log_2 n)^2)$ using CLA

Build a multiplier that adds $Y \cdot X_0 + 2 \cdot Y \cdot X_1$ and $Y \cdot X_2 + 2 \cdot Y \cdot X_3$ and $Y \cdot X_4 + 2 \cdot Y \cdot X_5$ etc., using $(n/2)$ CLAs with $(n+1)$ bits each.


Then, add the $(n/2)$ results using $(n/4)$ CLAs with $(n+3)$ bits each.

Continue till you need to add only 2 numbers.


Calculate the delay expected in a CLA has a delay of $T \cdot \log_2 n$

Signed array multiplier


CSA based signed multiplier

 

A full adder – a reminder

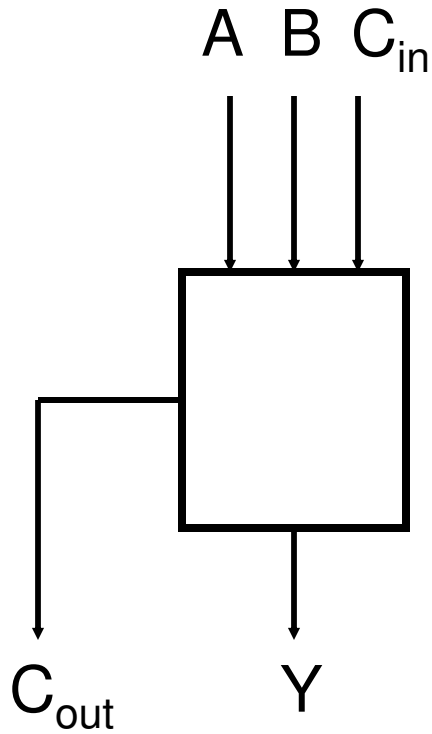

 
$$2 \cdot C_{\text{out}} + Y = A + B + C_{\text{in}}$$




$$2 \cdot Y_1 + Y_0 = A + B + C$$


A full adder – a reminder

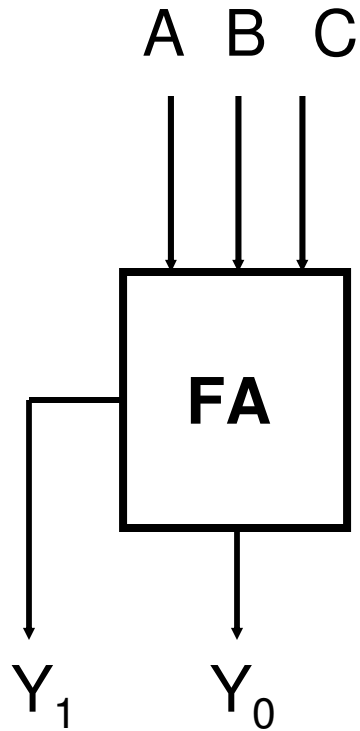

$$2*Y_1 + Y_0 = A + B + C$$

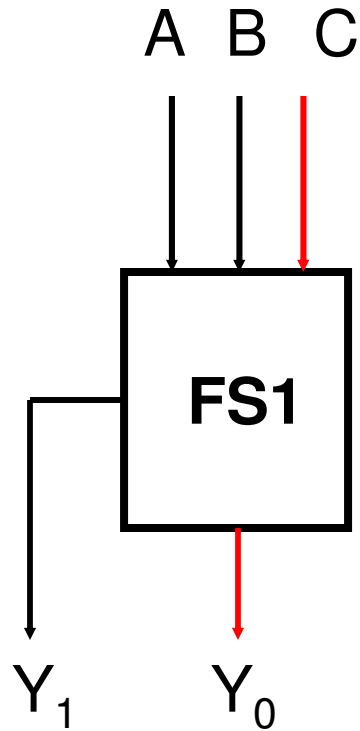


$$2*Y_1 - Y_0 = A + B - C$$

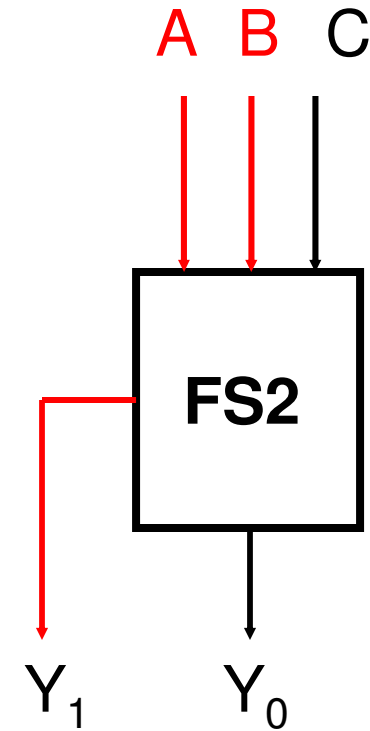


$$-2*Y_1 + Y_0 = -A - B + C$$


CSA based signed multiplier

 


CSA based signed multiplier

 

CSA based signed multiplier

 

CSA based signed multiplier

 

other array multipliers

other array multipliers

- | | |
|-------------------------------|---------------------|
| 1. Odd/Even CSA multiplier | $O(n/2 + \log_2 n)$ |
| 2. CLA binary tree multiplier | $O([\log_2 n]^2)$ |
| 3. Wallace tree multiplier | $O(\log_{1.5} n)$ |
| 4. CSA binary tree | $O(\log_2 n)$ |


And there are others!

Note: in all of the above except the Booth, we demonstrate unsigned multiplication


1. Odd/Even CSA multiplier

1. Similar to the "regular" CSA multiplier except that we add the "even" summands and the "odd" summands separately (and sum them together at the end)
2. This is done in parallel, so we get about half of the time


A regular CSA multiplier

 


Odd/Even CSA multiplier

 

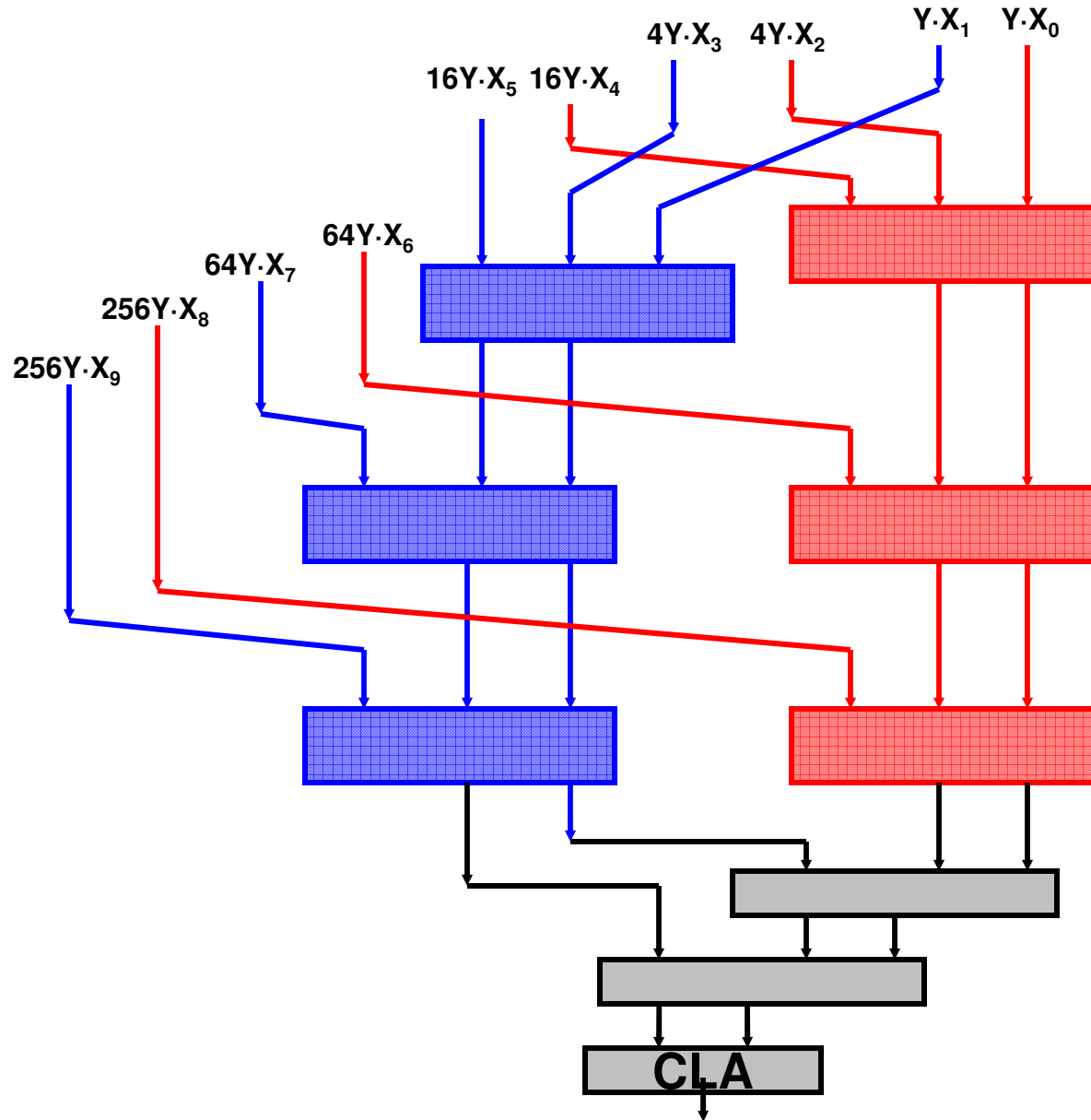Odd/Even CSA multiplier – The parallel flow



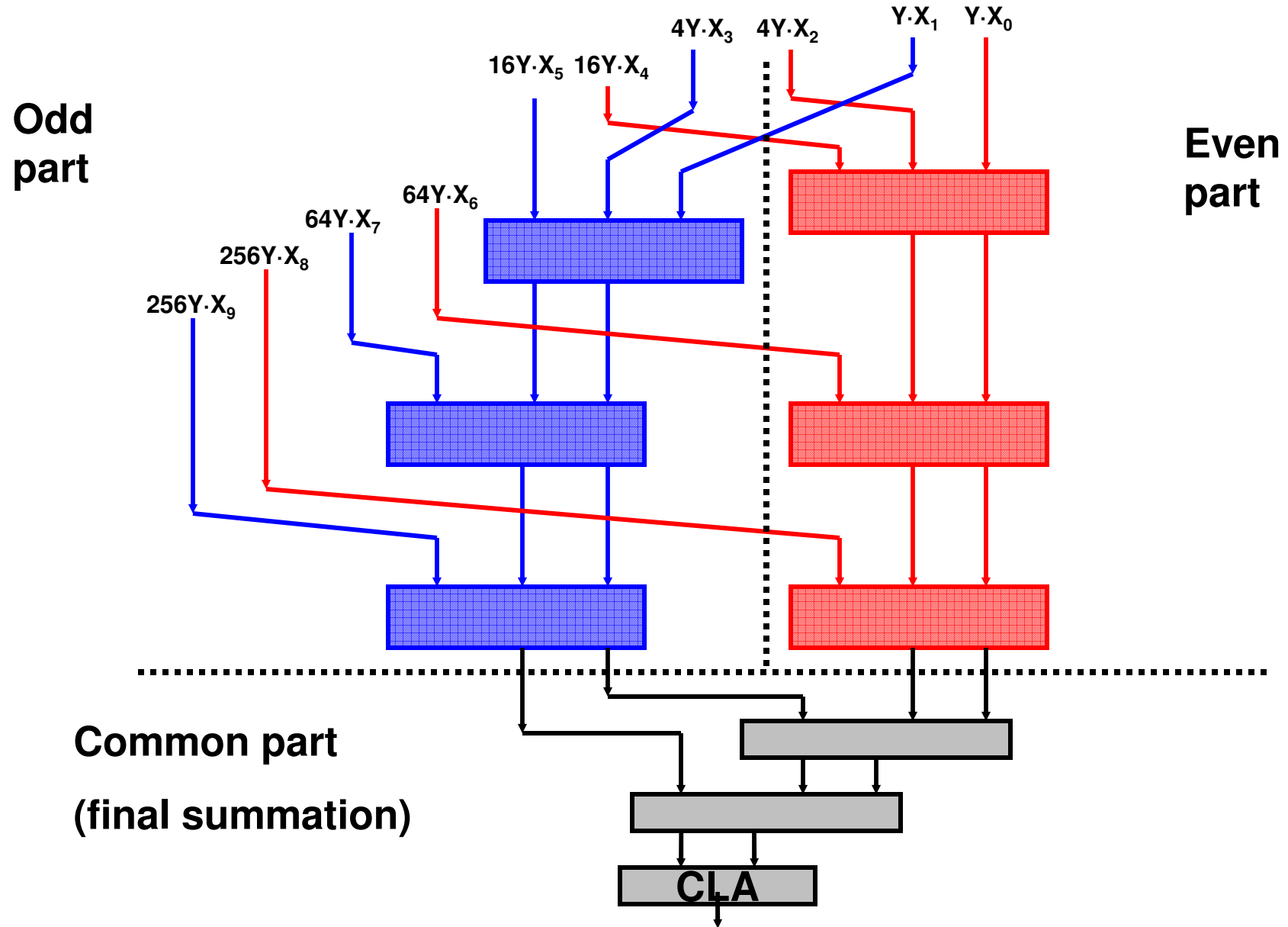Odd/Even CSA multiplier – The parallel flow



2. Binary tree with CLAs


(See homework)

1. $O([\log_2 n]^2)$
2. Use $(n/2)$ CLAs for adding $2Y_1+Y_0, 2Y_3+Y_1, 2Y_5+Y_4$, etc.
3. Use $(n/4)$ wider CLAs for adding the $(n/2)$ results
4. Continue in a tree like structure in the same manner
5. Delay is $T_{CLA} \cdot \log_2 n$ since the tree depth is $\log_2 n$
6. Since $T_{CLA} = \log_2 n$ we get $O([\log_2 n]^2)$
7. Cost is $C_{CLA} \cdot n \cdot (1/2 + 1/4 + \dots + 1/2^{n-1}) = n \cdot C_{CLA}$ (with average of 1.5n bits??) CHECK!!!

Binary tree with CLAs

All adders
are CLAs

 Delay is
 $T_{CLA} * \log_2 n$
 $= T_{FA} * (\log_2 n)^2$



Cost <

$(n-1) * C_{CLA} * 2$

3. Wallace tree = 3>2 reduction

(See Guy Even' lectures, Patterson & Hennessy Quantitative approach Fig. A.30, I. Koren, pp 88-89)

1. Delay is $O(\log_{1.5}n)$
2. Use $(n/3)$ CSAs for reducing the number of summands to $(2/3)n$
3. Use $(2/3)n/3$ 2 bit wider CSAs for adding the $(2/3)n$ results
4. Continue in a Wallace tree structure in the same manner
5. Delay is $T_{CSA} \cdot \log_{1.5}n$ since the tree depth is $\log_{1.5}n$
6. Since $T_{CSA} = T_{FA}$ we get delay of $O(\log_{1.5}n)$
7. Cost is $C_{CSA} \cdot [n/3 + (2/3)n/3 + (2/3)^2n/3 + \dots] = O(n^2)$ CHECK!!!

Wallace tree – an example – 8 summands


summands => levels:

3=>1, 4=>2, 5-6=>3,

7-9=>4, 10-13=>5,

14-19=>6, 20-28=>7,

29-42=>8, 43-63=>9

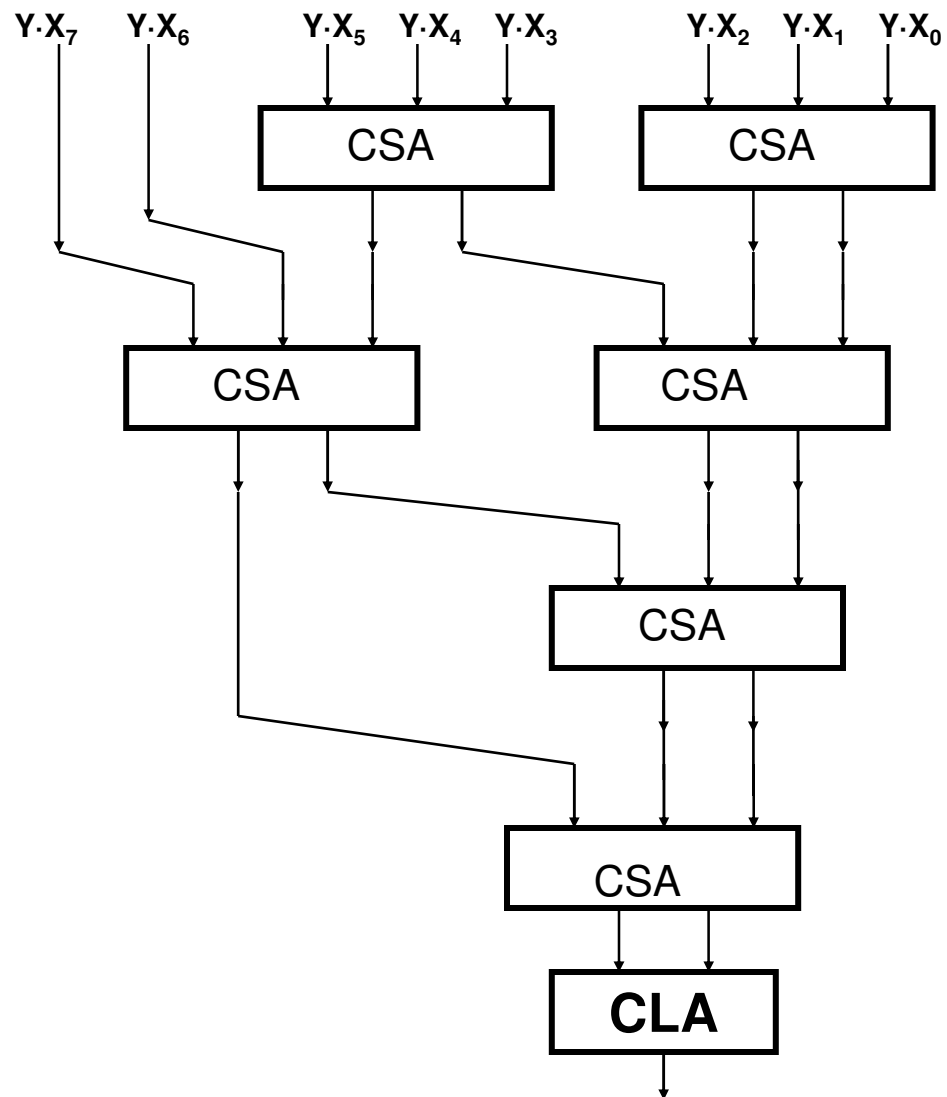

A note:

The ratio $2/3$ comes from the fact that a FA has inputs and 2 outputs


(looks like the last part of the Odd/Even CSA multiplier)

4. Binary tree with CSAs


(See Guy Even' lectures)

1. $O(\log_2 n)$
2. Use $(n/2)$ 4-to-2 CSA structure for adding $[8Y_3+4Y_2+2Y_1+Y_0]$, $[8Y_7+4Y_6+2Y_5+Y_4]$, etc.
3. Use $(n/4)$ wider 4-to-2 CSAs for adding the $(n/2)$ results
4. Continue in a binary tree like structure in the same manner
5. Delay is $T_{\text{CSA}} \cdot \log_2 n$ since the tree depth is $\log_2 n$
6. Since $T_{\text{CSA}} = T_{\text{FA}}$ we get $O(\log_2 n)$
7. Cost = $C_{\text{CSA}} \cdot n \cdot (1/2 + 1/4 + \dots + 1/2^{n-1}) = n \cdot C_{\text{CSA}}$ (with average of $1.5n$ bits??) CHECK!!!

4-to-2 CSA

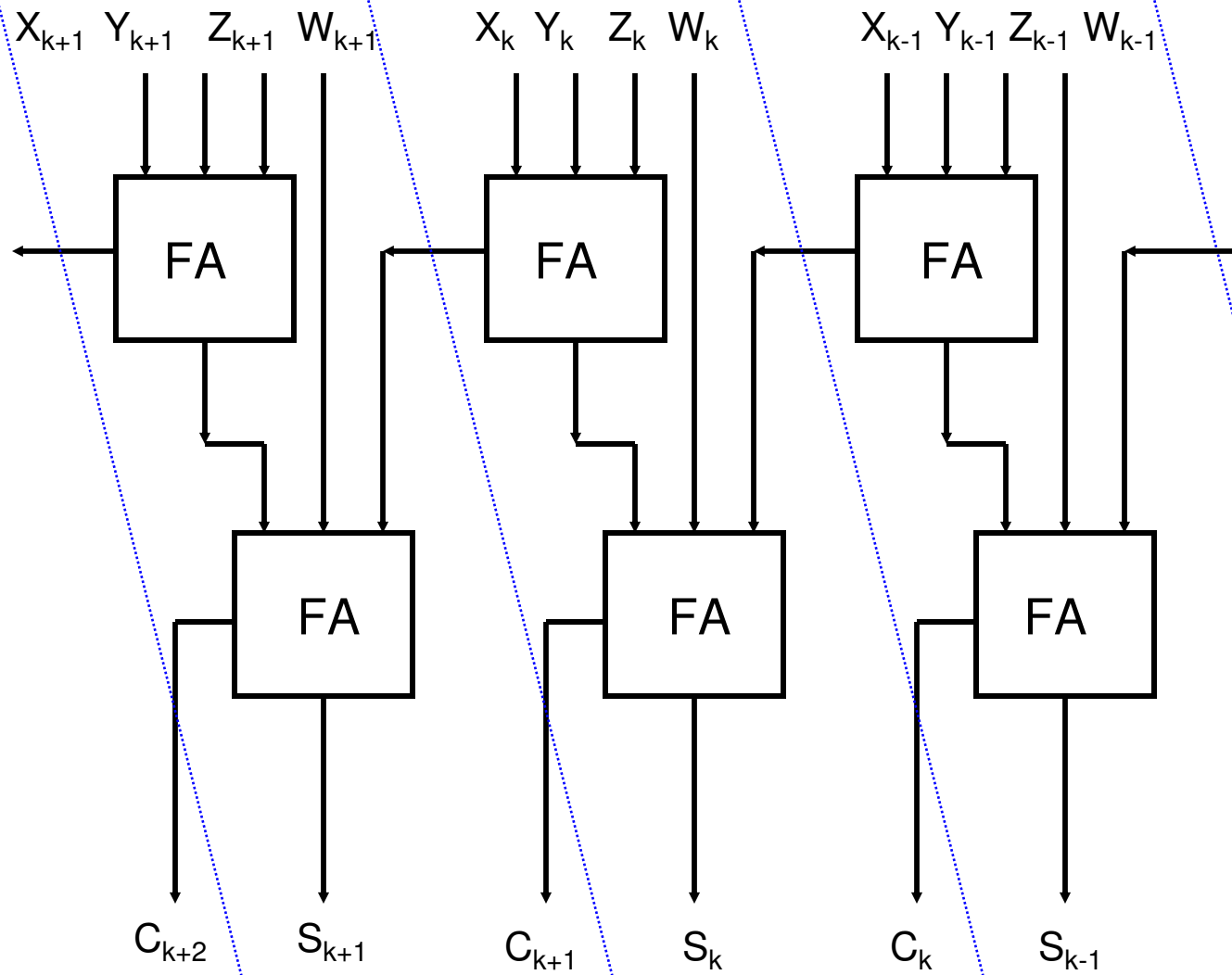

Binary tree with CSAs

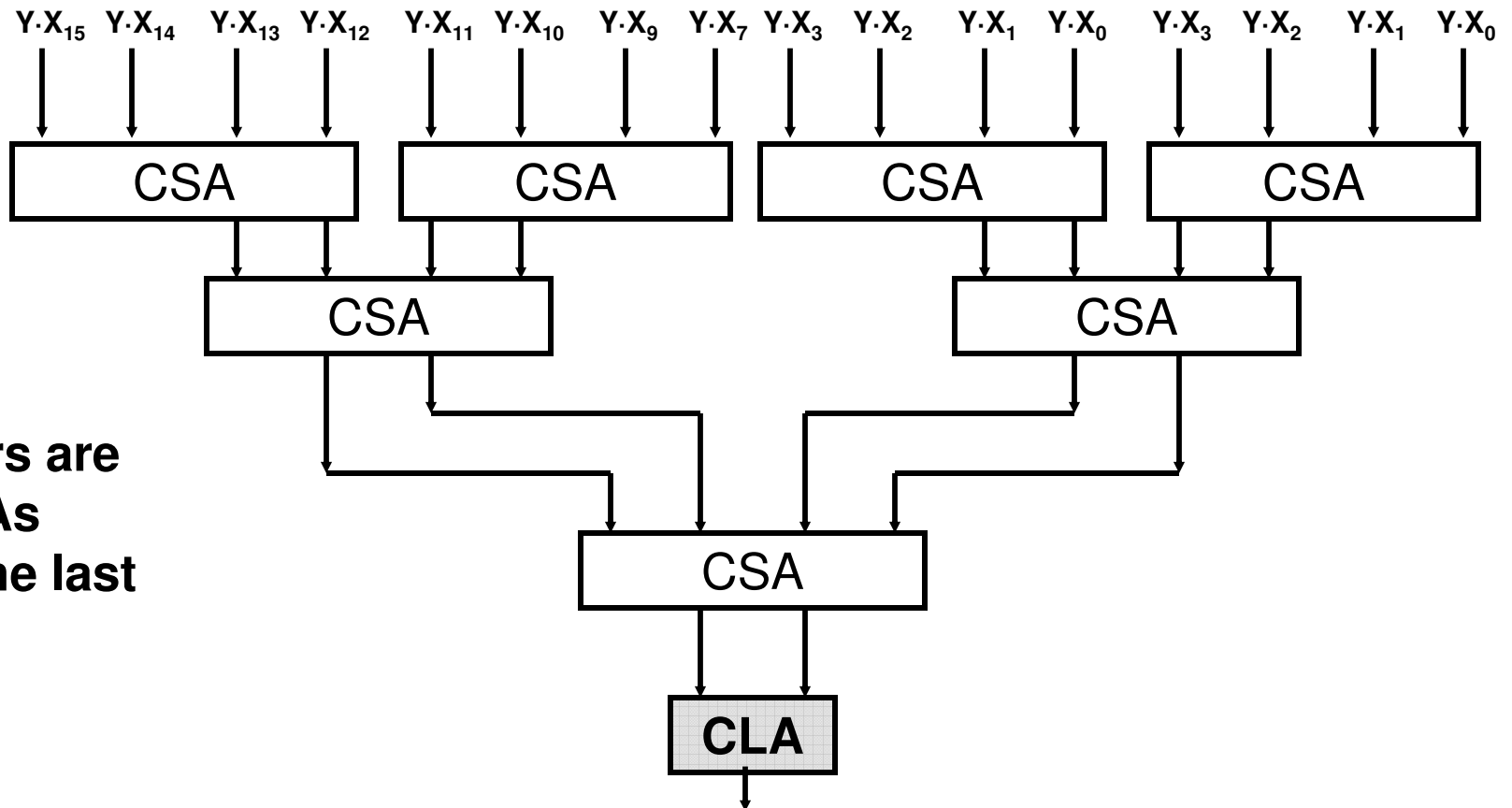

All adders are
4to2 CSAs
except the last
one

Delay is
 $T_{CSA} \cdot \log_2 n + T_{CLA}$
 $= 2 \cdot T_{FA} \cdot \log_2 n$